# **DESIGN OF A RESONANT SOFT SWITCHING POWER SUPPLY FOR STABILIZED DC IMPULSE DELIVERY**

by

Andrew H. Seltzman

A thesis submitted in partial fulfillment of the

requirements for the degree of

Master of Science

(Electrical Engineering)

at the

UNIVERSITY OF WISCONSIN-MADISON

2012

## **APPROVED**

**By** 

This thesis addresses the issues involved in the design and construction of a multiphase resonant switching power supply for delivery of a high voltage, high current stabilized DC impulse. Such a power supply may be used in place a pulse forming network (PFN) to drive a high power klystron amplifier, which typically requires voltages near -100kV at 10s of amps of current. Unlike an LC PFN, a switchmode power supply (SMPS) allows greater control over pulse duration while still allowing generation of longer duration pulses on the order of 10ms with constant output voltage by use of feedback regulation.

Specifically, the thesis documents the results from the design of a loosely coupled boost transformer with a parallel LC resonator on the secondary, a microcontroller based control system for feedback stabilization and techniques of harmonic mitigation to reduce switching noise on the output waveform.

I would like to thank Giri Venkataramanan, Paul Nonn, Bob Ganch, Jason Kauffold and Jay Anderson for assisting with this project. I would also like to thank the UW Madison Department of Physics, and Los Alamos National Lab (LANL) for providing support for this research.



















xi







- ADC Analog to Digital Converter
- DSP Digital Signal Processing
- ESL Effective Series Inductance
- IGBT Insulated Gate Bipolar Transistor
- IRQ Interrupt Request
- ISR Interrupt Service Routine
- MIPS Million Instructions Per Second
- OFC Oxygen Free Copper
- PFN Pulse Forming Network
- PWM Pulse Width Modulation
- SCR Silicon Controlled Rectifier
- SMPS Switch Mode Power Supply
- UART Universal Asynchronous Receiver and Transmitter
- ZCS Zero Current Switching
- ZVS Zero Voltage Switching

#### *0.1 Overview*

The use of resonant circuits in high voltage switching power converters allows the voltage boost ratio of the transformer to exceed the turns ratio, allowing for more compact designs and reduction of copper usage in the secondary winding. Further, the boost ratio's strong dependence on switching frequency allows the power supply to regulate output voltage by shifting switching frequency. By switching at full duty cycle near resonance, the primary voltage and current will be in phase, allowing for zero current switching (ZCS), and almost complete elimination of switching losses. As switching frequency moves away from resonance, the IGBT current at the switching event increases from zero, however with only two switching events per cycle, switching losses are considerably lower than if PWM feedback were used for voltage control. Additional benefits of resonant topologies include the strong dependence of power transfer on a matched output load; in the event of a short circuit, the resonant circuit will be de-Qed and power transfer will automatically reduce without damage to the supply or load.

The power supply described herein is a resonant three phase pulsed power converter capable of a nominal output of -80kV at 40A for 10ms. The input dc link of the power supply is connected to an electrolytic capacitor bank with a nominal starting voltage of 900V and sufficient capacitance to drive the supply for 10ms. The capacitor bank is connected to the

input of an h-bridge module that drives the boost transformers. Each transformer primary is independently driven by a dedicated IGBT H-bridge circuit that is fiber optically coupled to a microcontroller based control system. The transformers are driven with a full duty cycle square wave of varying frequency between 18.5kHz and 26kHz and have microcrystalline iron cores for low loss while providing adequate volt-seconds. Each resonant transformer has a parallel LC resonant circuit on the secondary winding. The secondary windings are configured in a Y configuration and connected to a voltage doubling three phase rectifier, where the output of the rectifier feeds a center tapped capacitor bank with the center tap connected to the Y point of the transformer secondaries. The output of the rectifier is also connected to a harmonic filter tuned to the  $6<sup>th</sup>$  harmonic of the average operating frequency to greatly reduce ripple on the power supply output. Additionally, an LC low pass filter may be connected in series with the output to further reduce ripple at the expense of a slightly increased rise time of the HV pulse.

The power supply is connected to a klystron tube load with a nominal impedance of 1800ohm through an RG-8 solid dielectric coaxial cable. An RC snubber consisting of a 400uH inductor in parallel with a 50ohm resistor prevents an HV pulse from being reflected back up the coaxial cable in the event the output of the cable is shorted to ground by an internal HV arc. Additionally, a triggerable spark gap is placed in parallel with the klystron tube to crowbar the voltage across the cathode in the event of an internal arc in order to prevent arc damage to the cathodes emissive surface.

#### *0.2 Research Contributions*

The main contributions of this research address the design and construction of a three phase resonant power supply. Specifically the contributions can be classified into the following groups:

- i. Design and analysis of a loosely coupled resonant transformer with a boost ratio that significantly exceeds the turns ratio with the capability of high voltage, high current output. The transformer in question includes a nano-crystalline iron core for low losses, and a specialized oil tank enclosing only the secondary winding for insulation and corona suppression.
- ii. Design of a suitable microprocessor based control system to generate switching signals to the IGBT module over a fiber optic link and receiving feedback signals from capacitor bank current, capacitor bank voltage, and output voltage. Maintaining good resistance to electromagnetic interference from high current switching events, and providing ground loop isolation to input signals. Providing computer control to adjust the output pulse parameters. Programing of a feedback control system to stabilize output voltage as the capacitor bank voltage decreases by adjusting switching frequency.
- iii. Mitigation of harmonic noise and ripple in the output through use of harmonic filters tuned to certain multiples of the switching frequency, inductive filers to make the output current stiff or low pass filters to selectively attenuate higher harmonics while still allowing rapid rise time at the beginning of the pulse.

iv. Design of a safety system for driving klystron tubes, that in the event of an internal arc, will cut output power from the supply, rapidly remove power from the load by use of a crowbar spark gap and prevent high voltage transients on the coaxial cable connecting the power supply to the load from being reflected back and damaging the supply.

#### *0.3 Overview of Chapters*

Chapter one presents a review of state of the art designs of high power SMPS design, topologies, and soft switching. A review of existing high power resonant SMPS designs is presented along with results from their testing. Techniques for harmonic mitigation are reviewed.

Chapter two presents the requirements and design constraints for construction of the power supply. While later chapters describe the design of the power supply, this chapter provides insight into why the power supply was designed in this particular manner based on the components available. The power supply was constructed to replace an LC based PFN for delivering power to a microwave amplifier. Requirements on the power supply include output voltage and current capabilities, fault tolerance, output voltage range, output stability, pulse duration, serviceability, safety, tolerance for voltage droop on the capacitor bank, and external control of parameters. Design constraints include the use of certain transformer cores, IGBTs, rectifier diode stacks, and capacitor banks which were either donated to the project or were available as surplus.

Chapter three presents the design of the power supply's power electronic components, transformers, filtering system and safety systems. Components include the capacitor bank's capacitor trays, bus bars and interconnecting wires, the IGBT switching network's mechanical relay, stiffening capacitors, low inductance bus plates, IGBTs, gate drivers and transformer connections, a detailed description of the resonant transformer, it's design, testing and comparison to numerical and analytical models, the three phase rectifier and it's doubling capacitor configuration, techniques of harmonic mitigation, and safety systems to prevent damage in the event of an arc fault.

Chapter four presents the design and construction of the power supplies control system. This chapter covers the microcontroller, its connecting circuits, i/o optical and galvanic isolators, and the design of the operating code.

Chapter five presents results from testing of the power supply and comparison to spice and analytical models. Models of the transformer, rectifiers, and filters are presented and compared to simulation. Open loop testing of the power supply is presented and compared to steady state spice simulations. Testing of the feedback control system and stabilization of output voltage during drooping capacitor bank in presented. Testing of the crowbar spark gam and associated LR snubber system is presented and compared to simulation.

Chapter six presents a brief summary of the research, presents conclusions and recommendations for resonant SMPS design, and outlines future research.

This chapter presents an overview of current research and development of pulsed power systems utilizing switched mode power supply (SMPS) systems for modulation and pulse stabilization. The first section presents several designs of high power SMPS, and high voltage SMPS topologies. The second section presents designs and characteristics of loosely coupled transformers. The third section covers resonant SMPS power converters, specifically a very similar design of a three phase resonant converter built at Los Alamos National Lab and results of its testing. The fourth section presents techniques of harmonic mitigation. The final section presents a summary of the chapter.

## **1.1 High power SMPS Design and Topologies**

Design of high power SMPS converters is challenging due to the high voltages and currents involved. Power electronics must be capable of multi-megawatt power transfer, sometimes at thousands of volts and thousands of amps. The majority of high voltage power converters utilize either boost, flyback, or tightly or loosely coupled transformer based topologies. Boost and flyback converters are usually limited to low power operation, while tightly coupled high voltage systems may present safety hazards in the event of an output short due to the low impedance between the primary and secondaries of the transformer.

Poly-phase resonant power converters are a new method to generate high voltages with high power while maintaining a small physical size of 10 times smaller than previous methods. Such power converters are capable of producing 10s of MWs at 100s of kV. Additional benefits include inherent fault tolerance; the power converter must be designed to be matched to a given load such that in the event of a fault, the resonant circuit will be de-Qed thereby preventing power transfer. In the event of an arc fault, the system can safely run through the fault without damage to the load or supply, while the reduction in power transfer may be sufficient to clear the arc fault. Resonant power converters with amorphous nanocrystalline iron cores maintain the high permeability of iron cores, while allowing efficient use at higher frequencies in the 10s of kHz usually reserved for ferrite materials. Consequentially, a nano-crystalline transformer can provide 300 times the power transfer capability as a 60Hz transformer for a given size and weight [1]. For comparison, a 100kV, 60Hz system carrying 20Arms and utilizing soft iron cores will be on the scale of 35 tons and have about 30kW losses while the transformer in a polyphase resonant converter operating at 140kV and 20kHz carrying 20Arms utilizing a nano-crystalline core will weight 450lbs and have about 3kW losses. Efficiency of as high as 97% may be realized with such a system. Such resonant systems can achieve significantly greater power levels with a given set power electronics in part to the resonant nature of the secondary which allows soft switching thereby reducing junction heating in the IGBTs. Given the exact nature of the system, either zero voltage switching or zero current switching may be utilized by switching the IGBTs during the period of reverse commutation of the anti-parallel diodes in the IGBT module, or by operating near resonance such that the IGBTs switch near the zero crossing period of primary current.

## **1.2 Loosely Coupled Transformers**

In contrast to closely coupled inductive systems, such as a tightly wound transformer with low leakage inductance, loosely coupled transformers provide a high leakage inductance that may be used to form a resonant circuit. In many cases efficient power transfer may only be attained if either or both the primary and secondary windings are capacitively compensated [2], described herein as a resonant transformer. In closely coupled reactive power systems, the reactive power is usually less than the real power transferred, while in certain loosely coupled systems, the reactive power can be up to 50 times the real power.

The majority of transformers used in the power supplies herein utilize a tightly wound uncompensated primary and a loosely coupled secondary with large leakage inductance and parallel capacitive compensation. Series compensation of the secondary leads to voltage source like characteristics while parallel compensation leads to current source like characteristics. Series compensation of the primary is utilized when the amplitude of the input waveform must be low, while parallel compensation is used when the primary winding must be concentrated into a small volume, thereby requiring high currents. The Q factor of a compensated winding is given by (1.1) as and is typically between 2 and 10.

$$
Q = \frac{VAR}{P} \tag{1.1}
$$

Larger secondary Q factors allow greater power transfer at the expense of a higher secondary VA utilization. The power transfer capability of a resonant transformer can be increased by increasing the VA rating of the secondary by adding more copper or core cross section, increasing the primary current or varying the coupling of the windings.

### **1.3 Resonant SMPS Power Converters**

Research in high power resonant power converters has been carried out at Los Alamos National Labs. The resonant power supply was designed to produce a high voltage pulse train of 140kV, at 1MW average, and 11MW peak that was used to drive klystron amplifiers. The output waveform was a chirp of 1.5ms pulses. The power supply drives the resonant transformers at a fixed 20kHz frequency using PWM to regulate the output waveform through feed forward and feedback techniques as shown in Figure 1.1 [3]. The supply used a resonant transformer with a nano-crystalline iron core and secondary LC resonator to achieve voltage boost to the required value. Zero voltage switching of the IGBTs was used to minimize switching losses.



Figure 1.1 Power supply output pulse without and with feedback control.

The input DC link of the power converter used a bipolar capacitor bank charged to a nominal +/- 1250 V through a three phase SCR regulator connected to a 2100V substation. The capacitor bank utilized a series of custom low inductance metalized hazy polypropylene traction capacitors, designed to clear any internal short that may occur, thereby allowing direct connection in parallel banks without individual capacitor safety fuses, which would increase inductance of the input DC link.

Each transformer was driven by an independent full h-bridge of IGBTs. The IGBTs used in this power supply were rated at 3.3kV and 1.2kA. The boost transformers utilized an amorphous nano-crystalline iron core operated at 20kHz with a bidirectional magnetic field swing of 1.6 Tesla. A parallel LC resonator was used on the secondary winding to achieve a high boost ratio. The transformers were measured to have 320W of loss per core during full power operation. The loosely coupled resonant secondary allows a boost ratio of 60:1 while using a turns ratio of 19:1 [4]. The turns ratio of the transformer is chosen to provide the required leakage inductance on the secondary to achieve a 20kHz resonant frequency with the parallel resonant capacitors.

The transformer cores were developed by National Arnold Magnetics and are constructed of 0.0008" nano-crystalline laminates for low loss at high frequency operation while maintaining a high magnetic permeability. The characteristics of the core material are presented in Table 1-1.

Table 1-1 Nano Material Characteristics [4]

Mu	50,000
<b>Lamination Thickness</b>	.0008"
Lamination Insulation	1 µM Namlite
<b>Stacking Factor</b>	$~10\%$
Bsat	12.3 kG
Core Loss (our use)	$~\sim$ 300 W
Core Weight (our use)	$\approx$ 95 lbs
Power (each core)	330 kW

The IGBT network consists of a set of 12 IGBTs configured in a set of three independent full h-bridges, with the top of each bridge connecting to the positive capacitor bank at +1250V and the bottom connecting to the negative capacitor bank at -1250V as shown in Figure 1.2.



Figure 1.2 Bipolar bank and IGBT h-bridge

The IGBTs are mounted on a low inductance buss plate with a rail to rail inductance of 4nH, allowing snubberless operation of the IGBTs by preventing overvoltage conditions generated by high frequency ringing during switching events, where dI/dt can exceed 10kA/uS [5]. Total inductance of the input DC link is further reduced by using low ESL stiffening capacitors mounted directly to the IGBT bus plates providing a total input inductance on the order of 7nH [6].

The power supply uses zero voltage switching to reduce switching losses, where primary winding current is carried by the IGBTs freewheeling diode during the switching event. The output voltage of the supply is controlled by PWM of the duty cycle of the switching period between 2.5us and 55us per half cycle which provides approximately 10% control range on the voltage output which is sufficient to stabilize output voltage during capacitor bank droop. PWM period is controlled by an adaptive feed forward / feedback system which provides very low ripple on the order of 150V. The voltage waveform on the transformer primary is shown in Figure 1.3.



Figure 1.3 Transformer primary waveform [4].

The secondaries of the transformers are connected in a Y configuration, each transformer with a parallel resonant capacitor as shown in Figure 1.4.



Figure 1.4 Three phase resonant transformer system.

The three output phases are connected to a three phase rectifier feeding a center tapped capacitor bank with the center tap connected to the Y point on the transformer secondaries as seen in Figure 1.5. The rectifier consisted of a string of 1.4kV, 75A diodes with a 50ns reverse recovery time [7].



Figure 1.5 Rectifier, doubler, filter and RL snubber.

A resistor is placed in series, forming part of a pi-R filter, along with a series inductor and shunt capacitor after the center tapped doubling capacitor. The power supply is connected to the klystron load through a coaxial transmission line and a series RL snubber.

Testing of a crowbar system demonstrated de-Qing of the resonant transformers, automatically interrupting power transfer to the klystron tube. In the event that modulation on the transformer primary continued, only a slight increase in total energy dissipated into the klystron, on the order of 10J, was observed.

Other resonant transformer topologies have been explored for high voltage, high power modulators [8]. A long pulse modulator capable of producing a 25kV, 10A pulse of 1-2ms has been developed at E2V technologies. In this system, a unipolar electrolytic capacitor bank powers three independent full h-bridges that drive a resonant LC tank circuit connected across the primaries of three ferrite core transformers. The secondaries of the transformers are connected in a Y topology with the center tap floating. The output of the transformers is then rectified with a three phase rectifier and connected to an LC low pass filter to reduce harmonics and ripple.

In this particular power supply, the input DC link is powered of a unipolar capacitor bank charged from a three phase IGBT PWM rectifier designed to maintain the capacitor bank in a suitable voltage range while drawing power from the AC mains at unity power factor to comply with harmonic and flicker regulations. The size of the capacitor bank is minimized by utilizing intelligent charging methods and designing the power converter with a suitable dynamic boost range to compensate for increased voltage droop during each output pulse. With the bank used in this power supply, a voltage droop of 25% is expected during each

pulse. The capacitor bank is comprised out of electrolytic capacitors connected to a low inductance bus plate in a unipolar configuration, and powering three independent h-bridges as shown in Figure 1.6.



Figure 1.6 Unipolar bank and IGBT h-bridge

Each h-bridge drives a resonant boost transformer, configured with a resonant LC tank circuit on the primary as shown in Figure 1.7 with each transformer primary in parallel with the capacitor in the tank circuit. The transformer is constructed out of ferrite I-bars and has single layer primary and secondary windings. The cores are magnetically independent.


Figure 1.7 Resonant primary tank circuit

The transformer secondaries are connected in a Y topology, with the Y point floating, and are connected to a three phase rectifier. Output voltage is controlled by adjusting both the phase between the primary voltage and current as well as the duty cycle of the input waveform. In order to minimize switching losses, soft switching is obtained by using ZCS during IGBT turn on and ZVS during IGBT turn off. ZCS at the leading edge is ensured by phase shifting the drive waveform so the IGBT turns on during current zero cross, while output voltage control is established by PWM of the width of the pulse. Input dc link capacitor bank voltage is adjusted so that the lagging edge of the IGBT pulse occurs when the primary current is being commuted by the antiparallel diode and zero switching occurs as shown in Figure 1.8.



Figure 1.8 IGBT current and tank voltage[9].

The output of the rectifier feeds an LC lowpass filter as shown in Figure 1.9 that acts both to reduce harmonic noise and ripple but also as the output DC link storage capacitor. The klystron load is connected to the supply by a coaxial transmission line.



Figure 1.9 Output LC filter.

Research at E2V technologies has shown that klystron cathode damage can occur if deposited energy during an arc exceeds approximately 20J [9]. A crowbar circuit has been connected across the power supply output to shunt stored energy in the LC filter's capacitor in the event of a tube arc. An unfortunate side effect of using an LC filter is that the filter's capacitor is directly connected in parallel across the klystron tube with minimal series

inductance between the capacitor and the load, thereby increasing the fraction of energy that can be dissipated into the tube before the crowbar circuit fires.

# **1.4 Harmonic Mitigation**

Reduction of switching noise and ripple in the output waveform is an important consideration when driving klystron tubes, since the tube's gain is a function of input voltage and current: such fluctuations in input voltage will result in fluctuation in RF gain generating a noisy output. Several methods of harmonic mitigation may be implemented to reduce noise and output ripple in an SMPS. The main source of harmonic noise in a three phase SMPS is the  $6<sup>th</sup>$  harmonic of the switching frequency, generated by the three phase full wave rectifier. Elimination of the  $6<sup>th</sup>$  harmonic will greatly reduce output voltage ripple. Further it is important to insure that the amplitudes of the secondary voltages are equal of the system will produce  $1<sup>st</sup>$  and  $2<sup>nd</sup>$  harmonic ripple as well [4].

The most basic methods of reducing ripple involves increasing parallel capacitance on the output DC link, however this introduces many undesirable characteristics to a SMPS driving a klystron that requires rapid output pulses. The increased capacitance provides more stored energy on the output bus that may damage the klystron in the event of an output arc [9]. Further the increased capacitance increases the rise and fall time of the pulse, wasting power and generating unnecessary heating of the klystron collector.

Another basic form of ripple control is an LC low pass filter [8]. Such filters rapidly reduce harmonic noise above their cutoff frequency, however to provide sufficient ripple reduction, the size of the parallel capacitor would increase rise time or may damage a klystron tube in the event of an internal arc, thereby requiring the use of an output crowbar circuit.

A shunt LC harmonic filter may be connected across the output and tuned to selectively filter the  $6<sup>th</sup>$  harmonic, however this filter losses effectiveness away from its resonant frequency, potently increasing noise if frequency is varies to stabilize output voltage. If the input capacitor bank is sufficient large, the switching frequency range may be placed near to the filter resonance at all times allowing the filter to reduce  $6<sup>th</sup>$  harmonic noise effectively.

Reduction in harmonics and ripples was obtained by utilizing a pi-R filter in the output, constructed by placing a 6 ohm resistor in series with the output of the rectifier stack and an LC pi filter on the output. Pi-R filters have been shown to greatly reduce output ripple while allowing fast rise times [3]. An additional benefit of pi-R filters is the ability to limit dI/dt during an output arc [7] thereby protecting the klystron from damage and increasing the probability that the fault will self-clear before the resonator is de-Qed.

## **1.5 Summary**

Techniques for designing high voltage, high power resonant SMPS have been presented in this chapter. The first section presented several designs of high power SMPS, and high voltage SMPS topologies. It was generally concluded most high voltage high power systems utilize either closely coupled transformers operating at 60Hz or loosely coupled resonant transformers with nano-crystalline cores operating at frequencies around 20kHz. The higher operating frequency allows a considerably smaller power conversion system that operates at higher efficiencies due to reduced core losses. The utilization of a resonant transformer system allows a boost ratio higher than the turns ratio, and the capability to utilize soft switching to greatly reduce switching losses.

 The second section presented designs and characteristics of loosely coupled transformers, different varieties of primary and secondary compensation, and methods of increasing power transfer.

The third section covers an in depth review of resonant SMPS power converters, including a designs of three phase resonant converters built at Los Alamos National Lab and E2V technologies, and results of their testing.

The fourth section presented techniques of harmonic mitigation, their benefits and drawbacks. It was concluded that increasing parallel output capacitance is not a feasible option due to the decreased rise time and potential to damage attached klystron loads in the event of an arc fault. Ideal candidates for harmonic reduction include pi-R filters and LC harmonic filters due to their low energy storage.

This chapter presents an overview of the design requirements and components available to construct the power supply presented herein. The first section presents the requirements and design constraints for construction of the power supply. Requirements on the power supply include output voltage and current capabilities, fault tolerance, output voltage range, output stability, pulse duration, serviceability, safety, tolerance for voltage droop on the capacitor bank, and external control of parameters. Design constraints include the use of certain transformer cores, IGBTs, rectifier diode stacks, and capacitor banks which were either donated to the project or were available as surplus. The second section presents a summary of the chosen design and the reasons certain features were selected.

# **2.1 Design Requirements and Constraints**

The power supply presented in this thesis is designed to power a klystron amplifier for a fusion power research experiment. The klystron in question requires a cathode potential of - 75kV and draws 40A of current, yielding a nominal impedance of 1875ohms. The klystron presents to a good approximation, a constant, purely resistive load with current linear to voltage within the rated operating range. Due to space constraints within the experimental area the power supply is required to have a compact design and be located approximately 30ft from the klystron tube which it powers. For safety the power supply and associated capacitor banks must be located in a caged area within the experimental area; however the system's output must be variable necessitating remote control over a computer terminal. To be placed into the requisite location in the engineering bay, the power supply must be lifted into position using a ceiling crane, favoring a light weight, modular design.

Due to the presence of high strength pulsed magnetic fields in the area, the power supply must not generate any ground loops when electrically connected to the experiment, requiring that all connections maintain galvanic isolation. Due to this requirement, all i/o lines connecting the power supply to the control system must be fiber optic, the secondary side of the power supply must get its ground from the klystron tube, and all voltage and current sensors must be galvanically isolated from the control system.

The klystron tube being powered is designed for sub-millisecond pulses, however for this experiment; the tube will be required to produce a 10ms pulse, in excess of its design specifications. Although this is permissible when using short duty cycles, it is probable that

the tube will occasionally arc internally. The stored energy in the power supply secondary must be sufficiently small so that no damage will occur to the tube. Further the power supply must be able to tolerate an arc fault that reflects a high voltage pulse back up the transmission line without damage. As the klystron gain is sensitive to voltage fluctuations, output ripple and harmonics must be minimized.

Due to budget constraints, a number of pats on the power supply were recycled from previous experiments, or donated to the project by LANL. The main capacitor bank is comprised of 450V electrolytic capacitors, each with capacitances of 1.8uF, 2uF or 2.4uF restricting the bank voltages to multiples of 450V. The capacitors were mounted in racks, with each rack containing 8 trays, with each tray containing 35 electrolytic capacitors. The bank has a total capacitance of 0.3F when configured in a 900V arraignment. Due to the configuration of the bus bars connecting the trays, it is easiest to configure the bank in the 900V configuration. A hipotronics high voltage power supply was obtained to charge the dc link input capacitor bank, capable of charging the bank to 900V.

A set of 20 matching Mitsubishi CM1200HB-66H IGBTs was donated, each rated at 3.3kV and 1.2kA with a rated pulse current of 2.4kA [A], of these 12 are used to construct a set of 3 full h-bridges. In addition, a number of 50kV 0.05uF Mylar foil capacitors, four low ESL IGBT bypass capacitors rated at 4kV, 10uF and 10nH ESL, three nano-crystalline iron cores with a length and width of 9.5" by 14" with a cross section of 2.5" by 1.75", and a three phase full wave rectifier assembly were also donated.

# **2.2 Summary**

This chapter presented the available parts, requirements, and constraints on the power supply described herein. These components and requirements formed the basis of the power supply design and governed the physical layout, dimensions and electrical parameters chosen. An electrolytic capacitor bank powered three phase resonant topology with independently driven primaries and Y connected parallel resonant secondaries was chosen. The secondaries are connected to a doubling three phase rectifier, with a pi and 6<sup>th</sup> harmonic shunt LC filters to reduce output ripple. The klystron load is connected to the power supply through RG-8/U coaxial cable and has an LR snubber in series and a triggerable spark gap snubber in parallel. The system is controlled with a fiber optically coupled microcontroller with galvanically isolated analog inputs for feedback control and fiber optic communication to the control computer.

This chapter presents the design of the resonant power supply including power electronics, magnetics, filtering, crowbar and snubber. The first section presents an overview and block diagram of the power supply hardware. The second section presents the connection and control of the capacitor charging power supply. The third section presents the design and construction of a smaller short pulse capacitor bank for safely testing the power supply and conditioning the klystron tube. The fourth section describes the design and construction of the long pulse capacitor bank including the electrolytic capacitors, capacitor fuses and connection to the bus plates, and the interconnection to the power supply. The fifth section presents the design of the IGBT switching network, its topology, the connection from the capacitor bank, the low ESL stiffening capacitors, a low inductance switching relay designed to disconnect the capacitor bank from the IGBT network, the low inductance bus plates and their insulation, the IGBTs and their gate drivers, and the connection to the resonant transformer primaries. The sixth section provide an overview of the transformer design, its nano-crystalline iron core, the design of its windings, the enclosure and insulation of its secondary winding within dedicated oil tanks, the feedthrough and cable connections to the transformers, the connection of the parallel resonant capacitors, and testing of the transformer's transfer function. The seventh section presents an overview of the doubling three phase rectifier configuration. The eight section presents filter networks for harmonic

mitigation. The ninth section presents safety systems to protect the klystron load including an LR snubber and crowbar spark gap. The tenth section summarizes the chapter.

# **3.1 Overview and Block Diagram**

The power supply is arraigned in an easily serviceable, modular design, consisting of a charging supply, a capacitor bank, three h-bridges, three resonant transformers, a doubling three phase rectifier, an output filter and a control system as shown in Figure 3.1.



Figure 3.1 Power Supply Block Diagram.

The capacitor bank charging supply charges the capacitor bank to 900V between pulses, ensuring acceptable voltage bounds during the pulse. The input DC link capacitor bank is mounted in three racks, configured as a 900V, 0.3F bank with each electrolytic capacitor connecting to the bank's bus plates using a stainless wire fuse that will open in the event of an internal short. The bank connects to the power supply using twisted pair wires which plug into the low inductance bus plates holding the IGBTs. The bus plate is connected directly to the low ESL capacitors, providing the IGBTs a stiff DC voltage source on the poles of the hbridges. The bus plate holds three full h-bridges, each driving the primary of a resonant transformer. The primaries of the transformers are electrically independent and the cores are magnetically independent. The secondaries are designed with high leakage inductance, a

parallel resonator capacitor and are connected in a Y topology to a doubling three phase rectifier. The output of the supply is optionally filtered by a pi and harmonic filter to reduce ripple and harmonic noise. The klystron load is connected to the supply by a 20-30ft long RG-8U coaxial cable. An RL snubber is placed in series with the klystron to protect the tube in the event of an internal arc and prevent HV transients from being reflected down the transmission line. A triggerable spark gap is placed in parallel with the klystron to crowbar the output in the event of an internal arc. The power supply is controlled by a microcontroller based control system that varies switching frequency to stabilize voltage output. The microcontroller varies switching frequency as a function of capacitor bank and output voltage. A picture of the power supply is presented in Figure 3.2.



Figure 3.2 Resonant power supply in construction.

# **3.2 Capacitor Charging Power Supply**

The capacitor bank charging supply charges the capacitor bank to 900V between pulses, which will be taken at very low duty cycle; one 10ms pulse approximately every 2-4 minutes. Due to the low duty cycle, the charge rate may be very slow, and the use of a linear power supply using hysteresis control is acceptable. A hipotronics 805-1A power supply as shown in Figure 3.3 capable of 1A output in the kV range will be used to charge the capacitor bank.



Figure 3.3 Hipotronics power supply.

The power supply is capable of being run directly from the AC mains and contains an internal control system to regulate output voltage. The power supply features operation off of

a 208/230VAC three phase input, 10% regulation and under 5% ripple [B]. Given that the power supply's voltage rating exceeds the voltage required on the bank, and the supply has current limiting, constant current charging may be utilized. The time to charge the capacitor bank is given by (3.1).

$$
T = \frac{CV}{I} \tag{3.1}
$$

For a 900V, 0.3F capacitor bank and 1A charging current, the power supply will be able to charge the bank from 0V to full voltage within 270s or 4.5 minutes. During cycling, the voltage droop on the bank will be a small fraction of the bank voltage allowing faster charge times between shots.

# **3.3 Testing Capacitor Bank**

In order to safely test the power supply during development, it was necessary to construct a smaller, lower capacitor bank to minimize stored energy. A testing bank consisting of 24 450V, 6.2mF capacitors configured into a 900V, 37mF bank as shown in Figure 3.4.



Figure 3.4 Testing capacitor bank.

The bank is charged by an internal rectified microwave oven transformer, with bank voltage being controlled by a hysteresis controller. The controller uses a comparator circuit to turn on the microwave oven transformer if bank voltage is below the preset voltage value. The system is designed to have 10V hysteresis.

 The capacitors are interconnected with copper bus bars and the bank is connected to the power supply with four 10 gauge wires twisted together to reduce inductance. The voltage droop on the capacitor bank may be solved for from the dissipated pulse energy, stored bank energy and power supply efficiency as seen in equation (3.2).

$$
V_f = V_i \sqrt{1 - \frac{E_{pulse}}{\eta E_{bank,i}}} = V_i \sqrt{1 - \frac{V_{out} I_{out} T_{pulse}}{\eta (1/2) C V_i^2}}
$$
(3.2)

Assuming output voltage and current are constant due to feedback control, and that the rise time is negligible, the voltage droop on the capacitor bank can be plotted vs pulse time, as shown in Figure 3.5. See matlab code in [G];



Figure 3.5 Testing bank voltage droop.

# **3.4 Long Pulse Capacitor Bank**

An increased capacitance will be required to extend the pulse duration to 10ms and beyond in order to reduce the voltage droop during the pulse to acceptable levels. The main capacitor bank consists of 450V electrolytic capacitors, each with capacitances of 1.8uF, 2uF or 2.4uF. The capacitors are mounted in racks, with each rack containing 8 trays, with each tray containing 35 electrolytic capacitors. The bank has a total capacitance of 0.3F when configured in a 900V arraignment. Each tray is connected to a set of bus bars on the back of the rack, and each capacitor is connected to the trays through a stainless wire fuse to prevent the bank charge from being shunted through a single capacitor in the event of an internal short. Assuming output voltage and current are constant due to feedback control, and that the rise time is negligible, the voltage droop on the capacitor bank can be plotted vs pulse time, as shown in Figure 3.6.



Figure 3.6 Main bank voltage droop.

## **3.4.1 Electrolytic Capacitors**

The main capacitor bank consists of 450V electrolytic capacitors, each with capacitances of 1.8mF, 2mF or 2.4mF as shown in Figure 3.7. These capacitors were arraigned into trays of 35 capacitors in three racks, with two racks containing all capacitors connected in parallel and the third rack containing two electrically separate banks. During construction it was ensured that each of the two larger banks and the two smaller banks has equal capacitance. The two half rack banks are placed in parallel with the two full rack banks, and then placed in series with each other forming a 900V 0.3F capacitor bank.



Figure 3.7 Main bank capacitors.

# **3.4.2 Capacitor Fuses**

Due to the possibility of a capacitor failure and the parallel connection of the capacitors in the bank it is necessary to individually fuse each capacitor such that in the event of a capacitor developing an internal short, the energy of the entire bank is not shunted through the failed capacitor.

Each capacitor is connected to an aluminum tray with one terminal and a bus bar above the tray through the wire fuse. The capacitor fuses consist of a stainless connecting wire between each capacitor and the bus bars on each tray that will melt open in the event of an internal short, as shown in Figure 3.8.



Figure 3.8 Capacitor bank fuses.

## **3.4.3 Capacitor Bank Bus Plates**

Each capacitor tray is connected to a set of vertical bus bars in the rear of the rack as shown in Figure 3.9 allowing the trays to be electrically connected in parallel. One bus bar is connected to the base of the aluminum trays, while the other vertical bus bar connects to the bus bars on each tray. Each bus bar is connected to low gauge interconnect cable that connects the capacitor bank racks to each other and to the power supply.



Figure 3.9 Capacitor bank bus bars.

## **3.4.4 Capacitor Bank Interconnect Cables**

The capacitor banks are connected to the power supply's low inductance buss plate over a set of four twisted wires in order to minimize inductance while allowing flexibility in the location of the banks with respect to the power supply. The effects of any inductance contributed by the interconnect cables are minimized by the DC link stiffening capacitors on the power supply.

# **3.5 Switching Network Design**

The switching network for this power supply consists of 12 Mitsubishi CM1200HB-66H IGBTs arraigned in three independent h-bridges, each riving the primary of a resonant transformer. The use of a low inductance bus plate to mount the IGBTs and the use of low ESL DC link stiffening capacitors allows snubberless operation near the transformer's resonant frequency

## **3.5.1 Topology**

The IGBTs on the bus plate are arraigned in a full h-bridge configuration with each transformer being independently driven as shown in Figure 3.10.



Figure 3.10 H-Bridge Topology.

Each IGBT has an antiparallel diode capable of commuting current during zero voltage switching during certain operating modes. Due to the low inductance of the bus plates that the IGBTs are mounted on and the presence of the DC link stiffening capacitors, snubberless operation is possible without ringing or high voltage spikes during switching events.

### **3.5.2 Cable Interconnects From Capacitor Bank**

Copper blocks located at the terminals of the low inductance bus plate allow connection of the capacitor bank cables to the power supply as shown in Figure 3.11.



Figure 3.11 Capacitor bank interconnects.

The copper blocks have holes drilled to match the oversized banana plugs on the end of the cables. The testing bank connects with two wires per terminal while the main bank connects with eight as shown in Figure 3.12.



Figure 3.12 Main capacitor bank interconnect block.

#### **3.5.3 Low ESL Stiffening Capacitor Bank**

Transition between the higher inductance electrolytic capacitor bank and the low inductance buss plates on the power supply requires the use of low ESL stiffening capacitors on the input DC link. A set of four General Atomics 37547 low ESL capacitors rated at 4kVDC, 10uF, and 10nH previously used at LANL were used as bypass capacitors [10]. The capacitors are each rated to handle high transient currents of up to 4kA, and high rms currents of 100+ amps. The capacitors are connected directly to the ends of the low inductance buss plates. In addition, a small 900V, 2mF capacitor bank is added to the buss plates to further increase capacitance as shown in Figure 3.13



Figure 3.13 IGBT bypass capacitor connection.

# **3.5.4 Low Inductance Relay**

A low inductance relay has been designed to serve as a master connect/disconnect switch capable of carrying the full current while maintaining a low inductance current path. The relay consists of a pair of 16.5" wide bus plates separated by a 1/16" of insulating G10-FR4 fiberglass. The top bus plate consists of a split input and output segment that can be connected and disconnected by physically pulling the overlapping segments of the busbar together as shown in Figure 3.14.



Figure 3.14 Low inductance relay.

The output busbar is rolled into a curved shape, so that with no pressure on it, it will disconnect from the input busbar. A pair of high strength mechanical AC relays connects the circuit by pulling a fiberglass bar against the top bus plate. The fiberglass bar is machined into a curved shape along its length and jacketed with a silicone boot to compensating for any deflection under stress and providing equal pressure to the busbar along its contact area. In this design the input and output busbars overlap by approximately 0.75" allowing the relay to carry the full power supply current. Dimensions of the relay busbar plates are given in [D].

#### **3.5.5 Low Inductance IGBT Busbars**

A voltage stiff source must be provided across the terminals of the IGBTs requiring a low inductance DC link. The IGBT busbars are designed to provide the minimum possible inductance, while allowing high current capability, physical rigidity, capability to connect to both the transformer primaries and low inductance relay with minimal added inductance and a large safety margin on insulation voltage standoff. Dimensions of the busbar plates are given in [E].

The IGBTs are arraigned into two modules, with each module containing three half hbridges. Each module consists of an aluminum plate onto which the six IGBTs are attached. The IGBT gate drives connect directly to the IGBT modules and the associated wiring is shielded from the input and output busbars with a 1/16" polycarbonate sheet. A set of 0.75" OD, 0.375" ID copper standoffs connect to the output terminals of the IGBTs through the polycarbonate insulating plates and connect to the output busbars which are then bolted down to the IGBT modules as shown in Figure 3.15. All busbar components are made out ov 1/16" thick oxygen free copper (OFC).



Figure 3.15 IGBT output busbars.

A second layer of 1/16" polycarbonate insulation is placed on top of the output busbars followed by the positive input busbar, which connects to the IGBTs with copper standoffs, followed by a third layer of polycarbonate insulation and the negative busbar as shown in Figure 3.16.



Figure 3.16 Input busbars.

Additional insulation between the busbars is accomplished by placing silicone o-rings between the layers of polycarbonate insulation so that when the busbars are tightened down,

the o-ring is compressed between the insulation layers forming an air tight seal. Additionally, overhang of the insulation layers increases the path between conductors, thereby reducing the possibility of arc tracking as shown in Figure 3.17.



Figure 3.17 Busbar layer cross section.

The two IGBT modules bolt together face to face with the positive busbars connecting with flanges near the output busbar terminals and the negative busbars connecting near the low inductance relay. The two output busbars for a given transformer are now located very close together, allowing a low inductance connection. The completed IGBT module bolts to the low inductance relay with flanged connections, allowing a low inductance connection. The insulation layers of the relay and IGBT module overlay by 0.25" preventing arc tracking at the flange connection as shown in Figure 3.18. All flange connections use pre-stressed aluminum compression bars to provide uniform force across the flange.



Figure 3.18 IGBT module connection flanges.

### **3.5.6 IGBTs and Gate Drivers**

The IGBTs used to assemble the h-bridges are Mitsubishi CM1200HB-66H modules rated at 3.3kV, 1.2kA continuous current 2.4kA pulsed current as shown in Figure 3.19. Testing at LANL has shown that these IGBTs can exceed the pulsed current rating for short duty cycle pulses used in these resonant power supplies when soft switching is used to limit junction power dissipation.



Figure 3.19 Mitsubishi CM1200HB-66H.

The IGBT gate drive signal was provided by a set of 1SD536F2-CM1200HB-66H gate drive modules manufactured by CT concepts. These gate drivers are matched to the electrical requirements of the IGBT and offer a plug and play solution. Each module can provide +- 36A of gate drive current and had 6kV isolation between any IGBT terminal and the DC power connection. Further, control and feedback of these modules is accomplished with a fiber optic interface, allowing galvanic isolation and immunity to electrical noise. The drivers allow the IGBT to achieve 15ns rise time and 20ns fall time. Full specifications are given in [F].

#### **3.5.7 Transformer Connections**

A set of intermediate busses connect the IGBT inverter module to the resonant transformers. The transformer bus connections are insulated with a sheet of fiber coated Mylar "whitepaper", allowing for a low inductance path to be maintained as shown in Figure 3.20.



Figure 3.20 Transformer connections.

# **3.6 Transformer Design**

A high power step up resonant transformer system has been designed for use on the power supply. The transformer is configured with electrically independent primaries and resonant secondaries connected in a Y configuration. Each secondary has a dedicated resonator capacitor connected in parallel across the winding as shown in Figure 3.21.



Figure 3.21 Resonant transformer configuration.

#### **3.6.1 Overview**

The resonant transformer is designed to provide a sufficient secondary leakage inductance to use in a resonant circuit by designing a loosely coupled secondary winding. The transformer is based on a nano-crystalline iron core that has a large magnetic permeability, thereby providing sufficient volt seconds for high power transfer while allowing low loss at high frequency operation. A tightly wound 10 turn primary is connected

to the IGBT inverter while a loosely wound secondary has enough privatized magnetic flux to provide a sufficiently large leakage inductance. Each secondary winding is enclosed in a dedicated oil tank for insulation and corona suppression. The transformer is pictures in Figure 3.22 and its mechanical design is presented in Figure 3.23.



Figure 3.22 Resonant transformer.



Figure 3.23 Resonant transformer design.

### **3.6.2 Nano-crystalline Iron Core**

A set of three identical nano-crystalline iron cores were donated to the project by LANL. Each core has properties as given in Table 3-1 and dimensions as given in Figure 3.24. Testing determined that the cores saturate at 5.4E-3 Volt Seconds per turn full swing, sufficient for operation at 900V, 20kHz with a ten turn primary, requiring 4.5E-3 Volt Seconds per turn.



Figure 3.24 Transformer core dimensions.

# **3.6.3 Primary Winding**

The transformer primary consists of a pair of 10 turn windings on each side of the core. Each winding used a 1/32" thick, 0.5" wide copper strap, wound in a helical manner around a 0.25" thick polycarbonate coil form. The primary is pictured in Figure 3.25 and has mechanical dimensions as given in Figure 3.26.



Figure 3.25 Transformer primary.



Figure 3.26 Transformer primary dimensions.

# **3.6.4 Secondary Winding Enclosure**

Due to the high frequency, high voltage operation, the secondary is susceptible to corona formation, potentially leading to arcing. To prevent this, each secondary in enclosed in a
dedicated oil tank with dimensions as shown in Figure 3.27. The oil tanks may be evacuated during oil filling to prevent air bubbles from being trapped in the windings.



Figure 3.27 Oil tank dimensions

### **3.6.5 Secondary Winding**

Each transformer has two loosely coupled secondaries, connected electrically in parallel. Each secondary winding is wound around a 6.5" diameter PVC coil form and consists of two layers of 22ga copper magnet wire connected electrically in parallel with a layer of Mylar foil insulation between them. Each secondary has 136 turns. The secondary winding dimensions and a picture are shown in Figure 3.28. The interior of the secondaries are lined with several axial lines of conductive copper tape which are then grounded to prevent capacitive coupling through the coil form from generating corona in the interior of the secondary oil tank.



Figure 3.28 Transformer secondaries.

### **3.6.6 Oil Tank Feedthroughs**

A set of high voltage oil tank feedthroughs have been designed to connect the transformer secondaries to the resonator capacitor banks. The feedthroughs must provide adequate high voltage insulation between the two terminals, and other conductive objects in near proximity. The oil tank feedthroughs are shown in Figure 3.29 and a CAD of the assembly is shown in Figure 3.30.



Figure 3.29 Oil tank feedthroughs.



Figure 3.30 Assembled oil tank components.

Each feedthrough consists of a polycarbonate tube housing an aluminum plug as shown in Figure 3.31. The aluminum plug maintains an oil seal to the polycarbonate tube with an oring and has a 6-32 thread on the interior for attaching to the secondary winding and a banana plug socket for connecting to the associated cabling.





The polycarbonate tubes are physically supported by a polycarbonate block with a matching radius to the oil tank that allows the block to be glued to the surface as shown in Figure 3.32. All polycarbonate components are welded together using ethylene dichloride solvent.



Figure 3.32 Polycarbonate tubes and supports.

The transformers are assembled between a pair of fiberglass support plates which bolt to the secondary oil tanks and hold the cores in place. Dimensions for the support plate are given in Figure 3.33.



Figure 3.33 Transformer support plate.

### **3.6.7 Parallel Resonator Capacitor**

The secondaries of each transformer are connected in parallel with a 0.05uF resonator capacitor assembly. Each assembly consists of four 50kV, 0.05uF Mylar foil capacitors connected in a series-parallel configuration to obtain a 100kV rating as shown in Figure 3.34. A set of rounded corona disks as shown in Figure 3.35 may be placed on the ends of the capacitors to reduce the risk of arcing.



Figure 3.34 Resonator capacitor assembly.





#### **3.6.8 Variation of Frequency, Turns Ratio, and Load Resistance**

Several iterations of transformer secondaries were tested during the design process. Secondary turn numbers between 76 and 156 were tested between 1kHz and 30kHz with load resistances between 1ohm and 60kohm. The frequency responses for transformers with a 1.8kohm load are presented in Figure 3.36, and frequency responses for transformers with a 820ohm load are presented in Figure 3.37. Far away from the resonant frequency, the boost ratio equals the turns ratio, while near resonance, the boost ratio is significantly higher than the turns ratio. Plots are generated with the matlab code found in [G].



Figure 3.36 1.8kohm frequency responses.



Figure 3.37 820ohm frequency responses.

Several analytical models for leakage inductance of the secondary were compared to measurements from the transformer. These analytical models include the long solenoid approximation (3.3), the long solenoid approximation with area compensation (3.4) where the area of the magnetic core is subtracted from the area of the secondary, making the approximation that magnetic flux is excluded from the core when measuring leakage inductance with a shorted primary. A second model for the inductance of a short solenoid was derived by wheeler in [11] and [12] is given by (3.5), with the corresponding area compensated version given by (3.6). The length of the coil, h, is given by (3.7) so that the inductance formulas may be evaluated in terms of N.

$$
L_{long} = \frac{\mu_0 N^2 A}{h_{coil}} \tag{3.3}
$$

$$
L_{long} = \frac{\mu_0 N^2 \left( A - A_{core} \right)}{h_{coil}} \tag{3.4}
$$

$$
L_{\text{wheeler}} = \frac{10\mu_0 N^2 A}{\left(9r_{\text{coil}} + 10h_{\text{coil}}\right)}
$$
(3.5)

$$
L_{wheeler} = \frac{10\mu_0 N^2 (A - A_{core})}{(9r_{coil} + 10h_{coil})}
$$
\n(3.6)

$$
h_{coil} = N \cdot D_{wire} \tag{3.7}
$$

The evaluation of these formulas is computed in matlab and plotted against measured values of inductance in Figure 3.38. The wheeler formula with area compensation is a nearly an exact match to the measured values of inductance. Note that in the matlab code, the formulas are multiplied by 0.5 since there is a parallel connection of the two separate secondary coils, thus halving the inductance.



Figure 3.38 Leakage inductance models.

 Analytical and numerical models for the transformer's transfer function were derived and compared to measured data. The final version of the transformer was chosen to have 136 turns, resulting in a primary leakage inductance of 8uH, primary magnetizing inductance of 1.69mH, secondary leakage inductance of 1.36mH, and a secondary series resistance of 1.2 ohms. A spice model of the transformer is presented in Figure 3.39.



Figure 3.39 Transformer model

A simplified model of the transformer may be obtained by approximating that the magnetizing inductance is infinite, which remains valid as long as the transformers are run without saturating the cores, that primary resistance and leakage inductance is negligibly, and that the cores are magnetically lossless. The system may then be modeled as a resonant LC tank circuit driven by a voltage equal to the primary voltage times the turns ratio as shown in Figure 3.40. The spice simulation of this model is presented in Figure 3.41.



Figure 3.40 Simplified transformer model.



Figure 3.41 Spice simulation of simplified model.

The transfer function for the simplified model may be found analytically, with the total impedance seen by the voltage source given by (3.8) and the voltage gain given by (3.9).

$$
Z(\omega) = \left[ R_{inductor} + j\omega L + \frac{\frac{R_{load}}{j\omega C}}{R_{load} + \frac{1}{j\omega C}} \right]
$$
(3.8)  

$$
G(\omega) = \frac{V_{sec}}{V_{pri}} = \frac{N}{Z(\omega)} \left[ \frac{\frac{R_{load}}{j\omega C}}{R_{load} + \frac{1}{j\omega C}} \right]
$$
(3.9)

The plot of the transfer function closely matches the measured data as plotted in Figure 3.42 with the only difference being a slightly higher boost ratio at resonance which may be attributed to the transfer function neglecting losses. This is further illustrated in a plot of the maximum boost ratio at resonance for a given turn number as shown in Figure 3.43 and the boost ratio at resonance for varying load resistance, as shown in Figure 3.44.



Figure 3.42 Comparison of transfer function and measured data.



Figure 3.43 Maximum boost ratio vs turns.



Figure 3.44 Boost ratio at resonance for varying load resistance.

The resonant frequency for the simplified system may be modeled analytically as (3.10). The analytical model matches the measured resonant frequencies with great accuracy as plotted in Figure 3.45.

$$
F_{res} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} + \frac{1}{(RC)^2}}
$$
(3.10)



Figure 3.45 Measured and calculated resonant frequency.

The analytical models found for the loosely coupled transformer system accurately match measured values and numerical simulations and may be used to design the turns ratios of such systems in the future. Such models will greatly reduce the design time of such systems by allowing the elimination of trial and error approaches to loosely coupled resonant transformer design.

## **3.7 Doubling 3 Phase Rectifier**

A doubling three phase rectifier is used to further increase the boost ratio of the system, compensating for the reduction in boost ratio that occurs when connecting the transformers to a capacitively loaded rectifier. A diagram of the rectifier configuration is presented in Figure 3.46 where the three transformers are connected in a Y configuration with the Y point connected to the midpoint of a capacitor bank across the output.



Figure 3.46 Doubling three phase rectifier.

#### **3.7.1 Rectifier Stack Design**

The rectifier stack is comprised of a series connection of a number of 1.4kV, 75A diodes providing a nominal rating of 160kV. The rectifier is capable of continuous operation when immersed in oil; however for the low duty cycle operation of this supply, they are capable of running in air. The set of rectifiers is presented in Figure 3.47.



Figure 3.47 Rectifier stack.

### **3.7.2 Doubling Configuration**

The output of the rectifier connects to a 0.05uF, 150kV capacitor bank consisting of four 75kV, 0.05uF capacitors connected in a series parallel configuration as shown in Figure 3.48. Previously utilized Mylar foil capacitors with a total bank rating of 100kV were damaged by reflected HV pulsed on the transmission line during klystron arcs; the newer capacitors provide greater resistance to damage.



Figure 3.48 Doubler capacitors.

# **3.8 Harmonic Mitigation**

The power supply is required to produce low ripple on the output due the klystron's gain dependence on input voltage. Methods of harmonic mitigation

## **3.8.1 Capacitive Loading**

Capacitive loading of the supply output by the doubler capacitors provides some mitigation of ripple, however the capacitance cannot be increased without adversely effecting pulse rise time and potentially damaging the klystron tube during an arc due to the increase in stored energy.

#### **3.8.2 Parallel LC Harmonic Filter for 6th Harmonic Mitigation**

The primary source of ripple is  $6<sup>th</sup>$  harmonic from the three phase rectifier. A series LC circuit tuned to the switching frequency, and placed across the power supply output may be used to selectively null out the sixth harmonic. The circuit may be tunable to a given harmonic frequency by use of a variable inductor as shown in Figure 3.49.



Figure 3.49 LC harmonic filter.

## **3.9 Safety Systems**

Due to the possibility of a klystron arcing, several safety systems were added to the supply to prevent damage to the klystron tube and power supply. An RL snubber placed in series with the tube will prevent an HV pulse from being reflected on the coaxial cable during an arc, and to some extent will limit energy dissipated into the tube during such a fault. A triggerable spark gap in parallel with the tube will rapidly crowbar tube voltage during a fault, preventing arc damage from occurring.

#### **3.9.1 LR Snubber**

The LR snubber is constructed with a 50ohm resistor in parallel with a 400uH inductor. The system is constructed by winding copper magnet wire around a large carborundum resistor, allowing the volume of both circuit elements to be minimized as shown in Figure 3.50. The snubber is enclosed a PVC insulation pipe for safety and mounted within the klystron cabinet, close to the cathode terminals.



Figure 3.50 LR snubber.

#### **3.9.2 Crowbar Spark Gap**

An innovative crowbar spark gap has been designed with three modes of triggering. The spark gap consists of two 4" metal balls enclosed within a polycarbonate tube. Both balls have trigger electrodes down the center with the grounded ball's trigger electrode connected to an external source and the top trigger electrode connected to across a 3mH inductor in series with the klystron tube. In event of an internal arc, the rapid di/dt will fire the top trigger electrode by providing a high voltage difference across the inductor. A 5nF capacitor in series with the trigger electrode will prevent current from being shunted through the trigger electrode. In the event of overvoltage, the gap will breakdown without a trigger source. In the event that an arc is detected first by external equipment monitoring the klystron RF output power, the bottom trigger electrode may be fired. The HV trigger pulse is generated by an SCR discharging a capacitor through a step up transformer. The SCR is

triggered by a fiber optic receiver. When the gap fires, a current sense transformer sends an output pulse on a fiber optic cable connected to the supply's control system, which will then terminate power transfer. A schematic of the gap is presented in Figure 3.51 and a picture of the gap is presented in Figure 3.52



Figure 3.51 Spark gap schematic.



Figure 3.52 Spark gap.

### **3.10 Summary**

This chapter presented the design of the resonant power supply including power electronics, magnetics, filtering, crowbar and snubber. A capacitor charging power supply was chosen to provide constant current charging ability to bring a 0.3F electrolytic capacitor bank up to 900V. The capacitor bank is sized appropriately such that the voltage droop during a 10ms pulse is acceptable. Each capacitor is individually fused for safety in the event of an internal short. The power supply drives the transformers through a set of three independent h-bridges and utilizes low inductance busbars and DC link stiffing capacitors. A low inductance relay is designed to disconnect the capacitor bank from the IGBT network when not pulsing. Gate drivers providing fiber optic isolation and control as well as rapid switching time were chosen for their plug and play functionality. The final design of a resonant transformer, its nano-crystalline iron core, the design of its windings, the enclosure and insulation of its secondary winding within dedicated oil tanks is described. Numerical and analytical models of loosely coupled resonant transformers were developed. Configuration of a coupling three phase rectifier configuration and filter networks for harmonic mitigation are presented. Several safety systems to protect the klystron load including an LR snubber and crowbar spark gap have been developed and installed in the system.

This chapter presents the design of the resonant power supply's control system. Section one presents an overview of the control system design. Section two presents the specifications and capabilities of the microcontroller used in the control system. Section three presents the analog isolators for the feedback control signals. Section four presents the feedback voltage dividers that measure voltage at the klystron tube, power supply output and capacitor bank. Section five presents current measurement systems for capacitor bank input current. Section six presents the fiber optic I/O isolators. Section seven describes the microcontrollers operating code. Section eight summarizes the chapter.

# **4.1 Overview**

The control system for the power supply is designed around a dsPIC30F2020 microcontroller due to the controller's built in peripherals. The microcontroller was specifically designed for SMPS control, including such features such as phase locked PWM generators, high speed analog to digital converters, and general purpose peripherals such as UARTs, timers, interrupt controllers, and oscillators. The microcontroller board is mounted in a shielded metal box with internal power supplies, analog isolator modules fro ground loop isolation and a fiber optic I/O system allowing the system to interface with the IGBT drivers and receive trigger or fault signals. A picture of the control system is presented in Figure 4.1.



Figure 4.1 Control system.

## **4.2 dsPIC Microcontroller**

Use of a high performance microcontroller specifically designed for SMPS operation allows a small compact system to be designed with minimal external equipment. A dsPIC30F2020 microcontroller manufactured by Microchip was chosen as the basis of the power supply's control system due to its small size, low cost, high processing speed of 30MIPS, built in DSP functionality, high speed ADC, and built in SMPS control modules. A datasheet for the microcontroller is given in [M].

The dsPIC microcontroller has several features designed to optimize performance in SMPS designs. The pinout of the microcontroller is given in Figure 4.2. The microcontroller is available in a 28 pin DIP package allowing easy integration and prototyping.

**Pin Diagrams** 



Figure 4.2 dsPIC30F2020 pinout.

The microcontroller has an internal fast RC oscillator allowing 30MIPS operation without use of an external crystal. A 10bit, 2msps ADC provides rapid sampling of analog inputs and allows the use of digital filters. The ADC can sample from 8 pins and can sample up to two inputs simultaneously. The system provides the option to synchronize ADC

sampling between switching events to prevent interference from switching transients. A set of three built in timers allows accurate timing of output pulses and repetitive triggering of interrupts for i/o operations. A built in UART allows communication over a serial bus for computer interfacing.

Most importantly, this series of microcontroller has a built in SMPS controller with 4 pairs of PWM outputs with the ability to synchronize the time bases and phase offsets between the different channels. Further, the PWM periods can be set to only update at the switching boundaries. These features are critical for use on this power supply since they ensure that the three separate phases will always remain 120 degrees apart, and that changes in PWM period will only occur near zero current, so that soft switching may be maintained.

A block diagram of the microprocessor hardware is shown in Figure 4.3.



Figure 4.3 Microcontroller subsystem block diagram.

# **4.3 Analog Input Galvanic Isolation**

Due to pulsed magnetic fields in the experiment area, isolation between the input and output of the power supply is required to prevent ground loops. As such the high voltage dividers providing voltage feedback to the control system must have their ground connection isolated. A set of four isolator boards using Analog Devices AD215BY isolator modules are connected between the voltage dividers and the microcontroller to provide noise filtering and ground loop isolation as shown in Figure 4.4. The isolator module has  $a +15$  volt dynamic range and a 120kHz bandwidth. A set of op-amp based analog filters limits the gain to 100kHz, while allowing signal amplification between a gain of 1 and 1000. A block diagram of the AD215 is provided in Figure 4.5. A data sheet for the AD215 is provided in [L].



Figure 4.4 Isolation modules.



Figure 4.5 Isolator block diagram.

# **4.4 Feedback Voltage Dividers**

A pair of voltage dividers is used to allow the control system to monitor voltage at the power supply output and at the klystron cathode. A 10000:1 Ross engineering voltage divider provides a high bandwidth measurement of output voltage while a custom voltage divider consisting of a high voltage resistor-capacitor divider with a Tektronix P6015A, 1000:1, 40kV high voltage probe connected to the half-way point extends the probe's range to 80kV and increases the division ratio to 2000:1 while maintaining the probe's original high bandwidth characteristics. Both probes are shown in Figure 4.6.



Figure 4.6 High voltage probes.

# **4.5 Current Measurement**

Capacitor bank current is measured with a Pearson electronics 301X current transformer, providing a 0.01V/A output. The transformer mounts on the power supply frame next to the low inductance bus bars and the positive cable from the capacitor bank passes through the center as shown in Figure 4.7. The transformer is rated at 50kA peak current, with a droop rate of 3% per millisecond and has a current time product of 22kA-ms. The low and high frequency -3dB points are 5Hz and 2MHz. A complete data sheet is provided in [K]



Figure 4.7 Pearson transformer.

# **4.6 Fiber Optic I/O**

In order to maintain galvanic isolation between the control system and the IGBT drivers, as well as peripheral equipment the control system uses a digital fiber optic isolator system as shown in Figure 4.8. The isolator converts fiber optic signals to TTL logic levels for interfacing with the microcontroller. The isolator consists of four boards, two transmitter boards and two receiver boards. Each board has 10 channels and provides an LED indicator of each channel's status to aid in diagnostics. The circuit diagram for the fiber optic interface is provided in Figure 4.9 (schematic courtesy of Mikhail Reyfman).



Figure 4.8 Fiber optic isolator.



**10 CHANNEL RECEIVER** 



Figure 4.9 Fiber optic interface.

## **4.7 Microcontroller Code Design**

The microcontroller code was designed to allow accurate, efficient feedback control, reliability and safety. The core allows for automated shutdown of the power supply in the event of voltage sensor failure, overvoltage condition, shorted output on startup, infinite loop conditions, and external fault inputs. Feedback control is accomplished by calculating the desired PWM period from the bank voltage measured with the ADC based on the equation found in Figure 5.14. The controller receives pulse start and external fault inputs over the fiber optic i/o module and pulse parameters are set by sending serial strings to the controller from a computer.

Complete microcontroller operating code is given in [N] with the leading number being the line of code. On startup, the processor in configured by lines 20-25 to use the fast RC internal oscillator, to run at the maximum execution speed of 30MIPS, and to enable the watchdog timer that will monitor operation during a pulse for safety. Variable values are initialized and stored into RAM by lines 100-196. The main function is located between lines 200-316.

Immediately on startup of the processor's code loop, lines 205-213 set all PWM outputs are overridden and turned off, and a pulse lockout timer bit is set to inhibit startup for a preset period, and feedback control is enabled. This is performed so that if a voltage transient caused by an external arc caused the microprocessor to reset but left the PWM peripheral on, the power supply would be prevented from receiving gate drive signals without the microcontroller realizing the pulse output was active. Line 225 calls the PWM lockout
subroutine, starting a 10ms countdown timer and inhibiting pulse activation for a set time. This was implemented early in testing when it was observed that after an arc causes the microcontroller to reset, residual transients and noise from ringing inductances occasionally triggered the input pin that calls the pulse start command, immediately triggering a second pulse.

The main code loop starts on line 252. In the main loop the processor checks bit flags controlling when collected date is sent to the connected computer over a serial port. If one of the timers that controls data output sets, the subroutine to transmit data is called on line 298 calling the subroutine on line 322 which transmits power supply status and ADC input values to a connected computer to allow the operator to monitor capacitor bank charging. Received commands from the operator are processed by the subroutines called between lines 303 and 312. Received serial characters are stored in RAM by the subroutine starting on line 358.

All power supply output pulse operations are handled by interrupts and synchronized by internal timers to ensure reproducible and accurate timing.

The interrupt service routine (ISR) on line 414 is triggered of an external fault is detected at any time. When triggered the subroutine to stop PWM output is called, the power supply is shut down, and an error message is sent to the user.

The ISR on line 450 is triggered of the fiber optic module receives a pulse start command. The system checks to see that pulse is not already running, the pulse start lockout timer has expired, and that the capacitor bank voltage is above a minimum threshold. If these conditions are met, the PWM start subroutine is called.

The ISR on line 472 controls ADC sampling rates and is triggered every time timer 1 expires. ADC sampling is automatically triggered when the timer expires, so the ISR only has to reset the timer.

The ISR on line 492 is used to terminate the power supply output pulse and set the PWM lockout timer. Timer 2 is started at the beginning of the pulse for the given pulse length, when it expires it triggers the ISR which calls the PWM stop subroutine and shuts down the pulse. The first time the timer calls the ISR, it is reset for 10ms and used as the PWM lockout timer, inhibiting another pulse from starting until it expires the second time.

The ISR on line 561 is triggered when timer 3 expires and sets a flag that is checked in the main loop to send the ADC readings back to the user over the serial port.

The PWM start subroutine starts on line 526. When called, it configures several variables used to acquire data during the pulse, sets timer 1 to a shorter period thereby increasing the ADC sampling rate, calculated the starting switching frequency based on capacitor bank voltage, configures the PWM generator for use, enables the watchdog timer that will reset the cpu if the control loop locks up, configures timer 2 to set the output pulse length and then enables the PWM output pins, starting the three phase gate drive signals.

The PWM stop subroutine starts on line 624. When called it resets timer 1 to a longer period thereby decreasing the ADC sampling rate, disables the PWM output pins, stopping the three phase gate drive signals, and turns off the watchdog timer.

The ISR on line 661 is triggered when the ADC conversion completes, meaning that the ADC, that was triggered when timer 1 expired, has completed digitizing the requested input channel and has it stored in its buffer. The ADC buffer values are stored in RAM, and voltages, and currents are computed by multiplying by the given scale factors. If the pulse is active, line 689 calls the PWM control subroutine that uses the ADC measurements to update the PWM period in order to obtain the correct boost ratio and stabilize output voltage. Lastly, after the control routine returns, the watchdog timer is cleared, preventing it from reaching zero and resetting the cpu if the control routing did not hang.

The PWM control subroutine that starts on line 712, uses the ADC measurements to update the PWM period in order to obtain the correct boost ratio and stabilize the output voltage. If feedback control is turned on, line 769 uses the linearized model for PWM period found in Figure 5.14 to calculate the desired period. The period is in terms of timer register clock counts. Safety checks are performed between lines 775 and 800 limiting the requested PWM period into acceptable bounds and monitoring voltages and sensor inputs for problems. Lines 804 to 811 set the PWM generator module to the newly calculated period and calculate the phase offset ties to maintain 120 degree separation between the phases.

Other code between lines 818 and 1410 is used to configure peripherals, the ADC, timers, interrupts, the PWM generator, and print out recorded data to the terminal. The subroutine starting on line 1247 is used to parse received serial strings for commands and present the operator with on screen menus on the terminal.

The code described herein provides reliable, accurate feedforward control to stabilize output voltage based on capacitor bank voltage droop.

#### **4.8 Summary**

This chapter presented the design of the resonant power supply's control system. An overview of the control system design and components was presented along with the specifications and capabilities of the dsPIC30F2020 microcontroller used in the control system. Support equipment such as analog isolators for the feedback control signals, the associated voltage dividers that measure voltage at the klystron tube, power supply output and capacitor bank, capacitor bank input current sensors, and fiber optic I/O isolators have been presented. A description of the microcontrollers operating code describes methods for SMPS control and methods for closing the control loop.

This chapter presents the results from testing the power supply. Section one presents a spice simulation model for the power supply and predicted numerical results. Section two presents open loop testing of the power supply. Section three presents results from testing the feedback control system to compensate for capacitor bank droop and stabilize output voltage. Section four presents models and testing of several filters to reduce harmonics. Section five presents simulation and testing of arc faults, operation of the spark gap and installation of the snubber circuit. Section six summarizes the chapter.

# **5.1 Spice Simulation Model**

A Spice simulation of the power supply has been created utilizing the simplified transformer model as shown in Figure 5.1. The secondary referred voltage is equal to the turns ratio of 1.36 times the maximum bank voltage of 900V. A doubling three phase rectifier feeds a simulated klystron load consisting of a 1.8kohm resistor without any output filtering.



Figure 5.1 Simplified spice model.

A time domain simulation of output voltage and the phase voltage at a rectifier terminal with respect to ground was generated, simulating operation of the three phase rectifier and transformer assembly. The simulated output voltage is lower in magnitude then the actual power supply output voltage measured at full bank voltage, however rise time, output waveform and ripple are almost identical with the exception that there is no capacitor bank droop on the simulation as seen in Figure 5.2.



Figure 5.2 Time domain simulation of output voltage.

Plots of output voltage and the voltage on a transformer phase equivalent to that in the spice simulation are plotted in Figure 5.3. Plots are displayed before and after digital filtering with a median filter as seen in Figure 5.4 to reduce high frequency noise. A median filter is a non-linear filter that returns the median point in a sliding window. Median filters are excellent for extracting a desired signal from higher frequency noise. The oscilloscope used to capture the waveform digitizes at 5ksamp/ms, and a 50point median filter was applied to clean up the signal to better visualize the phase voltage and harmonic ripple on the output. The 6th harmonic was found to dominate the power spectrum.



Figure 5.3 Output voltage and phase voltage before median filter.



Figure 5.4 Output voltage and phase voltage after 50 point median filter.

Measurements of voltage across the primary of a resonant transformer were acquired. Near resonant frequency, soft switching occurs on both the leading and lagging edges of an IGBT switching event as shown in Figure 5.5. As switching frequency increases above resonance, the voltage waveform begins to lead the current waveform causing a slight increase in switching current at the leading edge, but maintaining ZVS soft switching at the lagging edge due to the reverse diodes commutating the primary current as shown in Figure 5.6.



Figure 5.5 Transformer primary voltage and current at 18.5kHz.



Figure 5.6 Transformer primary voltage and current at 19kHz.

# **5.2 Open Loop Testing**

Initial testing of the power supply was carried out open loop to determine the proper linearized equation model for the feed forward segment of the control loop. Operation of the power supply was first verified by connecting the output voltage divider and gate drive signals to a mixed signal oscilloscope. In order to observe the relation between IGBT switching and voltage ramp up as seen in Figure 5.7.



Figure 5.7 Output voltage waveform and h-bridge gate drive signals.

The testing capacitor bank voltage was increased as shown in Figure 5.8. The linear nature of the relationship between output and bank voltage indicated that the transformer cores do not saturate near full power operation.



Figure 5.8 Output voltage vs bank voltage at 20kHz operation.

Testing of boost ratio at varying frequency was measured during open loop

Measurements of capacitor bank current, bank voltage, output voltage measured at the terminals of the power supply and load voltage measured at the terminals of the klystron tube were simultaneously acquired. As the pulse is generated, energy transfer from the capacitor bank causes its voltage to droop, leading to a decrease in output voltage. This effect is especially noticeable near resonance, where power transfer is maximized as seen in Figure 5.9. It should be noted that near resonance, a large amount of reactive power is stored in the resonator. After pulse termination this oscillation in the secondary coupled back to the primary and is rectified by the antiparallel diodes in the IGBTs, causing current flow back to the capacitor bank. As switching frequency increases, both output voltage and current draw from the capacitor bank decrease due to reduced power flow as seen in Figure 5.10, Figure 5.11, and Figure 5.12. The output voltage waveform becomes progressively flatter as the bank droop rate decreases.

Plots of bank voltage, current, and output and load voltage were generated by the matlab code found in [I].



Figure 5.9 Open loop pulse at 18.5kHz and 200V bank charge.



Figure 5.10 Open loop pulse at 20kHz and 200V bank charge.



Figure 5.11 Open loop pulse at 22kHz and 200V bank charge.



Figure 5.12 Open loop pulse at 24kHz and 200V bank charge.

Measurement of peak pulse voltage was obtained by similar methods and compared to capacitor bank voltage over the range of predicted operating frequencies to generate a plot of the power supplies effective boost ratio as a function of switching frequency. A linear regression line was fit to this data to provide the microcontroller with a method to determine proper switching frequency for a given commanded output voltage and bank voltage using feed forward techniques. Te ploted boost ratio data and regression line are presented in Figure 5.13. Open loop plots of boost ratio vs switching frequency were generated by the matlab code found in [J].



Figure 5.13 Boost ratio vs switching frequency.

#### **5.3 Feedback Controller Testing**

In order to close the control loop with feed forward techniques, the microcontroller measures the capacitor bank voltage and uses a linearized regression fit of boost ratio vs switching frequency to compute the required switching period. In practice, it is beneficial to fit a regression line to switching period vs required boost ratio as seen in Figure 5.14. This allows the removal of several divide operations from the control loop cycle; each divide operation required 16 instruction cycles to complete and is one of the more computationally intensive operations the microcontroller must complete. Removal of several divide operations was found to significantly enhance control loop execution speed, allowing an an increase from approximately 30 loops per ms to 120 loops per ms.



Figure 5.14 Microcontroller switching period vs required boost ratio.

Testing of the feed forward control system proved successful, allowing output voltage stabilization at -75kV output as shown in Figure 5.15. Note that the output voltage of the

power supply (light blue trace) is 10x the measurement and cursor readout. As capacitor bank voltage (bark blue trace) droops over the pulse, switching frequency in decreased toward resonance, thereby stabilizing output voltage. As expected, capacitor bank current (green trace) increases near to resonance compensation for the decreasing bank voltage to maintain constant power transfer to the load.



Figure 5.15 Feed forward control stabilized output voltage.

## **5.4 Filter Testing**

A spice model of a pi and harmonic filter were examined and compared to experimental results. The spice simulation is seen in Figure 5.16 including a 0.37mH series inductor and 40nF shunt capacitor, added to the output to form a pi filter with the doubler capacitor. A series LC harmonic filter consisting of a 0.005uF capacitor and 0.41mH inductor tuned to the 6th harmonic was connected across the rectifier terminals.



Figure 5.16 Spice model with pi and harmonic filters.

Time domain simulations seen in Figure 5.17 show an increase in rise time due to the increased capacitive loading of the output.



Figure 5.17 Spice time domain waveform with filters.

An FFT of the power supply output with no filters is presented in Figure 5.18 to provide a baseline for harmonic noise to compare to filtered outputs. Addition of a pi and harmonic filter greatly decreased 6th harmonic ripple as well as all other higher harmonics, as shown in Figure 5.19, however 3rd harmonic ripple was increased. Generation of 1st, 2nd, and 4th harmonics with unbalanced three phase excitation and no filter is demonstrated in Figure 5.20 by providing an approximately 10% mismatch in secondary phase voltages. Such a condition would result if the resonant frequencies of the secondaries are not equal due to variations in winding inductance.



Figure 5.18 Balanced three phase operation at 70kV.



Figure 5.19 Pi and 6th harmonic filter.



Figure 5.20 Unbalanced three phase operation.

Simulated results for the addition of filters are compared to experimental data. A baseline condition of an unfiltered output is seen in Figure 5.21. An LC harmonic filter consisting of a 0.005uF capacitor and adjustable inductor tuned to the 6th harmonic was connected across the rectifier terminals and harmonics were measured resulted in a decrease in 5th harmonic ripple as seen in Figure 5.22. With the addition of a pi filter by adding an 370uH series inductor, and 0.04uF shunt capacitor to the existing doubler capacitor eliminated 6th and higher harmonics but also increased 3rd harmonic as seen in Figure 5.23. This behavior is comparable to spice simulations.



Figure 5.21 Unfiltered operation.



Figure 5.22 Operation with 6th harmonic filter.



Figure 5.23 Operation with pi and 6th harmonic filters.

### **5.5 Output Arc Fault Simulation and Testing**

A spice model to simulate crowbar or klystron arcing is shown in Figure 5.24. The model closes the switch across the terminals that would be connected to the spark gap.



Figure 5.24 Spice model for spark gap simulation.

Time domain simulations of a spark gap firing event show almost instantaneous crowbarring of power supply output voltage as seen in Figure 5.25. In practice, stray inductance and the presence of a transmission line can generate a HV pulse of high amplitude traveling back on the coaxial cable in the event of a klystron arc as seen in Figure 5.26 (light blue trace). The amplitude of such a pulse exceeds the ratings of the doubler capacitors and can cause damage to the power supply.



Figure 5.25 Simulation of voltages during spark gap firing.



Figure 5.26 HV pulse caused by arc without snubber.

After the addition of an RL snubber circuit and associated spark gap allows safe operation of the system in the event of a power supply arc. A spark gap triggering event is shown in Figure 5.27. Upon firing of the spark gap, rapid crowbarring of the voltage across the klystron tube is observed, limiting energy that would be dissipate into the tube's cathode, potentially causing damage. An HV pulse is still reflected up the transmission line causing the voltage at the power supply terminals to swing from the previous negative value to a positive value of equal amplitude, however due to the presence of the snubber, the amplitude of the pulse is low enough to be safely tolerated by the system. Voltage on a transformer primary during a crowbar event is shown in Figure 5.28 demonstrating the rapid de-Qing of the secondary resonator observable as a reduction in primary current. Also visible is the cutoff of IGBT switching when the spark gap current sensor sends a fault condition pulse to the control system, cutting off the IGBT gate drive signals. A spark gap triggering event due

to an overvoltage condition is shown in Figure 5.29 and Figure 5.30, producing nearly identical effects.



Figure 5.27 Voltages during spark gap remote trigger



Figure 5.28 Phase current and voltages during spark gap remote trigger



Figure 5.29 Voltages during spark gap overvoltage trigger



Figure 5.30 Phase current and voltages during spark gap overvoltage trigger

#### **5.6 Summary**

This chapter presented the results from testing the power supply. Numerical spice simulation models for the power supply and simulated results were compared to measured data from power supply operation and found to be comparable. Open loop testing of the power supply was used to generate a linearized model of power supply voltage boost as a function of switching frequency. Section three presents results from testing the feedback control system to compensate for capacitor bank droop and stabilize output voltage. Section four presents models and testing of several filters to reduce harmonics. Section five presents simulation and testing of arc faults, operation of the spark gap and installation of the snubber circuit. Section six summarizes the chapter.

# *Chapter 6 Conclusions and Recommendations*

This thesis documents research on the design and construction of a three phase resonant power converter for driving klystron tubes. This chapter presents a summary of the research, provides conclusions and recommendations for the design of resonant power converters, and describes future research that will take place on this power supply.

#### **6.1 Summary of Research**

Chapter one presented a review of state of the art designs of high power SMPS design, resonant topologies, and soft switching. A review of three phase resonant power supplies constructed at LANL and E2V technologies

Chapter two presented the requirements and design constraints for construction of the power supply including available parts and constraints on integration into existing experiments. Requirements on the power supply include output voltage and current capabilities, fault tolerance, output voltage range, output stability, pulse duration, serviceability, safety, tolerance for voltage droop on the capacitor bank, and external control of parameters. Design constraints include the use of certain donated parts including transformer cores, IGBTs, rectifier diode stacks, and capacitor banks which were either donated to the project or were available as surplus.

Chapter three presented the design of the power supply's power electronic components, transformers, rectifier, filtering system and safety systems as well as comparison of experimental data to numerical simulations and the development of analytical models to provide the basis for future designs.

Chapter four presented the design and construction of the power supplies control system. This chapter covered the microcontroller, external electronics and the design of the operating code.

Chapter five presented results from power supply testing and comparison to numerical results from spice simulations. Models of the transformer, rectifiers, filters are presented and compared to simulation. Open loop testing of the power supply is presented and compared to spice simulations. Testing of the feedback control system and stabilization of output voltage during drooping capacitor bank in presented. Testing of a crowbar spark gap and associated LR snubber system is presented and compared to simulation.

#### **6.2 Conclusions**

Design and analysis has been performed on a three phase resonant power supply utilizing loosely coupled resonant transformers with a boost ratio that significantly exceeds the turns ratio with the capability of high voltage, high current output. It was determined that the use of nano-crystalline iron core allowed low loss, high frequency operation while providing high permeability. Use of such transformers allows extremely high power density when compared to equivalently rated 60Hz systems using soft iron cores.

A successful design of a feedback control system has been produced. The control system utilizes a low cost, high performance microcontroller with integrated SMPS control functionality to stabilize output voltage as the capacitor bank voltage decreases by adjusting switching frequency. It was determined that feedforward control from capacitor bank voltage is sufficient to stabilize output voltage, however the addition of feedback off of the output voltage would improve stability.

Several designs of noise and ripple filters were tested. It was found that use of a harmonic filter provide excellent reduction 6th harmonic noise, however effectiveness decreases as switching frequency moves away from resonance. It was determined that the addition of a pi filter on the output greatly reduced higher harmonic noise and ripple but produces an anomalous increase in third harmonic ripple. The addition of a pi filter does not greatly effect rapid rise time at the beginning of the pulse and only adds minimal stored energy.

The design of several safety systems for driving klystron tubes has been shown to prevent damage to the power supply in the event of an internal arc. A snubber circuit has been shown to reduce high voltage transients on the coaxial cable connecting the power supply to the load to sufficiently low amplitudes, preventing damaging the supply. The design of an optically or di/dt triggered spark gap allows rapid crowbarring of klystron voltage and provides an optical signal that cuts output power from the supply. Use of the spark gap has been shown to successfully de-Q the secondary resonators, interrupting power transfer and preventing damage to the power supply.

#### **6.3 Future Work**

Future work will focus on further analysis of soft switching, control system capabilities, and noise reduction.

Topics on soft switching will include measurements of the power supply's waveforms using instrumentation with greater numbers of channels to simultaneously record all three phases at once, analytical models of the resonant transformer including losses and nonidealities, and use of phase shifting techniques to allow soft switching off of resonance.

Topics on improving control system capabilities will include integration of feedback and feedforward control techniques to actively monitor output voltage, improvement in control loop functionality including techniques such as sampling analog inputs between switching events, implementation of digital filters for improved noise immunity, and improved resistance to electromagnetic noise during arcs and faults.

Topics on noise reduction will include design of low stored energy output filters, balancing secondary amplitude to reduce any 1st, 2nd, and 4th harmonic noise, potential frequency dithering of the IGBT switching to spread out harmonics, and use of actively tunable harmonic filters by using power electronic techniques to vary effective inductance.
- [1] W. A. Reass, D. M. Baca, and R. F. Gribble "DESIGN AND APPLICATION OF POLYPHASE RESONANT CONVERTER-MODULATORS" 4th CW and High Average Power Workshop LA-UR-06-3134
- [2] O.H. Stielau, G.A. Covic "Design of loosely coupled inductive power transfer systems" International Conference on Power System Technology, 2000. Proceedings. PowerCon 2000.
- [3] W.A. Reass, J.D. Doss, R.F. Gribble "A 1 MEGAWATT POLYPHASE BOOST CONVERTER-MODULATOR FOR KLYSTRON PULSE APPLICATION" Los Alamos National Laboratoy, PO. Box 1663, Los Alamos, NM87544, USA
- [4] W. A. Reass, D. M. Baca, and R. F. Gribble "DESIGN AND APPLICATION OF POLYPHASE RESONANT CONVERTER-MODULATORS" 4th CW and High Average Power Workshop LA-UR-06-3134
- [5] W. A. Reass, et.al. "DESIGN, STATUS, AND FIRST OPERATIONS OF THE SPALLATION NEUTRON SOURCE POLYPHASE RESONANT CONVERTER MODULATOR SYSTEM\*" Proceedings of the 2W3 Particle Accelerator Conference
- [6] W. A. Reass et.al "High-Frequency Multimegawatt Polyphase Resonant Power Conditioning" IEEE TRANSACTIONS ON PLASMA SCIENCE, VOL. 33, NO. 4, AUGUST 2005
- [7] W.A. Reass, J.D. Doss, M.G. Fresquez, D.A. Miera, J.S. Mirabal, P.J. Tallerico "A PROOF-OF-PRINCIPLE POWER CONVERTER FOR THE SPALLATION NEUTRON SOURCE RF SYSTEM" Proceedings of the 1999 Particle Accelerator Conference, New York, 1999
- [8] M. J. Bland, J. C. Clare, P. W. Wheeler, R. Richardson "A 25KV, 250KW MULTIPHASE RESONANT POWER CONVERTER FOR LONG PULSE APPLICATIONS" Pulsed Power Conference, 2007 16th IEEE International
- [9] M. J. Bland, J. C. Clare1, P. W. Wheeler, J. S. Pryzbyla "A HIGH POWER RF POWER SUPPLY FOR HIGH ENERGY PHYSICS APPLICATIONS" Proceedings of 2005 Particle Accelerator Conference, Knoxville, Tennessee
- [10] R.A. Cooper et.al. "DEVELOPMENT OF LOW INDUCTANCE HIGH POWER PLASTIC CASE CAPACITORS FOR THE SNS POLYPHASE RESONANT CONVERTER-MODULATOR" GENERAL ATOMICS ENERGY PRODUCTS Engineering Bulletin
- [11] H. A. Wheeler "SIMPLE INDUCTANCE FORMULAS FOR RADIO COILS" Proceedings of the Institute of Radio Engineers 1928
- [12] H. A. Wheeler "Formulas for the Skin Effect" Proceedings of the I.R.E. 1942

 $\overline{a}$ 

# *Appendix*

# A CM1200HB-66H IGBT

### **CM1200HB-66H**

2nd-Version HVIGBT (High Voltage Insulated Gate Bipolar Transistor) Modules

HIGH POWER SWITCHING USE **INSULATED TYPE** 

#### **MAXIMUM RATINGS (Tj = 25°C)**



#### ELECTRICAL CHARACTERISTICS (Tj = 25°C)



Note 1. Pulse width and repetition rate should be such that the device junction temp. (Tj) does not exceed Tjmax rating.<br>2. IE, VEC, tr, Qr & die/dt represent characteristics of the anti-parallel, emitter to collector fre

# B Hipotronics 8XX Series Power Supplies



#### **5kW High Power DC Supplies**

Note: Other Output Ratings Available, Consult Factory with Your Requirements

## C Matlab code for calculation voltage droop

```
clear all;
```

```
Vi=900;
Vout=80E3;
R=1800;
Iout=Vout/R;
N=[1:-0.1:0.6];
C=0.3;Tpulse=[0:0.1:10]/1E3;
Vfarr=[];
Tarr=[];
Legendarr=cell(length(N),1); %prealocate cell array for legend
for i=[1:length(N)]
%calculate final voltage
Neff=N(i);Vf=Vi.*sqrt(1-Vout.*Iout.*Tpulse./(Neff.*C.*Vi.^2/2)); 
Vfarr=[Vfarr;Vf];
Tarr=[Tarr;Tpulse];
%build cell array of legend strings
Legendarr\{i\}=[Eff=-1, num2str(Neff)];
```

```
%plot voltage droop vs pulse time
figure(1)
plot(Tarr'.*1000,Vfarr','LineWidth',2)
xlabel('Pulse Time (ms)')
ylabel('Final Voltage (V)')
grid on
legend(Legendarr)
title(['Initial Voltage= ', num2str(Vi),...
    'V, C= ' num2str(C), 'F'])
```
# D Low inductance relay CAD designs





EBW Relay Busbar<br>Insulator<br>Andrew Seltzman<br>seltzman@wisc.edu<br>Tol= +- 0.005



6061 Aluminum  $0.5"x0.75"$ 

EBW Relay Busbar Clamp<br>Negative Bus (bottom)<br>Andrew Seltzman<br>seltzman@wisc.edu<br>Tol= +- 0.005

 $E$ 

### **IGBT** busbar CAD designs





CT concepts IGBT driver.  $\boldsymbol{\mathrm{F}}$ 

# **Absolute Maximum Ratings**



Page 2

CT-Concept.com

### **Electrical Characteristics**



All data refer to +25°C and  $V_{DC}$  = 15V unless otherwise specified

### IGBT-Driver.com

### G Matlab code for resonant transformer plots

```
load('N156_R1800_F.txt'); %
load('N146_R1800_F.txt'); %
load('N136_R1800_F.txt'); %
load('N126_R1800_F.txt'); %
load('N116 R1800 F.txt'); %
load('N106_R1800_F.txt'); %
load('N096_R1800_F.txt'); %
load('N086_R1800_F.txt'); %
load('N076_R1800_F.txt'); %
load('N156 R820 F.txt'); %
load('N146 R820 F.txt'); %
load('N136_R820_F.txt'); %
load('N126_R820_F.txt'); %
load('N116_R820_F.txt'); %
load('N106 R820 F.txt'); %
load('N096_R820_F.txt'); %
load('N086_R820_F.txt'); %
load('N076_R820_F.txt'); %
load('N156_R.txt'); %
load('N146_R.txt'); %
load('N136 R.txt'); %
load('N126_R.txt'); %
load('N116_R.txt'); %
load('N106_R.txt'); %
load('N096_R.txt'); %
load('N086_R.txt'); %
load('N076_R.txt'); %
```
#### %turn number

N=[76,86,96,106,116,126,136,146,156]; Nrange=[76:156];

%resonant frequency at a given turn number

 $ResN=[N076_R1800_F(N076_R1800_F(:,4)=max(N076_R1800_F(:,4)),1),...$  $N086_R1800_F(N086_R1800_F(:,4)=max(N086_R1800_F(:,4)),1),\ldots$  $N096_R1800_F(N096_R1800_F(:,4)=max(N096_R1800_F(:,4)),1),\ldots$  $N106_R1800_F(N106_R1800_F(:,4)=max(N106_R1800_F(:,4)),1),\ldots$  $N116_R1800_F(N116_R1800_F(:,4)=max(N116_R1800_F(:,4)),1),...$ N126 R1800  $F(N126_R1800_F(:,4)=max(N126_R1800_F(:,4)),1),\ldots$ N136 R1800  $F(N136 R1800 F(:,4)=max(N136 R1800 F(:,4)),1),\ldots$  $N146_R1800_F(N146_R1800_F(:,4)=max(N146_R1800_F(:,4)),1),\ldots$ 

8

clear all;

N156\_R1800\_F(N156\_R1800\_F(:,4)==max(N156\_R1800\_F(:,4)),1)];

```
%maximum boost ratio at 1800 ohm load
MaxBoost1800=[
      max(N076_R1800_F(:,4)), \ldotsmax(N086_R1800_F(:, 4)), \ldotsmax(N096_R1800_F(:,4)), \ldotsmax(N106_R1800_F(:, 4)), \ldotsmax(N116_R1800_F(:,4)), \ldotsmax(N126_R1800_F(:,4)), \ldotsmax(N136_R1800_F(:,4)), \ldotsmax(N146_R1800_F(:,4)), \ldotsmax(N156 R1800 F(:,4))];
%Maximum boost ratio at 820 ohm load
MaxBoost820=[
      max(N076_R820_F(:,4)), \ldotsmax(N086_R820_F(:,4)), \ldotsmax(N096_R820_F(:, 4)), \ldotsmax(N106 R820 F(:,4)), \ldotsmax(N116_R820_F(:,4)), \ldotsmax(N126_R820_F(:,4)), \ldotsmax(N136_R820_F(:,4)), \ldotsmax(N146_R820_F(:,4)), \ldotsmax(N156_R820_F(:,4))];
%theoretical inductance of the secondary wining
mu0=4*pi*1e-7; %vacuum permiability
mur=50E3; %relative permiability of core
Nsec=136; %turns on secondary for this given plot
D22awg=0.644E-3; %diameter of 22AWG wire used on secondary in meters
Radsec=6.5.*0.0254/2; %Radius of secondary winding in meters (6.5" 
diameter)
A=pi*Radsec.^2; $area of secondary winding in m^2
Acore=(1.75*0.0254)*(2.5*0.0254); %area of iron core in m^2
length136=D22awg.*Nsec; %axial length of secondary winding
%inductance using long solonoid approximation
Lsec136th=(mu0.*(Nsec.^2).*A./length136).*(1/2) 
%inductance using short solonoid (wheeler 1942 eq50)
Lsec136th2=10.*pi.*mu0.*Nsec.^2.*Radsec.^2./...
     (9.*Radsec+10.*length136).*(1/2)
%compensated for flu excluded from iron core area
Lsec136th3=10.*mu0.*Nsec.^2.*(pi.*Radsec.^2-Acore)./...
     (9.*Radsec+10.*length136).*(1/2)
%transfer function model of transformer
Lsec136=1.36E-3; %1.36mH for N=135
Rsec=1.3; %secondary winding resistance 
             %(both cores in parallel, confirmed at 1.3ohm)
C=0.05E-6; %0.05uF parallel resonant capacitor
R=1800; %load resistance (measured and confirmed at 1800+-5ohm)
Nr=13.6; %turns ratio
```

```
10
```

```
%transfer function frequency sweep
freq=logspace(log10(1000),log10(33000),1000);
w=2*pi*freq;
Zs = j*w*Lsec136th3+Rsec+(R./(j*w*C))./(R+1./(j*w*C));%transfer function for transformer
Hw=Nr*abs(((R./(j*w*C))./(R+1./(j*w*C)))./Zs); 
%transfer function load resistance sweep
Rsw=logspace(log10(1),log10(60000),1000);
freqR=N136_R1800_F(N136_R1800_F(:,4)=max(N136_R1800_F(:,4)),1).*1000;w=2*pi*freqR;ZsR=j*w*Lsec136+Rsec+(Rsw./(j*w*C))./(Rsw+1./(j*w*C));
%transfer function for transformer
Hr = Nr * abs(( (Rsw. / (j * w * C)) . / (Rsw + 1. / (j * w * C))) . / ZsR);
%theoretical resonance vs turns
%Wheeler formula
%with compensation for magnetic flux excluded by shorted primary
%multiply by 1/2 since 2 coils in parallel
Larr=10.*mu0.*Nrange.^2.*(pi.*Radsec.^2-Acore)./...
     (9.*Radsec+10.*D22awg.*Nrange).*(1/2);
Fres=(1/(2*pi))*(sqrt(1./(Larr.*C)-1./((R.*C).^2)));
%measured inductance at a turns ratio
Lmeas=1./(((ResN.*(1000).*(2*pi)).^2+1./((R.*C).^2)).*C);
%models of inductance
%Wheeler formula
%multiply by 1/2 since 2 coils in parallel
LarrFullA=10.*mu0.*Nrange.^2.*(pi.*Radsec.^2)./...
     (9.*Radsec+10.*D22awg.*Nrange).*(1/2);
%simple long solonoid
%multiply by 1/2 since 2 coils in parallel
LarrLong=(mu0.*(Nrange.^2).*A./(D22awg.*Nrange)).*(1/2);
%simple long solonoid compensated area 
%multiply by 1/2 since 2 coils in parallel
LarrLongCompA=(\text{mu0.*(Nrange.^2)).*(A-Acore))./(D22awg.*Nrange)).*(1/2)i%theoretical max boost
w=2*pi*(Fres);%for 1800 ohm load
R=1800;
Zsmax1800=j.*w.*Larr+Rsec+(R./(j*w*C))./(R+1./(j*w*C));
 %transfer function for transformer
Hwmax1800=(Nrange./10).*abs(((R./(j*w*C))./(R+1./(j*w*C)))./Zsmax1800); 
%for 820 ohm load
R = 820;Zsmax820 = i.*w.*Larr+Rsec+(R./(i*wtC))./(R+1./(i*wtC));
%transfer function for transformer
Hwmax820=(Nrange./10).*abs(((R./(j*w*C))./(R+1./(j*w*C)))./Zsmax820);
```

```
%plot 
figure(1)
loglog(N156_R(:,1),N156_R(:,5),'-*',N136_R(:,1),N136_R(:,5),'-*',...N076 R(:,1), N076 R(:,5), '-*', Rsw, Hr, 'LineWidth', 2)
xlabel('Load Resistance (ohms)')
ylabel('Boost Ratio at Resonant Frequency')
grid on
legend('N=156 Measured','N=136 Measured',...
     'N=076 Measured','N=136 Transfer Fcn','Location','NorthWest')
%plot resonant frequency vs turns
figure(2)
plot(N,ResN,'-*',Nrange,Fres/1E3,'LineWidth',2)
xlabel('Secondary Turns')
ylabel('Resonant Frequency (kHz)')
grid on
legend('Measured Resonant F','Transfer Fcn Resonant F',...
     'Location','NorthEast')
%plot resonant frequency vs turns
figure(3)
plot(N, MaxBoost1800, '-'', Nrange, Hwmax1800, N, MaxBoost820, '-'', ... Nrange,Hwmax820,'LineWidth',2)
xlabel('Secondary Turns')
ylabel('Boost Ratio')
grid on
legend('R=1800 ohm Max Boost',...
       'R=1800 ohm Max Transfer Fcn',...
        'R=820 ohm Max Boost',...
        'R=820 ohm Max Transfer Fcn','Location','NorthWest')
%plot boost vs freq for n=136
figure(4)
plot(N136_R1800_F(:,1),N136_R1800_F(:,4),'-*',...
     freq/1000,Hw,'LineWidth',2)
xlabel('Frequency (kHz)')
ylabel('Boost Ratio')
grid on
legend('N=136 Measured','N=136 Transfer Fcn','Location','NorthWest')
%plot boost vs freq for n=all
figure(5)
plot(N156_R1800_F(:,1),N156_R1800_F(:,4),...N146 R1800 F(:,1), N146 R1800 F(:,4),...
     N136 R1800 F(:,1),N136 R1800 F(:,4),...
     N126_R1800_F(:,1), N126_R1800_F(:,4), ...
     N116_R1800_F(:,1), N116_R1800_F(:,4), ...
     N106 R1800 F(:,1), N106 R1800 F(:,4),...
     N096_R1800_F(:,1), N096_R1800_F(:,4), ...
     N086_R1800_F(:,1), N086_R1800_F(:,4), ...
      N076_R1800_F(:,1),N076_R1800_F(:,4),'LineWidth',2)
xlabel('Frequency (kHz)')
ylabel('Boost Ratio')
```

```
grid on
legend('N=156 R=1800ohm','N=146 R=1800ohm','N=136 R=1800ohm',...
     'N=126 R=1800ohm','N=116 R=1800ohm','N=106 R=1800ohm',...
     'N=096 R=1800ohm','N=086 R=1800ohm','N=076 R=1800ohm',...
     'Location','NorthWest')
%plot boost vs freq for n=all
figure(6)
plot(N156_R820_F(:,1),N156_R820_F(:,4),...N146_R820_F(:,1), N146_R820_F(:,4), ...
     N136_R820_F(:,1), N136_R820_F(:,4), ...
     N126_R820_F(:,1), N126_R820_F(:,4), ...
     N116_R820_F(:,1), N116_R820_F(:,4), ...
     N106_R820_F(:,1), N106_R820_F(:,4), ...
     N096_R820_F(:,1), N096_R820_F(:,4), ...
     N086_R820_F(:,1), N086_R820_F(:,4), ...
      N076_R820_F(:,1),N076_R820_F(:,4),'LineWidth',2)
xlabel('Frequency (kHz)')
ylabel('Boost Ratio')
grid on
legend('N=156 R=820ohm','N=146 R=820ohm','N=136 R=820ohm',...
     'N=126 R=820ohm','N=116 R=820ohm','N=106 R=820ohm',...
     'N=096 R=820ohm','N=086 R=820ohm','N=076 R=820ohm',...
     'Location','NorthWest')
%plot inductance vs turns
figure(7)
plot(N,Lmeas,'-*',Nrange,Larr,Nrange,LarrFullA,...
     Nrange,LarrLong,Nrange,LarrLongCompA,'LineWidth',2)
xlabel('Secondary Turns')
ylabel('Inductance (H)')
grid on
legend('Measured','Wheeler Compensated Area','Wheeler Full Area',...
     'Long Solenoid','Long Solenoid Compensated 
Area','Location','NorthWest')
```
### H Matlab code for plotting boost ratio at varying frequency

clear all; %load open loop ps output at 200v on the bank load('open\_loop\_200bank.txt'); fmod=open\_loop\_200bank(:,1); %frequency in khz vboost=open\_loop\_200bank(:,2)\*1000/200; %kv out / 200v on the bank ptper=235.\*(40000./(fmod.\*10));

%load open loop ps output at varying bank voltage

```
load('open_loop_vsweep_20khz.txt'); 
vbank=open_loop_vsweep_20khz(:,1);
vout=open_loop_vsweep_20khz(:,2);
Vin=[min(vbank):max(vbank)]; %
Vfit=0.1132*Vin; %regression fit for vout vs vin
Freq=[min(fmod):max(fmod)]; %BFfit=-12*Freq+343; %regression line for boost to frequency plot
Boost=[min(vboost):max(vboost)];
PBfit=172*Boost+29706; %regression line for PTPER to boost plot
%plot boost vs modulation frequency
figure(1)
plot(fmod,vboost,'.',Freq,BFfit,'LineWidth',2)
xlabel('Modulation Frequency (kHz)')
ylabel('Boost Ratio')
grid on
legend('Experimental Data','Fit Boost= -12*F(kHz)+343')
%plot ptper vs boost
figure(2)
plot(vboost,ptper,'.',Boost,PBfit,'LineWidth',2)
xlabel('Boost Ratio')
ylabel('PTPER')
grid on
legend('Experimental Data','Fit PTPER= 172*Boost+29706',...
     'Location','NorthWest')
%plot vout vs vbank
figure(3)
plot(vbank,vout,'*',Vin,Vfit,'LineWidth',2)
xlabel('Bank Voltage (V)')
ylabel('Output Voltage (kV)')
grid on
legend('Experimental Data','Fit Vout= 0.1132*Vbank',...
     'Location','NorthWest')
```
### I Matlab code for date with differential voltage on

transformer secondary.

clear all; %close all;

```
fignum=0;
```

```
shots=[4];
channels=[1, 2, 3, 4];
```
for shot=shots for channel=channels

```
TOP=load(['ts',num2str(shot),'ch',num2str(channel),'.isf']); %
BOT=load(['bs',num2str(shot),'ch',num2str(channel),'.isf']); %
assignin('base',['t'],TOP(:,1));
assignin('base',['tch',num2str(channel)],medfilt1(TOP(:,2),50));
assignin('base',['bch',num2str(channel)],medfilt1(BOT(:,2),50));
```
#### end

```
%plot 
fignum=fignum+1;
figure(fignum)
plot(t,tch1*3,t,tch2*100,t,tch3,t,tch4*500,'LineWidth',1)
xlabel('Time (s)')
ylabel('')
grid on
legend('I ph3 pri(x1kA)','V ph3 pri(x10V)',...
        'V ph3 sec1(R)(x1kV)','V ph3 sec2(Y)(x1kV)','Location','SouthEast')
fignum=fignum+1;
figure(fignum)
plot(t,bch1,t,bch2*10,t,bch3*2,t,-bch4*20,'LineWidth',1)
xlabel('Time (s)')
ylabel('')
grid on
legend('-I bank(x100A)','V supply(x1kV)',...
        'V load(x1kV)','-V bank(x10V)','Location','SouthEast')
fignum=fignum+1;
figure(fignum)
plot(t,tch3-tch4*500,'LineWidth',1)
xlabel('Time (s)')
ylabel('')
grid on
legend('V secondary differential','Location','SouthEast')
fignum=fignum+1;
figure(fignum)
plot(t,tch3+tch4*500,t,bch2*10,'LineWidth',1)
xlabel('Time (s)')
ylabel('')
grid on
legend('V sec wrt gnd(x1kV)','V out(x1kV)','Location','SouthEast')
```
### J Matlab code for date with differential voltage on

transformer primary.

```
clear all;
close all;
fignum=0;
shots=[11];
for shot=shots
for channel=[1,2,3]
TOP=load(['ts',num2str(shot),'ch',num2str(channel),'.isf']); %
assignin('base',['t'],TOP(:,1));
assignin('base',['tch',num2str(channel)],medfilt1(TOP(:,2),50));
end
for channel=[1,2,3,4]
BOT=load(['bs',num2str(shot),'ch',num2str(channel),'.isf']); %
assignin('base',['bch',num2str(channel)],medfilt1(BOT(:,2),50));
end
%plot 
fignum=fignum+1;
figure(fignum)
plot(t,tch1*3,t,tch2*100,t,tch3*100,'LineWidth',1)
xlabel('Time (s)')
ylabel('')
grid on
legend('I ph3 pri(x1kA)','V ph3 pri1(x10V)',...
        'V ph3 pri2(x10V)','Location','SouthEast')
fignum=fignum+1;
figure(fignum)
plot(t,bch1,t,bch2*10,t,bch3*2,t,-bch4*20,'LineWidth',1)
xlabel('Time (s)')
ylabel('')
grid on
```

```
16
```

```
legend('-I bank(x100A)'.'V supply(x1kV)'.... 'V load(x1kV)','-V bank(x10V)','Location','North')
fignum=fignum+1;
figure(fignum)
plot(t,-tch2*100+tch3*100,t,tch1*3,'LineWidth',1)
xlabel('Time (s)')
ylabel('')
grid on
legend('V ph3 pri diff(x10V)','I ph3 pri(x1kA)','Location','SouthEast')
fignum=fignum+1;
figure(fignum)
plot(t,10*(-tch2*100+tch3*100).*(tch1*3),...
      t,fastrms(10*((-tch2*100+tch3*100).*(tch1*3)),10000/(2*20)),...
      t,(bch1.*(-bch4*20)),t,(bch2*1E4).^2./(1800*1E3),'LineWidth',1)
xlabel('Time (s)')
ylabel('power')
grid on
legend('P ph3 (x1kW)','P ph3 rms(x1kW)',...
     'P in avg(x1kW)','P out (x1kW)','Location','SouthEast')
```
end

# K Pearson transformer datasheet.

# **PEARSON™ CURRENT MONITOR** MODEL 301X



@ 1999 Pearson Electronics, Inc. 301X.SPX 990506



#### AD215 datasheet  $\mathbf{L}$

### AD215-SPECIFICATIONS (Typical @ +25°C, V<sub>5</sub> = ±15 V dc, 2 kΩ output load, unless otherwise noted.)







#### Microcontroller datasheet M



# dsPIC30F1010/202X

## 28/44-Pin dsPIC30F1010/202X Enhanced Flash **SMPS 16-Bit Digital Signal Controller**

Note: This data sheet summarizes features of this group of dsPIC30F devices and is not intended to be a complete reference source. For more information on the CPU, peripherals, register descriptions and general device<br>functionality, refer to the "dsPIC30F Family Reference Manual" (DS70046). For more information on the device instruction set and programming, refer to the "dsPIC30F/ 33F Programmer's Reference Manual" (DS70157).

#### High-Performance Modified RISC CPU:

- Modified Harvard architecture
- C compiler optimized instruction set architecture
- 83 base instructions with flexible addressing modes
- 24-bit wide instructions, 16-bit wide data path
- 12 Kbytes on-chip Flash program space
- 512 bytes on-chip data RAM
- 16 x 16-bit working register array
- Up to 30 MIPS operation:
	- Dual Internal RC
		- 9.7 and 14.55 MHz (±1%) Industrial Temp
		- $-6.4$  and  $9.7$  MHz ( $\pm$ 1%) Extended Temp
	- 32X PLL with 480 MHz VCO
	- PLL inputs ±3%
	- External EC clock 6.0 to 14.55 MHz
	- HS Crystal mode 6.0 to 14.55 MHz
- 32 interrupt sources
- Three external interrupt sources
- 8 user-selectable priority levels for each interrupt
- 4 processor exceptions and software traps

#### **DSP Engine Features:**

- Modulo and Bit-Reversed modes
- Two 40-bit wide accumulators with optional saturation logic
- 17-bit x 17-bit single-cycle hardware fractional/ integer multiplier
- · Single-cycle Multiply-Accumulate (MAC) operation
- 40-stage Barrel Shifter
- · Dual data fetch

#### **Peripheral Features:**

- · High-current sink/source I/O pins: 25 mA/25 mA
- Three 16-bit timers/counters; optionally pair up 16-bit timers into 32-bit timer modules
- One 16-bit Capture input functions
- Two 16-bit Compare/PWM output functions
- Dual Compare mode available
- 3-wire SPI modules (supports 4 Frame modes)
- . I<sup>2</sup>C™ module supports Multi-Master/Slave mode and 7-bit/10-bit addressing
- UART Module:
	- Supports RS-232, RS-485 and LIN 1.2
	- Supports IrDA® with on-chip hardware endec
	- Auto wake-up on Start bit
	- Auto-Baud Detect
	- 4-level FIFO buffer

#### **Power Supply PWM Module Features:**

- Four PWM generators with 8 outputs
- Each PWM generator has independent time base and duty cycle
- Duty cycle resolution of 1.1 ns at 30 MIPS
- Individual dead time for each PWM generator:
	- Dead-time resolution 4.2 ns at 30 MIPS
	- Dead time for rising and falling edges
- Phase-shift resolution of 4.2 ns @ 30 MIPS
- Frequency resolution of 8.4 ns @ 30 MIPS
- PWM modes supported:
- Complementary
- Push-Pull
- Multi-Phase
- Variable Phase
- Current Reset
- Current-Limit
- Independent Current-Limit and Fault Inputs
- Output Override Control
- Special Event Trigger
- PWM generated ADC Trigger

#### **Analog Features:**

#### **ADC**

- 10-bit resolution
- · 2000 Ksps conversion rate
- Up to 12 input channels
- "Conversion pairing" allows simultaneous conversion of two inputs (i.e., current and voltage) with a single trigger
- · PWM control loop:
	- Up to six conversion pairs available
	- Each conversion pair has up to four PWM and seven other selectable trigger sources
- Interrupt hardware supports up to 1M interrupts per second

#### **COMPARATOR**

- Four Analog Comparators:
	- 20 ns response time
	- 10-bit DAC reference generator
	- Programmable output polarity
	- Selectable input source
	- ADC sample and convert capable
- PWM module interface
	- PWM Duty Cycle Control
	- PWM Period Control
- PWM Fault Detect
- Special Event Trigger
- PWM-generated ADC Trigger

#### **Pin Diagrams**

#### **Special Microcontroller Features:**

- Enhanced Flash program memory:
- 10,000 erase/write cycle (min.) for industrial temperature range, 100k (typical)
- · Self-reprogrammable under software control
- Power-on Reset (POR), Power-up Timer (PWRT) and Oscillator Start-up Timer (OST)
- Flexible Watchdog Timer (WDT) with on-chip low power RC oscillator for reliable operation
- Fail-Safe clock monitor operation
- Detects clock failure and switches to on-chip low power RC oscillator
- Programmable code protection
- . In-Circuit Serial Programming™ (ICSP™)
- · Selectable Power Management modes
	- Sleep, Idle and Altemate Clock modes

#### **CMOS Technology:**

- Low-power, high-speed Flash technology
- 3.3V and 5.0V operation (±10%)
- Industrial and Extended temperature ranges
- Low power consumption





#### **FIGURE 1-2:** dsPIC30F2020 BLOCK DIAGRAM

<b>Pin Name</b>	Pin Type	<b>Buffer</b> <b>Type</b>	<b>Description</b>
ANO-AN7		Analog	Analog input channels.
<b>AV<sub>DD</sub></b>	P	P	Positive supply for analog module.
<b>AVss</b>	P	P	Ground reference for analog module.
<b>CLKI</b> <b>CLKO</b>	т O	<b>ST/CMOS</b>	External clock source input. Always associated with OSC1 pin function. Oscillator crystal output. Connects to crystal or resonator in Crystal Oscillator mode. Optionally functions as CLKO in RC and EC modes. Always associated with OSC2 pin function.
<b>EMUD</b> <b>EMUC</b> EMUD1 EMUC1 EMUD <sub>2</sub> EMUC <sub>2</sub>	<b>I/O</b> <b>I/O</b> <b>I/O</b> <b>I/O</b> <b>I/O</b> <b>I/O</b>	ST ST ST ST ST ST	ICD Primary Communication Channel data input/output pin. ICD Primary Communication Channel clock input/output pin. ICD Secondary Communication Channel data input/output pin. ICD Secondary Communication Channel clock input/output pin. ICD Tertiary Communication Channel data input/output pin. ICD Tertiary Communication Channel clock input/output pin.
IC <sub>1</sub>	ı	ST	Capture input.
<b>INTO</b> INT <sub>1</sub> INT <sub>2</sub>	ı т I	ST SТ ST	External interrupt 0 <b>External interrupt 1</b> External interrupt 2
SFLT1 SFLT2 SFLT3 PWM1L PWM <sub>1H</sub> PWM2L PWM2H PWM3L PWM3H PWM4L PWM4H	Ī ı ı o O O O O O O O	ST ST ST — — $\overline{\phantom{0}}$	<b>Shared Fault Pin 1</b> Shared Fault Pin 2 Shared Fault Pin 3 PWM 1 Low output PWM 1 High output PWM 2 Low output PWM 2 High output PWM 3 Low output PWM 3 High output PWM 4 Low output PWM 4 High output
<b>MCLR</b>	I/P	ST	Master Clear (Reset) input or programming voltage input. This pin is an active low Reset to the device.
OC1-OC2 OCFLTA	O т		Compare outputs. Output Compare Fault pin
OSC <sub>1</sub> OSC <sub>2</sub>	т <b>I/O</b>	<b>CMOS</b>	Oscillator crystal input. Oscillator crystal output. Connects to crystal or resonator in Crystal Oscillator mode. Optionally functions as CLKO in FRC and EC modes.
<b>PGD</b> PGC PGD <sub>1</sub> PGC1 PGD <sub>2</sub> PGC <sub>2</sub>	<b>I/O</b> т <b>I/O</b> т <b>I/O</b> т	ST ST ST ST ST ST	In-Circuit Serial Programming™ data input/output pin. In-Circuit Serial Programming clock input pin. In-Circuit Serial Programming data input/output pin 1. In-Circuit Serial Programming clock input pin 1. In-Circuit Serial Programming data input/output pin 2. In-Circuit Serial Programming clock input pin 2.
Legend: CMOS ST ı	$\equiv$ Ξ $\equiv$	Input	CMOS compatible input or output Analog input Analog $\equiv$ Schmitt Trigger input with CMOS levels Output O $\equiv$ P Power $\equiv$

TABLE 1-2: PINOUT I/O DESCRIPTIONS FOR dsPIC30F2020

<b>Pin Name</b>	Pin Type	<b>Buffer</b> <b>Type</b>	<b>Description</b>
<b>RB0-RB7</b>	IЮ	ST	PORTB is a bidirectional I/O port.
RA9	<b>I/O</b>	<b>ST</b>	PORTA is a bidirectional I/O port.
RD <sub>0</sub>	IЮ	ST	PORTD is a bidirectional I/O port.
RE0-RE7	IЮ	ST	PORTE is a bidirectional I/O port.
<b>RF6, RF7, RF8</b>	<b>I/O</b>	ST	PORTF is a bidirectional I/O port.
SCK <sub>1</sub>	<b>I/O</b>	ST	Synchronous serial clock input/output for SPI #1.
SDI <sub>1</sub>	т	ST	SPI#1 Data In.
SDO <sub>1</sub>	O	$\overline{\phantom{0}}$	SPI #1 Data Out.
<b>SCL</b>	<b>I/O</b>	ST	Synchronous serial clock input/output for l <sup>2</sup> C™.
<b>SDA</b>	IЮ	ST	Synchronous serial data input/output for I <sup>2</sup> C.
T <sub>1</sub> CK	т	ST	Timer1 external clock input.
T <sub>2</sub> CK	п	sт	Timer2 external clock input.
U1RX	т	ST	<b>UART1</b> Receive.
U <sub>1</sub> TX	O		<b>UART1 Transmit</b>
U1ARX	п	<b>ST</b>	Alternate UART1 Receive
U1ATX	O	$\Omega$	Altemate UART1 Transmit
CMP <sub>1</sub> A	п	Analog	Comparator 1 Channel A
CMP <sub>1B</sub>	п	Analog	Comparator 1 Channel B
CMP <sub>1C</sub>	ı	Analog	Comparator 1 Channel C
CMP <sub>1D</sub>	ı	Analog	Comparator 1 Channel D
CMP <sub>2</sub> A	ı	Analog	Comparator 2 Channel A
CMP <sub>2B</sub>	п	Analog	Comparator 2 Channel B
CMP <sub>2C</sub>	п	Analog	Comparator 2 Channel C
CMP <sub>2D</sub>	п	Analog	Comparator 2 Channel D
CMP <sub>3</sub> A	ı	Analog	Comparator 3 Channel A
CMP3B	п	Analog	Comparator 3 Channel B
CMP3C	ı	Analog	Comparator 3 Channel C
CMP3D	ı	Analog	Comparator 3 Channel D
CMP4A	п	Analog	Comparator 4 Channel A
CMP4B	ı	Analog	Comparator 4 Channel B
CN0-CN7	п	ST	Input Change notification inputs
			Can be software programmed for internal weak pull-ups on all inputs.
V <sub>DD</sub>	P	—	Positive supply for logic and I/O pins.
Vss	P		Ground reference for logic and I/O pins.
<b>EXTREF</b>	т	Analog	External reference to Comparator DAC
<b>CMOS</b> Legend:	$\equiv$		CMOS compatible input or output Analog Analog input $\equiv$
ST	$\equiv$		Schmitt Trigger input with CMOS levels Output o $\equiv$
	Ξ	Input	P Power $\equiv$

**TABLE 1-2:** PINOUT I/O DESCRIPTIONS FOR dsPIC30F2020 (CONTINUED)

Microcontroller operating code  $\mathbf N$ 

```
\frac{1}{3}//*
4//* Code to run dsPIC30F2020 with fiber optic serial modem to send ADC data
5 //* Requires C30 compiler
6^{1/2}8<br>9 #include <p30f2020.h>
```
10//#include <stdio.h> 11 //#include <math.h> 12 13 15 //\* Configuration Bits 17 //Fey=(SOURCE OSCILLATOR FREQUENCY \* PLL MULTIPLIER)/(PROGRAMMABLE POSTSCALER \* 4) 18  $19$ 20\_FOSCSEL(FRC\_PLL) //Select Fast RC oscillator with PLL  $\,$ 21 FOSC(CSW\_FSCM\_OFF & FRC\_HI\_RANGE & OSC2\_IO & HS\_EC\_DIS); //if HI Fcy=30 MHz and Tcy=33.3 ns 22 //\_FPOR(PWRT\_128) 23 24\_FWDT(FWDTEN\_OFF & WDTPRE\_PR32 & WDTPOST\_PS1); //Turn OFF Hardware WDT enable and set config bits 25 FGS(CODE\_PROT\_OFF & GWRP\_OFF);  $\sqrt{C}$  Code Protect OFF 26 27 29 // Function prototypes  $30$  //\*\*\*\*\*\*\*\* 31 32 #define testbit(data.bitno) ((data>>bitno)&0x0001) 33 #define setbit(data,bitno) data=(data&(0x0001<<br/>sbitno))  $34$ 35 //Median filter definitions 36 #define PIX SORT(a,b) { if ((a)>(b)) PIX SWAP((a),(b)); } 37 #define PIX\_SWAP(a,b) { int temp=(a);(a)=(b);(b)=temp; } 38 39 void initCORE(void);  $\frac{1}{\pi}$  in core registers 40 void timersetup(void); //setup timers 41 void adcsetup(void);  $\sqrt{s}$ etup ADC 42 void uartsetup(void); //setup uart for serial output 43 void iosetup(void); //setup io 44 void pwmsetup(void); //setup PWM generator 45 void INTsetup(void); //setup interupts //print output data to terminal 46 void TxData(void); 47 void PWMstart(void); //enable PWM pins and start pulse timer 48 void PWMstop(void); //disable PWM pins and stop pulse timer 49 void PWMlockout(void); //PWM lockout timer, prevents EMI during shutdown from triggering second pulse 50 void PWMcontrol(void); //PWM control loop, updates frequency or duty cycle 51 void PSprintdata(void); //Pring PWM pulse data to console<br>51 void PSprintdata(void); //Pring PWM pulse data to console<br>52 void clrRXdata(void); //clear RX data buffer 53 54 void \_attribute\_((interrupt, auto\_psv)) \_T1Interrupt(void); 55 void \_attribute\_((interrupt, auto\_psv)) \_T2Interrupt(void); 56 void \_attribute\_((interrupt, auto\_psv)) \_T3Interrupt(void); 57 void \_attribute\_((interrupt, auto\_psv)) \_ADCInterrupt(void); 58 void \_\_attribute\_((interrupt, auto\_psv)) \_U1RXInterrupt(void); 59 60 void \_attribute\_((interrupt, auto\_psv)) \_INT0Interrupt(void); //interupt for error detection from i/o extender 61 void \_attribute\_((interrupt, auto\_psv)) \_INT1Interrupt(void); //interupt for push button 62 void \_attribute\_((interrupt, auto\_psv)) \_INT2Interrupt(void); //interupt for optical trigger in 63 64 void printSerial\_int(unsigned int); // print unsigned int 65 void printSerial\_binary\_int(unsigned int); // print unsigned int as binary string<br>66 void printSerial\_binary\_int(unsigned int); // print unsigned int as binary string<br>66 void printSerial\_signed\_int(signed int val); // p 67 void printSerial\_str(char \*); // print char string from ram 68 void printSerialROM\_str(const char \* str); // print char string from rom 69 void printSerial\_ASCII(char value); // print single char value  $\frac{1}{\sqrt{2}}$  parse string for data 70 void parse string(char  $*$ ); 71 int str\_to\_int(char \*);  $\frac{1}{\sqrt{2}}$  convert ascii numeric string to an int 72 int opt\_med3(int \* p); // execute median filter on given 3 element array  $73$ 75 // Variables / const (const puts value in program memory instead of ram) 77 const char ResetString[]={"RESET\r\n\0"}; // 78 const char InvalidString[]={"\r\nInvalid Command, type \"help\" for commands\r\n\0"}; // 79 const char InvalidNumberString[]={"\r\nNumber out of bounds\0"}; 80 const char ResetInitString[]={"\r\nInitiating dsPIC reset\r\n\0"}; 81 const char ADCString[]={" ADCcnt=\0"};  $\frac{1}{2}$  $^{\prime\prime}$ 82 //const char TimeString[]={" SYSt=\0"}; 83 //const char SpaceString[]={"\0"};  $\frac{1}{2}$ 84 //const char RxUARTString[]={"RxUART=\0"};  $/\!/$ 

```
85 const char SbufString\left[\right]=\left\{ \right. "Sbuf=\left\{0\right\}"}; //
 86 const char PulseString[] = \{\text{``\r\n} \in \text{Fly} \in \text{Fly} \in \text{Fly} \in \text{Fly} \};
  87 
 88 const char freqString[]={"\r\nPWM Frequency(00200=>20kHz)= \0"};
 89 const char dtyString[]={"\r\nPWM Duty Cycle(00100=>100%)= \0"};
  90 const char ptimeString[]={"\r\nPWM pulse time(00100=>10ms)= \0"}; 
  91 const char vsetString[]={"\r\nVout set point(08000=>80kV)= \0"}; 
 92 const char vlimitString[]={"\r\nVlimit set point(08000=>80kV)=\0"};
 93 const char kpString[]={"\r\nKp= \0"};
  94 const char kiString[]={"\r\nKi= \0"}; 
  95 const char Ch0123String[]={"ADC[0123]= \0"}; // String lables for ADC ch 0,1,2,3 
 96<br>97 const char CLS[]=\{0x1b, 0x5b, 0x32, 0x4a\};a}; // clear terminal screen sequence for VT100 emulation < ESC [2 J >// carage return and line feed
 98 const char NL[]={"\r\n\0"};<br>99 const char HOME[]={"\r\0"};
                                                                \# carage return without line feed
 100 
 101 // raw value from ADC 
102 int ADC_Ch0=0; // literal ADC value<br>103 int ADC_Ch1=0; // literal ADC value
103 int ADC-Ch1=0; // literal ADC value<br>104 int ADC-Ch2=0; // literal ADC value
                                                    1/1 literal ADC value 1/1 literal ADC value
105 int ADC_CCh3=0;
106<br>107 char received;
                                                1/107 UART Rx data element<br>1/104 UART Rx data string
108 char RxDataString[80];<br>109 int RxDataPoint = 0;
                                                    1/10 UART Rx data string pointer
 110 
 111 struct{ 
112 unsigned TxDataReady :1; //transmit data<br>113 unsigned RxDataReady :1; //process received data
         unsigned RxDataReady :1;
114 unsigned PSDataReady :1; //transmit PWM data<br>115 }ProgCON; // [15..0] program control f
                                                 // [15..0] program control flags 116 
 117 //counter variables 
118 unsigned int MAINcount=0; \frac{1}{2} // main program loop counter 119 unsigned int ADC_INTcount = 0; \frac{1}{2} // ADC conversion complet
                                                             1/14 ADC conversion complete interupt counter 1/11 timer 1 interupt counter
120 unsigned int TMR1_INTcount = 0; // timer1 interupt counter<br>121 unsigned int TMR2_INTcount = 0; // timer2 interupt counter
121 unsigned int TMR2_INTcount = 0; \frac{1}{2} interupt counter 122 unsigned int TMR3_INTcount = 0; \frac{1}{2} // timer3 interupt counter
122 unsigned int TMR3_INTcount = 0; // timer3 interupt counter 123 unsigned int U1RX_INTcount = 0; // UART Rx interupt counter
123 unsigned int UIRX INTcount = 0;
 124 
125 //data variables for power supply operation<br>126 int IIN DATA MAX = 0; // max current from bank
126 int IIN_DATA_MAX = 0; \frac{127}{10} max current from bank 127 int IIN_DATA_MIN = 0; \frac{127}{10} min current from bank
127 int IIN_DATA_MIN = 0;<br>128 int VIN_DATA_MAX = 0;
128 int VIN_DATA_MAX = 0; \# max voltage on bank at start of pulse 129 int VIN DATA MIN = 0; \# min voltage on bank at end of pulse
                                                           1/2 min voltage on bank at end of pulse 1/2 max current to load
130 int IOUT_DATA_MAX = 0;131 int VOUT_DATA_MAX = 0; \frac{1}{2} // max voltage to load 132 int TVSP_DATA = 0; \frac{1}{2} // time to reach data setpoin
132 int TVSP_DATA = 0; \frac{133}{133} int TVMAX DATA = 0: \frac{133}{136} // time to reach max voltage
                                                           1/ time to reach max voltage
 134 
 135 //control variables for power supply operation
136 struct\frac{137}{137} //uns
         //unsigned interlock :1; //must be set to 1 to enable triggering (not yet implimented)
138 unsigned dummypulse :1; //set is dummy pulse is running(no PWM output)<br>139 unsigned ConFreq :1: //set if output regulation via freq control
          unsigned ConFreq :1; //set if output regulation via freq control
140 unsigned PWMlockout :1; //set if PWM lockout is enabled 141 unsigned PSerror :1: //error in power supply
141 unsigned PSerror :1; //error in power supply<br>142 unsigned above Vlimit:1: //power supply over
142 unsigned aboveVlimit:1; //power supply over voltage unsigned extINTerror:1; //external interupt error
         unsigned extINTerror:1;
144 unsigned lowVin:1; //Vin reading too low (no charge or disconnected input)<br>145 unsigned lowVout:1: //Vout not reading above set threshold within set time
         unsigned lowVout:1; //Vout not reading above set threshold within set time \text{PSCONFIG}; //[15.0] power supply operation control flags
146 }PSCONFIG; // [15..0] power supply operation control flags 147 
148 //variables for PWM control<br>149 int PWMfreq = 220;
149 int PWMfreq = 220; //PWMfreq=200 for 20kHz (used for user input for const freq operation)<br>150 int PWMper=47000; //PWMper=47000 for 20khz (used in control loop for increaced speed)
                                               1/PWMper=47000 for 20khz (used in control loop for increaced speed)
151 int Dty = 100; /PWM duty cycle 100 => 100%
 152 
153 //setpoints and limits<br>154 int Vset = 7500:
                                          //output voltage setpoint 8000=80kV
155 int Vlimit=8500; //output voltage upper limit (85kV)<br>156 int Vinmin=150: //input voltage minimum limit for n
156 int Vinmin=150; //input voltage minimum limit for power supply operation<br>157 int Ptime = 10; //pulse time setpoint in uS 100=10ms (duration of output pul
157 int Ptime = 10; //pulse time setpoint in uS 100=10ms (duration of output pulse)<br>158 int LOCKtime=100; //lockout time(post pulse trigger inhibit) setpoint in uS (100
                                               1/lockout time(post pulse trigger inhibit) setpoint in uS (100=10ms)
 159 int Fmax=250; //max frequency limit(user input)
```
160 int Fres=185; //resonant frequency(user input)<br>161 int PWMpermin=37600; //minimum PWM period( 161 int PWMpermin=37600; //minimum PWM period(corosponds to maxumum frequency)<br>162 int PWMperres=50810; //resonant PWM period(corosponds to resonant frequency)  $1$ esonant PWM period(corosponds to resonant frequency) 163 //int Fmin=150; //min frequency limit(user input)<br>164 int Dtvmax=100: //max duty cycle limit 164 int Dtymax=100; //max duty cycle limit<br>165 int Dtymin=50: //mim duty cycle limit //mim duty cycle limit 166 int VoutminTH=2; //Vout startup threshold(5=50%Vset, if not above threshold, at given time, shutdown) 167 int VsetTH=750; //Vout startup internal threshold (pre-calc value to eliminate devide operation in loop)<br>168 int VoutminTHtime=10: //Vout startup threshold time(10=0.1ms) 168 int VoutminTHtime=10; //Vout startup threshold time(10=0.1ms)<br>169 int VoutminTHtimeTMR2=0; //Vout startup threshold time converte  $1/1$ Vout startup threshold time converted to counts of TMR2 170 171 //PID variables<br>172 int Kpfreq=0; 172 int Kpfreq=0; //preportinal term gain<br>173 int Kifreq=0; //integral term gain 173 int Kifreq=0; //integral term gain<br>174 int Kilimit=2000; //limit on integral 174 int Kilimit=2000; //limit on integral accumulator<br>175 signed int KiACC=0; //integral term accumulator  $//$ integral term accumulator 176 177 int ADC\_convINTcount=0; //ADC interupts during the pulse 178 int ADC\_trigINTcount=0; //ADC trigger requests during pulse<br>179 //int ADCthcnt=0; //ADC samples under a given thresho 179 //int ADCthcnt=0; //ADC samples under a given threshold###########debuging<br>180 //int ADCth=200; //ADC sample threshold##########debuging //ADC sample threshold##########debuging 181 182 //measured voltage and current<br>183 int Vout=0: //outpu 183 int Vout=0;  $\frac{183 \text{ int} \text{ Vout}}{184 \text{ int} \text{ Iout}}$ //output current 185 int Vin=0;  $\frac{\text{Number of 186}}{\text{Number of 186}}$ //input current 187 signed int Vouterror=0; //voltage error 188 189 //pulse data storage<br>190 int VinBuff3[3]; 190 int VinBuff3[3]; //cyclic buffer for ADC input 191 int VinBuff3ptr; //array element pointer //array element pointer 192 int MedianBuff[3]; 193 //int timearr[40]; 194 //int Voutarr[40]; 195 //int Vinarr[40]; 196<br>197 // 197 //--- 198 // \*\*\*\*\*\*\*\*\* MAIN function \*\*\*\*\*\*\*\*\*\*\*\*\* 199 //--- 200 int main(void){ 201 202 //for safety, the first thing on power up, make sure pwm output is stopped 203 //incase processor crashed and reset, leaving PWM generator in the on state 204 //Overide PWM outputs to shutdown pwm 204 //Overide PWM outputs to shutdown pwm<br>205 / IOCON1bits.OVRENH=1: //PW  $\frac{1000 \text{ N} \cdot \text{D} \cdot \text{D} \cdot \text{D} \cdot \text{D} \cdot \text{D} \cdot \text{D} \cdot \text{D}}{1000 \text{ N} \cdot \text{D} \cdot \text{D} \cdot \text{D} \cdot \text{D} \cdot \text{D} \cdot \text{D}} = \frac{1}{2}$  // PWMI pin override output value =OVRDAT<1> (1) or PWM gen output(0) 206 IOCON1bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)<br>207 IOCON2bits OVRENH=1: // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0) 10CON2bits.OVRENH=1; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0)<br>10CON2bits.OVRENI =1: // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0) 208 IOCON2bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)<br>209 IOCON3bits.OVRENH=1; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0) 209 IOCON3bits.OVRENH=1; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0)<br>210 IOCON3bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0) // PWML pin override output value = OVRDAT<0> (1) or PWM gen output(0)  $\frac{211}{212}$ 212 PSCONFIG.PWMlockout=1; //enable PWM lockout<br>213 PSCONFIG.ConFreq=1; //set to 1 (Feedback on by  $1/1$ set to 1 (Feedback on by default) 214 215 //initilize non-critical systems<br>216 initCORE(); //init system 216 init CORE();<br>217 uartsetup(); 217 uartsetup();  $\frac{1}{218}$  // setup UART for communication alcosetup();  $\frac{1}{218}$  // setup ADC  $\frac{1}{2}$  setup ADC 219 timersetup();  $\frac{1}{220}$  is the  $\frac{1}{220}$  is setup timers  $\frac{1}{220}$  is setup to  $\frac{1}{20}$  setup i/o pins 220 iosetup();  $\frac{1}{221}$  is and ports  $\frac{221}{21}$  pwmsetup();  $\frac{1}{21}$  is setup PWM system  $p$ wmsetup();  $\qquad$  // setup PWM system 222 223 //now that timers are setup lockout PWM for designated time on startup 224 //since the first PWMstop() is called before timer setup, it may cleared<br>225 PWMlockout(): //start timer2 for PWM lockout MUSI PWMlockout(); //start timer2 for PWM lockout MUST BE CALLED AFTER PWMstop() 226 227 //initilize interupts(after PWM lockout is started) 228 INTsetup(); // setup INT 0,1,2 interupts  $229$ 230 //init received character value and print out RESET to console 231 received= $\frac{10^{11}}{2}$ received='\0': 232 printSerialROM\_str(ResetString); //print out string that says "RESET" 233 234 //print out cause of reset and intcon1 configuration

235 // printSerialROM\_str(NL);<br>236 printSerialROM str("RCC 236 printSerialROM\_str("RCON= \0"); //print out RCOD data to display cause of reset 237 printSerial binary int(RCON): 237 printSerial\_binary\_int(RCON);<br>238 printSerialROM str(NL); 238 printSerialROM\_str(NL);<br>239 printSerialROM\_str("INT) 239 printSerialROM\_str("INTCON1= $\langle 0" \rangle$ ; //print intcon1 to display configuration of interupts<br>240 printSerial binary int(INTCON1) printSerial\_binary\_int(INTCON1); 241 printSerialROM\_str(NL);<br>242 printSerialROM\_str(NL); printSerialROM\_str(NL); 243 244 //alert if watchdog timer timeout was cause of reset 245 if(RCONbits.WDTO==1){ 246 printSerialROM\_str("WDT RESET: Woof Woof \"The Watchdog\" did not get feed \r\n\0");<br>247 RCONbits.WDTO=0; RCONbits.WDTO=0; 248 } 249 250 251 // Main Program Loop (entire program is interupt driven) 252 while(1){ 253<br>254 MAINcount++;  $//$  increment loop counter 255 256 //Power supply error<br>257 if(PSCONFIG.PSe 257 if(PSCONFIG.PSerror==1){<br>258 printSerialROM str("\r\n--258 printSerialROM\_str("\r\n-----------Power supply error:-----------\0");<br>259 PSCONFIG PSerror=0. PSCONFIG.PSerror=0;  $\frac{260}{261}$ //output over voltage limit error 262 if(PSCONFIG.aboveVlimit==1){<br>263 printSerialROM str("\r\nOutpu printSerialROM\_str("\r\nOutput overvoltage\0"); 264 PSCONFIG.aboveVlimit=0;<br>265 }  $\frac{265}{266}$ 266 //external interupt error<br>267 if(PSCONFIG.extIN) if(PSCONFIG.extINTerror==1){ 268 printSerialROM\_str("\r\nExternal error interupt\0");<br>269 PSCONFIG.extINTerror=0; PSCONFIG.extINTerror=0; 270 }  $\frac{271}{272}$ 272 //Vin capacitor bank feedback sensor not conected or voltage too low<br>  $273$  if (PSCONFIG.lowVin==1){ 273 if(PSCONFIG.lowVin==1){<br>274 printSerialROM\_str("\r\nV printSerialROM\_str("\r\nVin too low or sensor disconected\0"); 275 PSCONFIG.low $\overline{V}$ in=0; //DC link undervolt flag<br>276 } 276 } 277 278 //Vout feedback sensor not conected or voltage too low during startup  $279$  if (PSCONFIG.low Vout==1){ 279 if(PSCONFIG.lowVout==1){<br>280 printSerialROM str("\r\nVo 280 printSerialROM\_str("\r\nVout too low or sensor disconected\0");<br>281 **PSCONFIG** lowVout=0: //Output undervolt flag PSCONFIG.lowVout=0; //Output undervolt flag 282 283 284 //Power supply error list newline to prevent last entery from being covered by ADC data output 285 reinfSerialROM str(NL): printSerialROM\_str(NL); 286 printSerialROM\_str(NL);<br>287 } 287 } 288 289 290 //transmit PS data<br>291 if(ProgCON.PS 291 if(ProgCON.PSDataReady==1){<br>292 PSprintdata(): 292 PSprintdata();<br>293 ProgCON.PSI ProgCON.PSDataReady=0; 294 } 295  $296$  //transmit data string<br>297 if (ProgCON.TxDa 297 if  $(Program.TxDataReady=1){$ <br>
298 TxData(); // trans 298 TxData(); // transmit data<br>299 ProgCON.TxDataReady=0: ProgCON.TxDataReady=0; 300 } 301 302 //parse recived data if ProgCON.RxDataReady is set by interupts 303 if (ProgCON.RxDataReady==1){ 304 305 printSerialROM\_str(NL);<br>306 printSerialROM\_str(Sbuf! 306 printSerialROM\_str(SbufString);<br>307 printSerial\_str(RxDataString);  $1/7$  print received string to terminal 308 309 parse\_string(RxDataString); // Parse received string for commands

310 clrRXdata(); //clear RX data buffer<br>311 ProgCON.RxDataReady=0; //clear progra 311 ProgCON.RxDataReady=0; //clear program control flag to parse data 312  $\frac{1}{2}$  //end if  $}/\ell$ end if 313 314 315 }//end while 316 }//end main 317  $318$ <br> $319$  //--- 319 //--- 320 // Transmit data set as ASCII srting 321 //--- 322 void TxData(void){ 323 printSerialROM\_str(HOME); 325 326 if (received=='#'){<br>327 printSerialROM 327 printSerialROM\_str(CLS);<br>328 received=0; 328 received=0;<br>329  $\frac{1}{\frac{329}{1-\frac{1}{2}}}$  $}/\ell$ end if 330 else { 331<br>332 332 printSerialROM\_str(Ch0123String);<br>333 printSerial signed int(ADC Ch0): 333 printSerial\_signed\_int(ADC\_Ch0);<br>334 printSerial\_signed\_int(ADC\_Ch1); printSerial\_signed\_int(ADC\_Ch1);  $335$  printSerial\_signed\_int(ADC\_Ch2);<br> $336$  printSerial\_signed\_int(ADC\_Ch3); 336 printSerial\_signed\_int(ADC\_Ch3);<br>337 printSerialROM str(ADCString); 337 printSerialROM\_str(ADCString);<br>338 printSerial\_int(ADC\_INTcount); printSerial\_int(ADC\_INTcount);  $339$ <br> $340$  // 340 // printSerialROM\_str(" ADCth=");<br>341 // printSerial int(ADCthcnt): printSerial\_int(ADCthcnt);  $342$ <br> $343$  // printSerialROM\_str(ConfigString); 344<br>345 345 printSerialROM\_str(SbufString);<br>346 printSerial\_str(RxDataString); printSerial\_str(RxDataString); 347<br>348 // printSerialROM\_str(NL); 349 350 } //end else 351 352 } 353  $354$ <br> $355$  //-- 355 //--- 356 // U1RX interrupt, triggered by incoming serial data 357 //--- 358 void \_\_attribute\_\_((\_\_interrupt\_\_)) \_U1RXInterrupt(void){ 359 IFS0bits.U1RXIF = 0; // clear interrupt flag<br>360 U1RX\_INTcount++; // increment interupt  $1/1$  increment interupt counter 361 while(U1STAbits.URXDA){ //while there is data in buffer 363 364 received = U1RXREG; //received character into temp variable 365 //(reading the character, pops it from buffer stack) 366<br>367 367 if(received  $==$  '\$'){<br>368 clrRXdata();  $1$ //clear RX data buffer 369<br>370 370 RxDataString[RxDataPoint]=received; // store received char into Rx data string<br>371 RxDataPoint++; // incriment pointer  $//$  incriment pointer 372  $373$  }//end if<br> $374$  else if(re 374 else if(received  $= \langle r' \rangle$ { //if carage return<br>375 RxDataPoint++; //incriment point //incriment pointer 376 RxDataString[RxDataPoint]='\0'; //write zero after end of data<br>377 RxDataString[80]='\0'; //write zero to end of string buffer  $\frac{1}{2}$ RxDataString[80]='\0'; //write zero to end of string buffer (backup overflow prevention)<br>RxDataPoint = 0; //reset pointer beck to beginning of string  $378$  RxDataPoint = 0; //reset pointer beck to beginning of string 379 380 ProgCON.RxDataReady=1; //set program control flag to parse data 381 382 *}//end else if*<br>383 else if(receive else if(received == 0x08){ //if backspace<br>if(RxDataPoint>0){RxDataPoint--;} //decrim

384 if(RxDataPoint>0){RxDataPoint--;} //decriment pointer if greater then zero, else just clear the first char

385 RxDataString[RxDataPoint]='\0'; //write zero after end of data 386 }//end else if 386 }//end else if 387 388 else{<br>389 Rx 389 RxDataString[RxDataPoint]=received; // store received char into Rx data string  $//$  incriment pointer 391 }//end else 392 393 }//end while 394 395 } 396 397<br>398 //-- 398 //--- 399 // Clear RX data buffer  $400$  //---- 401 void clrRXdata(void){ 402 RxDataString[0]='\0'; //clear buffer (write zeros)<br>403 for(RxDataPoint=0; RxDataPoint!=80; RxDataPoint++){ 403 for(RxDataPoint=0; RxDataPoint=80; RxDataPoint++){<br>404 RxDataString[RxDataPoint]='\0'; //clear buffer (write zeros) 404 RxDataString[RxDataPoint]= $\sqrt{0}$ ;<br>405  $\frac{1}{2}$  //end for  $405$  }//end for<br>406 RxDataStr 406 RxDataString[80]= $\sqrt{0}$ ;<br>407 RxDataPoint = 0;  $//$  UART Rx data string pointer 408 } 409 410 411 //--- 412 // INT0 interrupt, error detection from i/o extender 413 //--- 414 void \_\_attribute\_\_((\_\_interrupt\_\_)) \_INT0Interrupt(void) 415 { 416 IFS0bits.INT0IF = 0;  $\frac{1}{2}$  // clear(0) interrupt flag<br>417 PWMstop();  $\frac{1}{2}$  // stop PWM output 417 PWMstop(); // stop PWM output<br>418 PSCONFIG.PSerror=1; // set error flag 418 PSCONFIG.PSerror=1; // set error flag<br>419 PSCONFIG.extINTerror=1; // set external  $1/1$  set external interupt error flag 420 421 } 422 423 424 //--- 425 // INT1 interrupt, front panel push button  $426$  //---- 427 void \_\_attribute\_\_((\_\_interrupt\_\_)) \_INT1Interrupt(void) 428 {<br>429 IFS1bits.INT1IF = 0;  $1/2$  clear(0) interrupt flag 430 431 //start PWM pulse<br>432 if((IOCON1bits) if((IOCON1bits.OVRENH==1)&(PSCONFIG.PWMlockout==0)){ // If the pulse isnt running and lockout disabled 433 if((Vin<Vinmin)&(PSCONFIG.dummypulse==0)){<br>434 PSCONFIG.PSerror=1; //set power supply 434 PSCONFIG.PSerror=1; //set power supply error flag<br>435 PSCONFIG.lowVin=1; //set DC link undervolt flag //set DC link undervolt flag 436 PWMstop(); //shut down power supply 437<br>438 438 else{<br>439 PWMstart();  $4/3$  start pulse timer and enable outputs  $\begin{matrix}440\\441\end{matrix}$  }//  $\frac{1}{4}$  end of if statement 442 443 } 444 445  $446$ <br> $447$  //- 447 //--- 448 // INT2 interrupt, optical trigger in 449 //--- 450 void \_\_attribute\_\_((\_\_interrupt\_\_)) \_INT2Interrupt(void) 451 { 452 IFS1bits.INT2IF = 0;  $\angle$  // clear(0) interrupt flag 453 454 //start PWM pulse<br>455 if((IOCON1bits) 455 if((IOCON1bits.OVRENH==1)&(PSCONFIG.PWMlockout==0)){ // If the pulse isnt running and lockout disabled <br>456 if((Vin<Vinnin)&(PSCONFIG dummypulse==0)){ // If the pulse isnt running and lockout disabled 456 if((Vin<Vinmin)&(PSCONFIG.dummypulse==0)){<br>457 PSCONFIG.PSerror=1; //set power supply 457 PSCONFIG.PSerror=1; //set power supply error flag<br>458 PSCONFIG.lowVin=1; //set DC link undervolt flag 458 PSCONFIG.lowVin=1; //set DC link undervolt flag<br>459 PWMstop(); //shut down power supply //shut down power supply

```
\begin{matrix} 460 & 1 \\ 461 & e \end{matrix}461 else{<br>462 PWMstart();
                                         \frac{1}{4} start pulse timer and enable outputs
\begin{array}{c} 463 \\ 464 \end{array} }//
          464 }// end of if statement 
 465 
 466 } 
 467 
\frac{468}{469}//---
 469 //----------------------------------------------------------------------------- 
 470 // TMR1 interrupt, used to trigger ADC 
 471 //----------------------------------------------------------------------------- 
 472 void __attribute__((__interrupt__)) _T1Interrupt(void) 
473\{ 474
474 IFS0bits.T1IF = 0; \frac{1}{2} // clear interrupt flag, set when timer=PR1 475 TMR1=0; \frac{1}{2} // clear timer register
                                       \frac{1}{\sqrt{2}} clear timer register
 476 
477 //##################for testing<br>478 if((IOCON1bits.OVRENH=
478 if((IOCON1bits.OVRENH==0)){ //if the pulse is active ADC_trigINTcount++; //ADC interupts during the
       \overrightarrow{ADC\_trigINTcount++}; //ADC interupts during the pulse
 480 } 
 481 
482 //ADC now triggered using speciel event trigger from TMR1 period match 483 // ADCPC0bits.SWTRG0=1: //Start conversion of AN0 and AN1 if
483 // ADCPC0bits.SWTRG0=1; //Start conversion of AN0 and AN1 if trigger source is SWTRG 484 // ADCPC0bits.SWTRG1=1; //Start conversion of AN2 and AN3 if trigger source is SWTRG
                                                    1/Start conversion of AN2 and AN3 if trigger source is SWTRG
 485 } 
 486 
 487 
 488 
 489 //----------------------------------------------------------------------------- 
 490 // TMR2 interrupt, used to time power supply output pulse 
491 //----
 492 void __attribute__((__interrupt__)) _T2Interrupt(void) 
493 {<br>494 IFS0bits.T2IF = 0;
494 IFS0bits.T2IF = 0; \text{/}/ clear interrupt flag, set when timer=PR2<br>495 T2CONbits.TON=0; \text{/}/ 1=> start timer, 0=> stop timer
495 T2CONbits.TON=0; \frac{1}{2} / 1=> start timer, 0=> stop timer<br>496 TMR2=0; \frac{1}{2} / clear timer register
496 TMR2=0; // clear timer register<br>497 IEC0bits.T2IE = 0; // disable timer inte
                                          1/4 disable timer interupt(timer not runing after pulse ends)
 498 
 499 //trigger PWM lockout 
500 if((IOCON1bits.OVRENH==0)){ //if PWM is running
 501 PSCONFIG.PWMlockout=1; //enable PWM lockout 
502 PWMlockout(); //start timer2 for PWM lockout<br>503 ProgCON.PSDataReady=1: //set flag to print PWM d
           ProgCON.PSDataReady=1; //set flag to print PWM data to console
504 }<br>505 else{
                                   /if PWM lockout enabled and pulse not running
506 PSCONFIG.PWMlockout=0; //clear lockout
 507 } 
508 //stop PWM pulse(called twice,at pulse end and lockout end for safety)<br>509 PWMstop(); //stop PWM pulse
509 PWM stop();
 510 } 
 511 
 512 
 513 //----------------------------------------------------------------------------- 
 514 // TMR3 interrupt, used to send data I/O 
 515 //----------------------------------------------------------------------------- 
 516 void __attribute__((__interrupt__)) _T3Interrupt(void) 
 517 { 
518 IFS0bits.T3IF = 0; \frac{1}{2} // clear interrupt flag<br>519 TMR3=0; \frac{1}{2} // clear timer register (r
519 TMR3=0; // clear timer register (reset timer)
520 ProgCON.TxDataReady = 1; //set program control flag to transmit data
 521 } 
522<br>523 //---
 523 //----------------------------------------------------------------------------- 
 524 // PWMstart enable PWM outputs and start TMR2 to time pulse lenght 
 525 //----------------------------------------------------------------------------- 
 526 void PWMstart(void){ 
 527 
 528 //set control variables to default 
 529 //duty cycle = 100% (varies between 50-100%) 
 530 //PWMfreq controls PWM frequency 200 => 20kHz 
 531 PWMfreq=Fres; 
 532 
 533 //clear old pulse data
```

```
534 IIN_DATA_MAX = 0; \frac{1}{2} // max current from bank
```

```
535 IIN_DATA_MIN = 9999; // min current from bank(set to large number, so less then operation will overwrite) 536 VIN DATA MAX = 0: // max voltage on input
536 VIN_DATA_MAX = 0; \frac{1}{2} // max voltage on input 537 VIN_DATA_MIN = 9999; \frac{1}{2} // min voltage on input
537 VIN_DATA_MIN = 9999; // min voltage on input(set to large number, so less then operation will overwrite)<br>538 IOUT DATA MAX = 0: // max current to load
538 IOUT_DATA_MAX = 0; // max current to load<br>539 VOUT_DATA_MAX = 0; // max voltage to load
539 VOUT_DATA_MAX = 0;<br>540 TVSP_DATA = 0;
                                              1/1 time to reach data setpoint
541 TVMAX DATA = 0; \frac{1}{2} // time to reach max voltage
 542 
543 //clear old variables<br>544 KiACC=0;
                                         //integral term accumulator
545 ADC_convINTcount=0; //ADC interupts during the pulse<br>546 ADC_trigINTcount=0; //ADC trigger requests during puls
546 ADC_trigINTcount=0; //ADC trigger requests during pulse<br>547 VsetTH=Vset/10:
547 VsetTH=Vset/10;<br>548 VinBuff3[0]=Vin;
        VinBuff3[0]=Vin; //cyclic buffer for ADC input<br>VinBuff3[1]=Vin; //cyclic buffer for ADC input
549 VinBuff3[1]=Vin; //cyclic buffer for ADC input 550 VinBuff3[2]=Vin; //cyclic buffer for ADC input
550 VinBuff3[2]=Vin; //cyclic buffer for ADC input<br>551 VinBuff3ptr=0; //array element pointer
                                          //array element pointer
 552 
 553 
554 //set timer 1 to trigger ADC at higher sampling rate during pulse<br>555 T1CONbits.TCKPS=0b00; // prescale: 0b00=>clk/1, 0b
555 T1CONbits.TCKPS=0b00; // prescale: 0b00=>clk/1, 0b01=>clk/8, 0b10=>clk/64, 0b11=>clk/256<br>556 TMR1=0: // clear timer register
556 TMR1=0; \frac{1}{2} // clear timer register<br>557 PR1=200; \frac{1}{2} // Interrupt after this n
                                       // Interrupt after this many cycles
 558 
559 //Toggle PWM generator enable to reset timebase to 0<br>560 PTCONbits.PTEN=0; //Enable(1) or Disab
560 PTCONbits.PTEN=0; // Enable(1) or Disable(0) PWM timebase
561 PTCONbits.PTEN=1; // Enable(1) or Disable(0) PWM timebase
 562 
563 //set PTCONbits.EIPU=1 during changes of preiod and duty cycle so they take place before the cycle starts 564 PTCONbits.EIPU=1: // Active period undates immediativ(1) or on cycle bounderies(0)
                                                     \#Active period updates immediatly(1) or on cycle bounderies(0)
 565 
566 if(PSCONFIG.ConFreq==1){ //if in frequency control mode<br>567 PWMper=(Vset/(Vin+1))*1724+29706; //faster calculation of PW.
           PWMper=(Vset/(Vin+1))*1724+29706; //faster calculation of PWM period(fewer devides required)
568 }<br>569 else{
569 else{<br>
\frac{\text{else}}{\text{from }10000} /manual frequency setpoint for testing<br>
\frac{\text{FWMper}}{\text{from }10000} / PTPER<15:3>: PWM
        PWMper=235*(40000/PWMfreq); // PTPER<15:3>: PWM Time Base Period Value bits (20kHz = 47000 ~(235*200) for complimentary,)
 571 } 
 572 
 573 
        PTPER=PWMper;<br>MDC=PTPER/2;
575 MDC=PTPER/2; // MDC<15:0> PWM MASTER DUTY CYCLE REGISTER (0xFFFF to 0x0008)<br>576 DTR1=50+(PTPER/2)*(100-Dtv): // Dead time register
576 DTR1=50+(PTPER/2)*(100-Dty); // Dead time register<br>577 DTR2=DTR1; // Dead time register
577 DTR2=DTR1; // Dead time register<br>578 DTR3=DTR1; // Dead time register
578 DTR3=DTR1; // Dead time register
579 ALTDTR1=DTR1; // Alternate Dead time register
580 ALTDTR2=DTR1;<br>581 ALTDTR3=DTR1: // Dead time register
581 ALTDTR3=DTR1; // Dead time register<br>582 PHASE1=0: // PWM timebase phase s
        PHASE1=0; \frac{1}{2} // PWM timebase phase shift time value<br>PHASE2=PTPER*1/3: // PWM timebase phase shift time
583 PHASE2=PTPER*1/3; // PWM timebase phase shift time value<br>584 PHASE3=PHASE2*2; // PWM timebase phase shift time value
584 PHASE3=PHASE2*2; // PWM timebase phase shift time value
 585 
586 PTCONbits.EIPU=0; // Active period updates immediatly(1) or on cycle bounderies(0)
 587 
 588 //-------------start watchdog timer before pulse---------------- 
589 RCONbits.SWDTEN=1; //turn on(1) or off(0) software watchdog timer enable
590<br>591 //-
 591 //---------------code to start output pulse------------------ 
592 // now config timer 2 to control power supply output pulse<br>593 //Ptime => pulse time setpoint 100=10ms
            \frac{1}{9} //Ptime => pulse time setpoint 100=10ms<br>PR2=(460*Ptime)/10; //(4692=>10n
594 PR2=(460*Ptime)/10; // (4692=>10ms) Interrupt after this many cycles timer runs ar Fosc/4<br>595 //VoutminTHtime=> Vout startup threshold time(10–0 1ms)
595 //VoutminTHtime=> Vout startup threshold time(10=0.1ms)<br>596 VoutminTHtimeTMR2=(46*VoutminTHtime)/10; //set sta
             596 VoutminTHtimeTMR2=(46*VoutminTHtime)/10; //set startup threshold timer 
 597 
598 // start countdown<br>599 TMR2=0:
599 TMR2=0; // clear timer register<br>600 IECObits.T2IE = 1; // 1=> enable intern
                                          \frac{1}{2} = enable interrupts, 0= disable interupts
 601 T2CONbits.TON=1; // 1=> start timer, 0=> stop timer 
 602 
603 //enable pwm pins<br>604 IOCON1bits.PENH=1:
 604 IOCON1bits.PENH=1; // PWMxH pin is enabled(1, PWM) or disabled(0, general i/o) 
 605 IOCON2bits.PENH=1; // PWMxH pin is enabled(1, PWM) or disabled(0, general i/o) 
 606 IOCON3bits.PENH=1; // PWMxH pin is enabled(1, PWM) or disabled(0, general i/o) 
 607 
            IOCON1bits.PENL=1; // PWMxL pin is enabled(1, PWM) or disabled(0, general i/o)<br>IOCON2bits.PENL=1; // PWMxL pin is enabled(1, PWM) or disabled(0, general i/o)
 609 IOCON2bits.PENL=1; // PWMxL pin is enabled(1, PWM) or disabled(0, general i/o)
```

```
 610 IOCON3bits.PENL=1; // PWMxL pin is enabled(1, PWM) or disabled(0, general i/o) 
 611 
612 //Enable PWM outputs<br>613   IOCON1bits.OVRENH=0;
613 IOCON1bits.OVRENH=0; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0) 614 IOCON1bits.OVRENL=0: // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)
614 IOCON1bits.OVRENL=0; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)<br>615 IOCON2bits OVRENH=0; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0)
 615 IOCON2bits.OVRENH=0; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0) 
616 IOCON2bits.OVRENL=0; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)<br>617 IOCON3bits.OVRENH=0: // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0)
 617 IOCON3bits.OVRENH=0; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0) 
 618 IOCON3bits.OVRENL=0; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0) 
 619 } 
620<br>621 //--
 621 //----------------------------------------------------------------------------- 
 622 // PWMstop disable PWM outputs and stop pulse 
 623 //----------------------------------------------------------------------------- 
 624 void PWMstop(void){ 
 625 
626 //set timer 1 (ADC trigger) to lower sampling rate after pulse 627 T1CONbits.TCKPS=0b01; // prescale: 0b00=>clk/1,
627 T1CONbits.TCKPS=0b01; // prescale: 0b00=>clk/1, 0b01=>clk/8, 0b10=>clk/64, 0b11=>clk/256<br>628 TMR1=0: // clear timer register
628 TMR1=0; \frac{1}{2} / clear timer register 629 PR1=10000; \frac{1}{2} / Interrupt after this
                                        \frac{1}{2} Interrupt after this many cycles 16mhz
 630 
 631 //---------------code to stop output pulse------------------ 
 632 
633 //Overide PWM outputs to shutdown pwm(soft switching shutdown, activates at cycle boundary)<br>634 / IOCON Ibits OVR ENH=1: //PWMH pin override output value = OVRDAT<1> (1) or PW
 634 IOCON1bits.OVRENH=1; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0) 
635 IOCON1bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)<br>636 IOCON2bits.OVRENH=1: // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0)
636 IOCON2bits.OVRENH=1; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0) 637 IOCON2bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)
637 IOCON2bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)<br>638 IOCON3bits.OVRENH=1: // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0)
                                                   // PWMH pin override output value = OVRDAT<1> (1) or PWM gen output(0)
 639 IOCON3bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0) 
 640 
641 //--------------stop watchdog timer after pulse--------------<br>642 RCONbits.SWDTEN=0; //turn on(1) or off
                                                 //turn on(1) or off(0) software watchdog timer enable
 643 
644 //------------------clear dummy pulse flag if it was a dummy pulse------------<br>645 PSCONFIG.dummypulse=0; //dummy pulse flag
645 PSCONFIG.dummypulse=0;
 646 } 
647<br>648 //-
 648 //----------------------------------------------------------------------------- 
 649 // PWMlockout starts timer2 for a time during which the pulse can't be re-triggered 
 650 //----------------------------------------------------------------------------- 
 651 void PWMlockout(void){ 
652 PR2=(469*LOCKtime)/10; // (1173=>10ms) Interrupt after this many cycles timer runs ar Fosc/4<br>653 TMR2=0: // clear timer register
      TMR2=0; \angle // clear timer register<br>IEC0bits.T2IE = 1; \angle // 1=> enable intern
654 IECObits.T2IE = 1; \frac{1}{1} => enable interrupts, 0=> disable interupts<br>655 T2CONbits.TON=1: \frac{1}{1} => start timer. 0=> stop timer
                                         1/1 => start timer, 0=> stop timer
 656 } 
 657 
 658 //----------------------------------------------------------------------------- 
 659 // ADC interrupt, triggered when ADC conversion completes 
 660 //----------------------------------------------------------------------------- 
 661 void __attribute__((__interrupt__)) _ADCInterrupt(void) 
 662 { 
663 IFS0bits.ADIF=0; // reset interupt flag<br>664 ADC_INTcount++; // inc interupt coun
                                         // inc interupt counter
 665 
666 if(ADSTATbits.P0RDY==1){ //if ADC pair 0 converted 667 ADC_Ch0 = ADCBUF0; // pin 2 (Vout)
667 ADC_Ch0 = ADCBUF0; \frac{\text{N}}{\text{pin 2 (Vout)}}<br>668 ADC_Ch1 = ADCBUF1; \frac{\text{N}}{\text{pin 3 (Iout)}}ADC\_Ch1 = ADCBUF1; 669 ADSTATbits.P0RDY=0; // ADSTATbits.P#RDY Conversion Data for Pair # Ready(1) 
 670 } 
671 if(ADSTATbits.P1RDY==1){ //if ADC pair 1 converted<br>672 ADC_Ch2 = ADCBUF2; //pin 4 (Vin)
672 ADC_Ch2 = ADCBUF2; // pin 4 (Vin)673 ADC_Ch3 = ADCBUF3; // pin 5 (lin)674 ADSTATbits.P1RDY=0; // ADSTATbits.P#RDY Conversion Data for Pair # Ready(1)
 675 } 
 676 
 677 //----------------calculate voltages and currents from ADC inputs 
678 Vout=(ADC_Ch0*10); //assuming 10000=100kV (20000:1 probe)<br>679 Iout=(ADC_Ch1); //assuming ?x probe (?:1)
                                         \sqrt{a}ssuming ?x probe (?:1)
680 Vin=(ADC_Ch2); //assuming 200x probe(1kV in = 5V => ADC_Ch2=1013) 1000=1kV<br>681 Iin=(ADC_Ch3); //assuming ?x probe (?:1)
                                       \sqrt{a}ssuming ?x probe (?:1)
 682 
 683 
 684 //if(Vin<ADCth){ADCthcnt++;} //#######threshold counter for testing
```
 685 686 //---------------run control loop------------------------------ 687 if((IOCON1bits.OVRENH==0)){//if the pulse (or dummypulse) is active, so start control loop 688 ADC\_convINTcount++; //ADC interupts during the pulse 689 PWMcontrol(); // Use new ADC data to update Dty or  $\frac{1}{2}$  // Use new ADC data to update Dty or Freq 690 }//end if 691 692 //---------------clear watchdog timer-------------------------- 693 //for safety WDT is enabled during pulse, WDT will reset dsPIC in 2mS if not cleared in control loop //clear watchdog timer if control loop is running 695 } 696 697<br>698 //-- 698 //--- 699 // Sort 3 element array and return median value  $700$  //--- 701 int opt\_med3(int \* p){ 702 PIX\_SORT(p[0],p[1]); 703 PIX\_SORT(p[1],p[2]); 704 PIX\_SORT(p[0],p[1]); 705  $return(p[1])$ ; 706 } 707  $708$ <br> $709$  //----- 709 //--- 710 // Update PWM control variables 711 //--- 712 void PWMcontrol(void){ 713 714 //----------------filter data----------------------------- 715 716 //write to cyclic buffer 717 // VinBuff3ptr++; //array element pointer 718 //if(VinBuff3ptr>2){ //reset pointer 719 // VinBuff3ptr=0;} 720 // VinBuff3[VinBuff3ptr]=Vin; //cyclic buffer for ADC input 721 722 //copy array 723 // MedianBuff[0]=VinBuff3[0]; //Median filter buffer 724 // MedianBuff[1]=VinBuff3[1]; //Median filter buffer 725 // MedianBuff[2]=VinBuff3[2]; //Median filter buffer 726 727 //find median value 728 //Vin=opt\_med3(MedianBuff); //Overwrite Vin with filtered value 729 //Vin=(VinBuff3[0]+VinBuff3[1]+VinBuff3[2]+VinBuff3[VinBuff3ptr])>>2;  $730$ <br> $731$  //------------------record data---------------- 732 733 if(Iin>IIN\_DATA\_MAX){ 734 IIN\_DATA\_MAX = Iin;  $\}$  // max current from bank 735 736 if(Iin<IIN\_DATA\_MIN){ 737 IIN\_DATA\_MIN = Iin;  $\frac{1}{2}$  // min current from bank 738 739 if(Vin>VIN\_DATA\_MAX){ 740 VIN\_DATA\_MAX = Vin;}  $\mathcal{W}$  max voltage on input 741 742 if((Vin<VIN\_DATA\_MIN)){ 743 VIN\_DATA\_MIN = Vin;}  $\mathcal{V}$  min voltage on input 744 745 if(Iout>IOUT\_DATA\_MAX){ 746 IOUT\_DATA\_MAX = Iout;} // max current to load 747 748 if(Vout>VOUT\_DATA\_MAX){  $749$  VOUT\_DATA\_MAX = Vout; 750 TVMAX\_DATA= TMR2;} // max voltage to load 751 //note: nested if statments run faster then if with the & of two conditions in argument 752 if(TVSP\_DATA==0){ // time to reach data setpoint 753 if(Vout>Vset){<br>754 TVSP DAT/ TVSP\_DATA = TMR2;  $755$  } 756 } 757 758 //-------------------------update PWM switching frequency------------- 759 if(PSCONFIG.ConFreq==1){ //if in frequency control mode
```
760 //PWMfreq controls PWM frequency 200 => 20kHz<br>761 // Vouterror=(Vout-Vset): //voltage error
761 // Vouterror=(Vout-Vset); //voltage error<br>762 // KiACC=KiACC+Vouterror/64; //integrate error
762 // KiACC=KiACC+Vouterror/64; //integrate error<br>763 // if(KiACC>Kilimit){KiACC=Kilimit:} //limit accumulator positive bound
763 // if(KiACC>Kilimit){KiACC=Kilimit;} //limit accumulator positive bound<br>764 // if(KiACC<-Kilimit){KiACC=-Kilimit;} //limit accumulator negative bound
           if(KiACC<-Kilimit){KiACC=-Kilimit;}
 765 
 766 //compute required PWM frequency 
767 //(Vin+1) to eliminate devide by zero error if Vin=0
768 // PWMfreq=( 275-((Vset/(Vin+1))*100)/14+(Vouterror*Kpfreq)/1024 +(KiACC*Kifreq)/128 );<br>769 PWMper=(Vset/(Vin+1))*1724+29706:
           PWMper=(Vset/(Vin+1))*1724+29706;
 770 }//end if 
771<br>772 //----
                   -------perform safety checks------------------
 773 //if(PWMfreq>Fmax){PWMfreq=Fmax;} //limit commanded frequency in safe bounds 
 774 //if(PWMfreq<Fres){PWMfreq=Fres;} //limit commanded frequency in safe bounds 
 775 if(PWMper<PWMpermin){PWMper=PWMpermin;} //limit commanded frequency in safe bounds 
 776 if(PWMper>PWMperres){PWMper=PWMperres;} //limit commanded frequency in safe bounds 
777<br>778 if(Vout>Vlimit){
                                         1/if over maximum safe voltage limit<br>1/set power supply error flag
779 PSCONFIG.PSerror=1; //set power supply error<br>780 PSCONFIG.aboveVlimit=1; //set over voltage flag
780 PSCONFIG.aboveVlimit=1;<br>781 PWMstop(); //sh
                                       //shut down power supply
 782 } 
 783 //note: nested if statments run faster then if with the & of two conditions in argument 
 784 if(Vin<Vinmin){ 
785 if(PSCONFIG.dummypulse==0){<br>786 PSCONFIG.PSerror=1:
                                               1/8et power supply error flag
787 PSCONFIG.lowVin=1; //set DC link undervolt flag<br>788 PWMstop(); //shut down power supply
                                        //shut down power supply
 789 }} 
 790 
 791 //if((Vout<((Vset*VoutminTH)/10))&(TMR2>VoutminTHtimeTMR2)&(PSCONFIG.dummypulse==0)){ 
 792 //note: nested if statments run faster then if with the & of two conditions in argument 
 793 if(Vout<(VsetTH*VoutminTH)){ 
 794 if(TMR2>VoutminTHtimeTMR2){ 
795 if(PSCONFIG.dummypulse==0){<br>796 PSCONFIG.PSerror=1; //set power supply error flag
796 PSCONFIG.PSerror=1; //set power supply error<br>797 PSCONFIG.lowVout=1; //Output undervolt flag
797 PSCONFIG.lowVout=1;<br>798 PWMstop();
                                        //shut down power supply
 799 }}} 
 800 
 801 
 802 //------------------------update control variables----------------- 
803 // PTPER<15:3>: PWM Time Base Period Value bits (20kHz = 47000 \sim (235*200) for complimentary)
 804 
805 // PTPER=235*(40000/PWMfreq); // PTPER<15:3>: PWM Time Base Period 806 PTPER=PWMper; // PTPER<15:3>: PWM Time Base Period
806 PTPER=PWMper; // PTPER<15:3>: PWM Time Base Period<br>807 MDC=PTPER/2: // MDC<15:0> PWM MASTER DUTY CY
                                             // MDC<15:0> PWM MASTER DUTY CYCLE REGISTER (0xFFFF to 0x0008)
808 PHASE1=0; \frac{\text{W} \times \text{W}}{\text{W} \times \text{W}} timebase phase shift time value 809 PHASE2=PTPER*1/3: \frac{\text{W} \times \text{W}}{\text{W} \times \text{W}} timebase phase shift time
809 PHASE2=PTPER*1/3; // PWM timebase phase shift time value 810 PHASE3=PHASE2*2; // PWM timebase phase shift time value
                                                // PWM timebase phase shift time value
 811 
 812 } 
 813 
 814 
 815 //----------------------------------------------------------------------------- 
 816 // Print PWM data to console 
 817 //----------------------------------------------------------------------------- 
 818 void PSprintdata(void){ 
819<br>820820 printSerialROM_str(NL);<br>821 printSerialROM_str("------
821 printSerialROM_str("----------Pulse Data:---------------|r\n");<br>822 if(PSCONFIG.ConFreq==0){//if in manual mod
822 if(PSCONFIG.ConFreq==0){ //if in manual mode for frequency responce testing 823 printSerialROM str(freqString);
823 printSerialROM_str(freqString);<br>824 printSerial int(PWMfreq);
           printSerial_int(PWMfreq);
 825 } 
 826 printSerialROM_str(dtyString); 
827 printSerial_int(Dty);
828 printSerialROM_str(ptimeString);<br>829 printSerial int(Ptime);
        printSerial_int(Ptime);
830 printSerialROM_str(vsetString);<br>831 printSerial int(Vset);
831 printSerial_int(Vset);<br>832 printSerialROM str(v
832 printSerialROM_str(vlimitString);<br>833 printSerial_int(Vlimit);
        printSerial_int(Vlimit);
 834 printSerialROM_str("\r\nKp= ");
```

```
835 printSerial_int(Kpfreq);<br>836 printSerialROM_str("K
836 printSerialROM_str("Ki=");<br>837 printSerial int(Kifreq);
         printSerial_int(Kifreq);
838<br>839
839 printSerialROM_str("\r\nADCtrig samp= ");<br>840 printSerial int(ADC trigINTcount);
         printSerial_int(ADC_trigINTcount);
841 printSerialROM_str("\r\nADCconv samp=");
 842 printSerial_int(ADC_convINTcount); 
843<br>844
         printSerialROM_str(NL);
845<br>846
846 printSerialROM_str("Data from last pulse:\0");<br>847 printSerialROM_str("\r\nVin MAX= \0");
847 printSerialROM_str("\r\nVin MAX= \0");<br>848 printSerial_signed_int(VIN_DATA_MAX)
       printSerial_signed_int(VIN_DATA_MAX);
849 printSerialROM_str(" Vin MIN= \sqrt{0}");<br>850 printSerial_signed_int(VIN_DATA_MI
850 printSerial_signed_int(VIN_DATA_MIN);<br>851 printSerialROM_str("\r\nIin MAX= \0");
851 printSerialROM_str("\r\nIin MAX= \0");<br>852 printSerial_signed_int(IIN_DATA_MAX);
852 printSerial_signed_int(IIN_DATA_MAX);<br>853 printSerialROM str(" Iin MIN= \0");
853 printSerialROM_str(" Iin MIN= \sqrt{0}");<br>854 printSerial_signed_int(IIN_DATA_MI
854 printSerial_signed_int(IIN_DATA_MIN);<br>855 printSerialROM_str("\r\nVout MAX= \0"
855 printSerialROM_str("\r\nVout MAX= \0");<br>856 printSerial signed int(VOUT DATA MAX
856 printSerial_signed_int(VOUT_DATA_MAX);<br>857 printSerialROM str("Iout MAX= \0");
857 printSerialROM_str(" Iout MAX= \0");<br>858 printSerial signed int(IOUT DATA M.
         printSerial_signed_int(IOUT_DATA_MAX);
 859 
860 printSerialROM_str("\r\nT to Vset= \0");
 861 printSerial_signed_int(TVSP_DATA); 
862 printSerialROM_str(" T to Vmax= \langle 0" \rangle;<br>863 printSerial signed int(TVMAX DATA
         printSerial_signed_int(TVMAX_DATA);
\frac{864}{865}printSerialROM_str(NL);
 866 
 867 } 
 868 
869<br>870 //--
 870 //----------------------------------------------------------------------------- 
 871 // Initilize system variables, stacks 
 872 //----------------------------------------------------------------------------- 
873 void initCORE(void){<br>874 OSCCON=0x3300;
                                              // Select Primary Oscillator
 875 // CORCON= 
 876 } 
 877 
 878 //----------------------------------------------------------------------------- 
 879 // Initilize i/o ports 
 880 //----------------------------------------------------------------------------- 
 881 void iosetup(void){ 
882<br>883 TRISDbits.TRISD0=1;
        TRISDbits.TRISD0=1; // RD0 (pin 15) as input<br>TRISAbits.TRISA9=0; // RA9 (pin 16) as output
884 TRISAbits.TRISA9=0; // RA9 (pin 16) as output
885 TRISFbits.TRISF6=1; // RF6 (pin 14) as input
 886 
 887 } 
 888 
 889 
 890 //----------------------------------------------------------------------------- 
 891 // Initilize INT 0,1,2 interupts 
892 //-----------------------
 893 void INTsetup(void){ 
 894 
895 //INT0 => int from i/o extender<br>896 INTCON2bits.INT0EP=1;
896 INTCON2bits.INT0EP=1; //INT0 Interupt on rising edge(0) of falling edge(1) 897 IPC0bits.INT0IP=6; //INT0 Set priority level 7=>highest, 1=>lowest, 0=>dis
 897 IPC0bits.INT0IP=6; //INT0 Set priority level 7=>highest, 1=>lowest, 0=>disabled 
898 IEC0bits.INT0IE = 1; //INT0 interupt enable(1) or disable(0)
 899 
900 //INT1 => int from front panel button<br>901 INTCON2bits.INT1EP=1; //
901 INTCON2bits.INT1EP=1; //INT1 Interupt on rising edge(0) of falling edge(1) 902 IPC/dbits INT1IP-4: //INT1 Set priority level 7->highest 1->lowest 0->dis
902 IPC4bits.INT1IP=4; //INT1 Set priority level 7=>highest, 1=>lowest, 0=>disabled<br>903 IEC1bits.INT1IE = 1; //INT1 interupt enable(1) or disable(0)
                                                // INT1 interupt enable(1) or disable(0)
 904 
905 //INT2 => int from optical trigger<br>906 INTCON2bits.INT2EP=1;
906 INTCON2bits.INT2EP=1; //INT2 Interupt on rising edge(0) of falling edge(1)<br>907 IPC4bits.INT2IP=5; //INT2 Set priority level 7=>highest, 1=>lowest, 0=>dis
907 IPC4bits.INT2IP=5; //INT2 Set priority level 7=>highest, 1=>lowest, 0=>disabled 908 IEC1bits.INT2IE = 1; //INT2 interupt enable(1) or disable(0)
                                                 //INT2 interupt enable(1) or disable(0)
 909
```
914 //---

```
 916 //----------------------------------------------------------------------------- 
 917 
 918 void pwmsetup(void){ 
 919 
920 //disable PWM controller if enabled at startup SET TO 0 BEFORE CONFIGURATION<br>921 PTCONbits.PTEN=0; // Enable(1) or Disable(0) PWM timebase
                                                       1/2 Enable(1) or Disable(0) PWM timebase
922<br>923
          /pwm timebase setup
924 PTCONbits.EIPU=0; \frac{1}{25} // Active period updates immediatly(1) or on cycle bounderies(0) 925 PTCONbits.PTSIDL=1; \frac{1}{25} // Halt(1) or Run(0) PWM timebase in CPU idle
                                                        \frac{1}{2} Halt(1) or Run(0) PWM timebase in CPU idle
926<br>927
927 PTPER=235*(40000/PWMfreq); // PTPER<15:3>: PWM Time Base Period Value bits (20kHz = 47000 ~(235*200) for complimentary,)<br>928 MDC=PTPER/2: // MDC<15:0> PWM MASTER DUTY CYCLE REGISTER (0xFFFF to 0x0008)
928 MDC=PTPER/2; //MDC<15:0> PWM MASTER DUTY CYCLE REGISTER (0xFFFF to 0x0008)<br>929 DTR I=50+(PTPER/2)*(100-Dtv); // Dead time register
929 DTR1=50+(PTPER/2)*(100-Dty); // Dead time register<br>930 DTR2=DTR1; // Dead time register
930 DTR2=DTR1; // Dead time register<br>931 DTR3=DTR1; // Dead time register
931 DTR3=DTR1; // Dead time register<br>932 ALTDTR1=DTR1; // Alternate Dead
932 ALTDTR1=DTR1; // Alternate Dead time register<br>933 ALTDTR2=DTR1: // Dead time register
933 ALTDTR2=DTR1; // Dead time register<br>934 ALTDTR3=DTR1: // Dead time register
                                                       // Dead time register
935 PHASE1=0; \frac{1}{2} // PWM timebase phase shift time value<br>936 PHASE2=PTPER*1/3: // PWM timebase phase shift time
          PHASE2=PTPER*1/3; // PWM timebase phase shift time value<br>PHASE3=PHASE2*2: // PWM timebase phase shift time value
937 PHASE3=PHASE2*2; // PWM timebase phase shift time value
938
939 PWMCON1bits.MDCS=1; // MDC register provides timebase(1) or PDCx provides timebase(0)<br>940 PWMCON2bits.MDCS=1; // MDC register provides timebase(1) or PDCx provides timebase(0)
940 PWMCON2bits.MDCS=1; // MDC register provides timebase(1) or PDCx provides timebase(0)<br>941 PWMCON3bits.MDCS=1; // MDC register provides timebase(1) or PDCx provides timebase(0)
                                                            \# MDC register provides timebase(1) or PDCx provides timebase(0)
 942 
943 PWMCON1bits.DTC=0; //DTC<1:0> Dead time control Positive(0) Negative(1) or Disabled(2) 944 PWMCON2bits.DTC=0; //DTC<1:0> Dead time control Positive(0) Negative(1) or Disabled(2)
944 PWMCON2bits.DTC=0; // DTC<1:0> Dead time control Positive(0) Negative(1) or Disabled(2)<br>945 PWMCON3bits.DTC=0; // DTC<1:0> Dead time control Positive(0) Negative(1) or Disabled(2)
                                                          \#DTC<1:0 Dead time control Positive(0) Negative(1) or Disabled(2)
946<br>947
947 IOCON1bits.OVRDAT=0b00; // PWM pin override output values <1:0> PWMH=OVRDAT<1> and PWML=OVRDAT<0>948 IOCON2bits.OVRDAT=0b00; // PWM pin override output values <1:0> PWMH=OVRDAT<1> and PWML=OVRDAT<0>
948 IOCON2bits.OVRDAT=0b00; // PWM pin override output values <1:0> PWMH=OVRDAT<1> and PWML=OVRDAT<0>949 IOCON3bits.OVRDAT=0b00; // PWM pin override output values <1:0> PWMH=OVRDAT<1> and PWML=OVRDAT<0>
                                                              // PWM pin override output values <1:0> PWMH=OVRDAT<1> and PWML=OVRDAT<0>
950<br>951
951 IOCON1bits.OVRENH=1; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0) 952 IOCON1bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)
952 IOCON1bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)<br>953 IOCON2bits.OVRENH=1; // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0)
953 IOCON2bits.OVRENH=1; // PWMH pin override output value =OVRDAT<1>(1) or PWM gen output(0)<br>954 IOCON2bits.OVRENL=1; // PWML pin override output value =OVRDAT<0>(1) or PWM gen output(0)
954 IOCON2bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)<br>955 IOCON3bits OVRENH=1: // PWMH pin override output value =OVRDAT<1> (1) or PWM gen output(0)
          \text{IOCON3bits. OVERH=1}; // PWMH pin override output value =\text{OVRDAT} < 1 or PWM gen output(0)<br>\text{IOCON3bits. OVERE=1}; // PWML pin override output value =\text{OVRDAT} < 0 or PWM gen output(0)
956 IOCON3bits.OVRENL=1; // PWML pin override output value =OVRDAT<0> (1) or PWM gen output(0)
957<br>958
          \text{IOCON1bits.PENH=0}; // PWMxH pin is enabled(1, PWM) or disabled(0, general i/o) \text{IOCON2bits.PENH=0}: // PWMxH pin is enabled(1, PWM) or disabled(0, general i/o)
959 IOCON2bits.PENH=0; // PWMxH pin is enabled(1, PWM) or disabled(0, general i/o)<br>960 IOCON3bits.PENH=0: // PWMxH pin is enabled(1. PWM) or disabled(0, general i/o)
                                                        \# PWMxH pin is enabled(1, PWM) or disabled(0, general i/o)
961 IOCON1bits.PENL=0; // PWMxL pin is enabled(1, PWM) or disabled(0, general i/\omega)<br>962 IOCON2bits PENL=0: // PWMxL pin is enabled(1, PWM) or disabled(0, general i/\omega)
962 IOCON2bits.PENL=0; // PWMxL pin is enabled(1, PWM) or disabled(0, general i/o)<br>963 IOCON3bits.PENL=0; // PWMxL pin is enabled(1, PWM) or disabled(0, general i/o)
                                                       // PWMxL pin is enabled(1, PWM) or disabled(0, general i/o)
 964 
965 TRISEbits.TRISE0=0; // RE0 (pin 26) as output(0)<br>966 TRISEbits.TRISE1=0; // RE1 (pin 25) as output(0)
966 TRISEbits.TRISE1=0; \angle // RE1 (pin 25) as output(0)<br>967 TRISEbits.TRISE2=0: \angle // RE2 (pin 24) as output(0)
967 TRISEbits.TRISE2=0; \# RE2 (pin 24) as output(0)<br>968 TRISEbits.TRISE3=0; \# RE3 (pin 23) as output(0)
          TRISEbits.TRISE3=0; \frac{1}{2} // RE3 (pin 23) as output(0)<br>TRISEbits.TRISE4=0; \frac{1}{2} // RE4 (pin 22) as output(0)
969 TRISEbits.TRISE4=0; // RE4 (pin 22) as output(0)<br>970 TRISEbits.TRISE5=0; // RE5 (pin 21) as output(0)
                                                      \frac{1}{2} RE5 (pin 21) as output(0)
 971 
972 IOCON1bits.PMOD=0; // PWMH/PWML pair mode configuration Complementery(0) Independent(1) push-pull(2) 973 IOCON2bits.PMOD=0; // PWMH/PWML pair mode configuration Complementery(0) Independent(1) push-pull(2)
973 IOCON2bits.PMOD=0; // PWMH/PWML pair mode configuration Complementery(0) Independent(1) push-pull(2) 974 IOCON3bits.PMOD=0: // PWMH/PWML pair mode configuration Complementery(0) Independent(1) push-pull(2)
                                                         // PWMH/PWML pair mode configuration Complementery(0) Independent(1) push-pull(2)
 975 
976 IOCON1bits.OSYNC=1; // PWM override update at end of PWM period(1) or CPU clock boundary(0)<br>977 IOCON2bits OSYNC-1: // PWM override update at end of PWM period(1) or CPU clock boundary(0)
977 IOCON2bits.OSYNC=1; // PWM override update at end of PWM period(1) or CPU clock boundary(0)<br>978 IOCON3bits.OSYNC=1: // PWM override update at end of PWM period(1) or CPU clock boundary(0)
978 IOCON3bits.OSYNC=1; // PWM override update at end of PWM period(1) or CPU clock boundary(0)
 979 
 980 
981 //enable PWM controller(1) SET THIS LAST<br>982 PTCONbits.PTEN=1; // Enable(1)
                                                       \frac{1}{2} Enable(1) or Disable(0) PWM timebase
 983
```
984 }

 910 } 911 912  $913$ <br>914 //-

915 // Initilize PWM generator

```
 985 
 986 
987<br>988 //-
 988 //----------------------------------------------------------------------------- 
 989 // Initilize UART for serial communication 
 990 //----------------------------------------------------------------------------- 
 991 void uartsetup(void){ 
 992 // Set Up UART TX side 
 993 
         TRISEbits.TRISE7=0; // Alt UART TX as output(0)
995 TRISEbits.TRISE6=1; // Alt UART RX as input(1)
996<br>997
         U1BRG=194; \frac{1}{9600 \text{ Baud}} for tcy=30MHz (frc hi and 32x pll)
 998 
999 U1MODE=0x8000; // Enable, 8data, no parity, 1 stop<br>1000 U1STAbits.URXISEL=0b00; // URXISEL<1:0>: Receive
1000 U1STAbits.URXISEL=0b00; // URXISEL<1:0>: Receive Interrupt Mode Selection bit<br>1001 // (Interupt when 11=>buffer full. 10=>buffer 3/4 full. 0x=>character is
1001 // (Interupt when 11=>buffer full, 10=>buffer 3/4 full, 0x=>character is received) 1002 U1MODEbits.ALTIO = 1; // Alt UART io pins
1002 U1MODEbits.ALTIO = 1;<br>1003 U1MODEbits.UARTEN = 1;
1003 U1MODEbits.UARTEN = 1; // UART enabled(1) or disabled(0)<br>1004 U1STAbits.UTXEN = 1; // UART transmitter enabled(1) or disa
                                                      1/1000 UART transmitter enabled(1) or disabled(0) (UARTEN=1 must be set prior to this)
1005
1006 //Receiver interupt initialize<br>1007 / IFS0bits.U1RXIF = 0:
1007 IFS0bits.U1RXIF = 0; // set interupt flag to 0<br>1008 IPC2bits.U1RXIP = 4; // set priority level 7 = z1008 IPC2bits.U1RXIP = 4; // set priority level 7=>highest, 1=>lowest, 0=>disabled 1009 IEC0bits.U1RXIE = 1; // enable reciever interupt
                                                   1/1 enable reciever interupt
1010 } 
1011 
\frac{1012}{1013}//-
1013 //----------------------------------------------------------------------------- 
1014 // Setup ADC to scan analog inputs 
1015 //----------------------------------------------------------------------------- 
1016 
1017 void adcsetup(void) { 
1018<br>1019
1019 ADPCFG=0b11111111111110000; // PCFG[15..0] A/D Port Configuration Control bits enable(0) pin as ADC or disable(1) for digital I/O<br>1020 TRISB=0b11111111111111111; // TRISB[15..0] set to 1 to connect pin tri-state buffe
          TRISB =0b11111111111111111; // TRISB[15..0] set to 1 to connect pin tri-state buffer to input
1021<br>1022
1022 ADCONbits.ADSIDL=0; // Stop(1) in Idle Mode or run(0)<br>1023 ADCONbits.FORM=0; // Data Output Format bit fraction1023 ADCONbits.FORM=0; // Data Output Format bit fractional(1) or decimal(0)<br>1024 ADCONbits.EIE=0; // Early Interrupt Enable bit after first conversion(1) or s
          ADCONbits.EIE=0; // Early Interrupt Enable bit after first conversion(1) or second(0)<br>ADCONbits.ORDER=0; // Conversion Order bit first chanels to convert are odd(1) or e
1025 ADCONbits.ORDER=0; // Conversion Order bit first channels to convert are odd(1) or even(0) 1026 // in the dsPIC30f2020 ADC conversions are preformed in pairs 01.23.45 etc
1026 // in the dsPIC30f2020 ADC conversions are preformed in pairs 01,23,45 etc 1027 // after conversion they show up sequentialy in the ADCBUFx variable
1027 // after conversion they show up sequentialy in the ADCBUFx variable 1028 // this sets wether the odd or even channel is converted first
1028 // this sets wether the odd or even channel is converted first 1029 ADCONbits.SEQSAMP=1; // Sequential Sample Enable(1) or disable(0)
1029 ADCONbits.SEQSAMP=1; // Sequential Sample Enable(1) or disable(0) controlles if set and holds of the ADC<br>1030 // pair are triggered at the same time(first conversion) or during senerate conversions
          \ell pair are triggered at the same time(first conversion) or during seperate conversions<br>ADCONbits.ADCS=0b011: \ell ADCSI2..01A/D Conversion Clock Divider Select bits(0-7) => Fa
1031 ADCONbits.ADCS=0b011; // ADCS[2..0]A/D Conversion Clock Divider Select bits(0-7) => Fadc/(4+2*ADCS)<br>1032 ADSTAT=0: // (5..0) Conversion Data for Pair #x Ready bits
                                               1/2 [5..0] Conversion Data for Pair #x Ready bits
1033 
1034 
1035 // ADCPC0bits.TRGSRC0=0b00001; //Trigger 0 Source Selection bits for channels AN0 and AN1 
1036 // ADCPC0bits.TRGSRC1=0b00001; //Trigger 1 Source Selection bits for channels AN2 and AN3<br>1037 ADCPC0bits.TRGSRC0=0b01100: //Trigger 0 Source Selection bits for channels AN0 and AN1
1037 ADCPC0bits.TRGSRC0=0b01100; //Trigger 0 Source Selection bits for channels AN0 and AN1<br>1038 ADCPC0bits.TRGSRC1=0b01100; //Trigger 1 Source Selection bits for channels AN2 and AN3
1038 ADCPC0bits.TRGSRC1=0b01100; //Trigger 1 Source Selection bits for channels AN2 and AN3<br>1039 //ADC trigger selection
                                     //ADC trigger selection
1040 //0b00001 = software trigger<br>1041 // For SW trigger, set AD
1041 // For SW trigger, set ADCPC0bits.SWTRG1=1;<br>1042 //0b00010 = Global software trigger selected
1042 //0b00010 = Global software trigger selected<br>1043 // For global SW trigger set ADCONbits.
1043 // For global SW trigger set ADCONbits.GSWTRG=1; must be cleared afer conversion 1044 //0b00011 = PWM Special Event Trigger selected
1044 //0b00011 = PWM Special Event Trigger selected<br>1045 //0b00100 = PWM generator #1 trigger selected
1045 //0b00100 = PWM generator #1 trigger selected<br>1046 //0b01100 = Timer #1 period match
1046 //0b01100 = Timer #1 period match<br>1047 //0b01101 = Timer #2 period match
                                     1001101 = Timer #2 period match
1048<br>1049
1049 ADCPC0bits.IRQEN1=1; //Interrupt Request Enable of channels AN3 and AN2 Enable(1) or disable(0) 1050 ADCPC0bits.IROEN0=1; //Interrupt Request Enable of channels AN1 and AN0 Enable(1) or disable(0)
                                                       1nterrupt Request Enable of channels AN1 and AN0 Enable(1) or disable(0)
1051 
1052 
1053 IFS0bits.ADIF=0; // Clear(0) ADC Interrupt Flag<br>1054 IPC2bits ADIP=6; // set priority level 7=>highest
          IPC2bits.ADIP=6; \frac{1}{2} // set priority level 7=>highest, 1=>lowest, 0=>disabled<br>IEC0bits.ADIE=1: \frac{1}{2} // ADC Interrupt Enable(1) or Disable(0)
1055 IEC0bits.ADIE=1; // ADC Interrupt Enable(1) or Disable(0)
1056<br>1057
          ADCONbits.ADON=1; // A/D Operating Mode bit Enable(1) or Disable(0) ADC operation
1058 } 
1059
```
1060 1061  $\frac{1062}{1063}$  //-1063 //--- 1064 // Sets up timers and timer interupts 1065 //--- 1066 void timersetup(void) { 1067 1068 SRbits.IPL = 3; // CPU interupt priority levels<br>1069 INTCON1bits.NSTDIS=1; // Disable(1) or enable  $1/10$  Disable(1) or enable(0) nested interupts 1070 1071 // Set up TMR1 for ADC trigger<br>1072 T1CONbits.TCS=0; // 1072 T1CONbits.TCS=0;  $\frac{1}{2}$  // 1=> external clock from TxCK, 0=> internal clk 1073 T1CONbits.TCKPS=0b01: // prescale: 0b00=>clk/1. 0b01=>clk/8. 0b10=> T1CONbits.TCKPS=0b01; // prescale: 0b00=>clk/1, 0b01=>clk/8, 0b10=>clk/64, 0b11=>clk/256<br>T1CONbits.TGATE=0; // gated time accululation: 1=>enable, 0=>disable 1074 T1CONbits.TGATE=0; // gated time accululation: 1=>enable, 0=>disable<br>1075 T1CONbits.TSIDL=1; // stop timer in idle: 1=>disable, 0=>enable 1075 T1CONbits.TSIDL=1; // stop timer in idle: 1=>disable, 0=>enable<br>1076 TMR1=0; // clear timer register // clear timer register 1077 // Set up TMR1 interupts<br>1078 PR1=10000; 1078 PR1=10000; // Interrupt after this many cycles (testing)<br>1079 IPC0bits.T1IP = 6; // set priority level 7=>highest, 1=>lowes 1079 IPC0bits.T1IP = 6; // set priority level  $7 = >$ highest, 1=>lowest, 0=>disabled 1080 IFS0bits.T1IF = 0; // clear interrupt flag, set when timer=PRx 1080 IFS0bits.T1IF = 0; // clear interrupt flag, set when timer=PRx 1081 T1CONbits.TON=1; // 1=> start timer, 0=> stop timer 1081 T1CONbits.TON=1;  $\text{/}/\text{1} \Rightarrow$  start timer, 0=> stop timer<br>1082 IECObits.T1IE = 1;  $\text{/}/\text{1} \Rightarrow$  enable interrupts. 0=> disable  $11$  =  $\epsilon$  enable interrupts, 0= $\epsilon$  disable interupts 1083 1084 // Set up TMR2 for PWM pulse time 1085 T2CONbits.TCS=0;  $// 1=>$  external clock from TxCK,  $0=>$  internal clk<br>1086 T2CONbits.TCKPS=0b10:  $//$  prescale: 0b00=>clk/1.0b01=>clk/8.0b10=> T2CONbits.TCKPS=0b10; // prescale: 0b00=>clk/1, 0b01=>clk/8, 0b10=>clk/64, 0b11=>clk/256<br>T2CONbits.TGATE=0; // gated time accululation: 1=>enable, 0=>disable 1087 T2CONbits.TGATE=0; // gated time accululation: 1=>enable, 0=>disable 1088 T2CONbits.TSIDL=1; // stop timer in idle: 1=>disable, 0=>enable  $1/8$  stop timer in idle: 1=>disable, 0=>enable 1089 TMR1=0; // clear timer register 1090 // Set up TMR2 interupts<br>1091 PR2=469; 1091 PR2=469; // Interrupt after this many cycles (4692=10ms at clk/64, 1173=10ms at clk/256)<br>1092 IPC1bits.T2IP = 6; // set priority level 7=>highest, 1=>lowest, 0=>disabled  $10P21 bits.T2 IP = 6;$  // set priority level  $7 \Rightarrow$  highest, 1=>lowest, 0=>disabled IFS0bits.T2IF = 0; // clear interrupt flag, set when timer=PRx 1093 IFS0bits.T2IF = 0; // clear interrupt flag, set when timer=PRx 1094 T2CONbits.TON=0; // 1=> start timer, 0=> stop timer 1094 T2CONbits.TON=0;  $\text{/}$  1 = > start timer, 0= > stop timer<br>1095 IECObits.T2IE = 0;  $\text{/}$  / 1 = > enable interrupts, 0 = > disable  $11$  =  $>$  enable interrupts, 0= $>$  disable interupts 1096 1097 // Set up TMR3 for I/O control<br>1098 T3CONbits.TCS=0; 1098 T3CONbits.TCS=0;  $\text{/}/\text{1}$  => external clock from TxCK, 0=> internal clk<br>1099 T3CONbits.TCKPS=0b11;  $\text{/}/\text{prescale}: 0b00 = \text{c} \cdot \text{lk/1}, 0b01 = \text{c} \cdot \text{lk/8}, 0b10 = \text{c}$ T3CONbits.TCKPS=0b11; // prescale: 0b00=>clk/1, 0b01=>clk/8, 0b10=>clk/64, 0b11=>clk/256<br>T3CONbits.TGATE=0; // gated time accululation: 1=>enable, 0=>disable 1100 T3CONbits.TGATE=0; // gated time accululation: 1=>enable, 0=>disable 1101 T3CONbits.TSIDL=1; // stop timer in idle: 1=>disable, 0=>enable T3CONbits.TSIDL=1; // stop timer in idle: 1=>disable, 0=>enable<br>TMR3=0: // clear timer register 1102 TMR3=0; // clear timer register 1103 // Set up TMR3 interupts<br>1104 IPC1bits.T3IP = 4: 1104 IPC1bits.T3IP = 4; // set priority level 7=>highest, 1=>lowest, 0=>disabled<br>1105 PR3=10000 // Interrunt after this many cycles PR3=10000;  $\frac{1}{15}$  // Interrupt after this many cycles<br>IFS0bits T3IF = 0:  $\frac{1}{2}$  // clear interrupt flag set when the 1106 IFS0bits.T3IF = 0; // clear interrupt flag, set when timer=PRx<br>1107 T3CONbits TON=1: // 1=> start timer 0=> stop timer  $111$  T  $115$  start timer, 0=> stop timer 1108 IEC0bits.T3IE = 1;  $\qquad$  // 1=> enable interrupts, 0=> disable interupts 1109 1110 } 1111 1112 1113 //--- 1114 // Prints signed int as ASCII string on serial port (-32768 to +32767) 1115 //--- 1116 void printSerial\_signed\_int(signed int val) { 1117 int index=0;<br>1118 char str6[6]; char str6[6];  $\frac{1}{6}$  //6 char string 1119 1120 //determins sign<br>1121 if(val<0){  $1121$  if(val < 0){<br>1122 val = - val  $1122$  val=-val;<br> $1123$  str6[0]='- $1123$  str6[0]='-';<br>1124 \else{ 1124 }else{<br>1125 str6 str6[0]='+'; 1126 1127 //build num string 1128 for(index=5;index>=1;index--){<br>1129 str6lindex]=(val%10 + '0'):  $str6[index] = (val\%10 + '0');$ 1130 val=val/10;  $\frac{1131}{1132}$ 1132 //transmit string<br>1133 if((U1MODEbit if((U1MODEbits.UARTEN == 1)&&(U1STAbits.UTXEN =1)){ // only transmit of uart and uart tx are enabled 1134 for(index=0;index<=6;index++){

1135 while(U1STAbits.UTXBF==1);<br>1136 U1TXREG=str6[index]; 1136 U1TXREG=str6[index];<br>1137 *Wend for* 1137  $\frac{1}{2}$  //end for<br>1138  $\frac{1}{2}$  //end if  $1$ //end if 1139 1140 } 1141 1142 //--- 1143 // Prints unsigned int as ASCII string on serial port (0 to 65535) 1144 //--- 1145 void printSerial\_int(unsigned int val) { 1146 int index=0;<br>1147 char str5[5];  $1/5$  char string 1148 //build num string 1150 for(index=0;index<5;index++){<br>1151 str5[4-index]=(val%10 + '0'); 1151  $str5[4\text{-}index] = (val\%10 + 0');$ <br>1152  $val = val/10;$  $val=val/10;$ 1153 } 1154 //transmit string<br>1155 if((U1MODEbit 1155 if((U1MODEbits.UARTEN == 1)&&(U1STAbits.UTXEN =1)){ // only transmit of uart and uart tx are enabled 1156 for(index=0:index = 4:index + + ){ 1156 for(index=0;index<=4;index++){ 1157 while((U1STAbits.UTXBF==1));//wait while buffer full or tx register not empty 1158 U1TXREG=str5[index];<br>1159 while((U1STAbits TRM) while((U1STAbits.TRMT==0));//wait while buffer full or tx register not empty 1160 }//end for 1161 }//end if 1162 } 1163  $\frac{1164}{1165}$ //---1165 //--- 1166 // Prints literial ASCII value from variable on serial port  $1167$  //--1168 void printSerial\_ASCII(char value) { 1169 if((U1MODEbits.UARTEN == 1)&&(U1STAbits.UTXEN =1)){ // only transmit of uart and uart tx are enabled 1170 while((U1STAbits.UTXBF==1));//wait while buffer full or tx register not empty 1170 while((U1STAbits.UTXBF==1));//wait while buffer full or tx register not empty<br>1171 U1TXREG=value; 1171 U1TXREG=value;<br>1172 while((U1STAbits.) while((U1STAbits.TRMT==0));//wait while buffer full or tx register not empty 1173 }//end if 1174 }  $1175$ <br> $1176$  //-1176 //--- 1177 // Prints string of ASCII characters on serial port from RAM 1178 //--- 1179 void printSerial\_str(char \* str) { 1180 int  $i = 0$ ; 1181<br>1182 if((U1MODEbits.UARTEN == 1)&&(U1STAbits.UTXEN =1)){ // only transmit of uart and uart tx are enabled 1183 while(str[i]!=0) { 1184 while((U1STAbits.UTXBF==1));//wait while buffer full or tx register not empty<br>1185 U1TXREG=str[i]: U1TXREG=str[i]; 1186 i++;<br>1187 whil 1187 while((U1STAbits.TRMT==0));//wait while buffer full or tx register not empty 1188 }//end while 1188  $\frac{1}{\sqrt{end}}$  if<br>1189  $\frac{1}{\sqrt{end}}$  if  $\frac{1}{2}$ //end if 1190 }  $1191$ <br> $1192$  //-1192 //--- 1193 // Prints string of ASCII characters on serial port from program memory 1194 //--- 1195 void printSerialROM\_str(const char \* str) { 1196 int  $i = 0$ ; 1197<br>1198 1198 if((U1MODEbits.UARTEN == 1)&&(U1STAbits.UTXEN =1)){ // only transmit of uart and uart tx are enabled while(str[il!=0) { 1199 while(str[i]!=0) {<br>1200 while((U1STA) while( $(U1STAbits.UTXBF==1)$ );//wait while buffer full or tx register not empty 1201 U1TXREG=str[i];  $1202$  i++;<br>1203 while 1203 while((U1STAbits.TRMT==0));//wait while buffer full or tx register not empty 1204  $\frac{1}{2}$ }//end while 1205 }//end if 1206 } 1207  $1208$  //--1209 // Convert int into a binary ascii string

```
1210 //--------
1211 void printSerial_binary_int(unsigned int val){
1212 int index=0;
1213 
1214 //transmit string<br>1215 if((U1MODEbit)
         if((U1MODEbits.UARTEN == 1)&&(U1STAbits.UTXEN =1)){ // only transmit of uart and uart tx are enabled
1216 for(index=15;index>=0;index--){
1217 U1TXREG=(testbit(val,index)+'0');
1218 while((U1STAbits.UTXBF==1)|( U1STAbits.TRMT==0));//wait while buffer full or tx register not empty 1219 }//endfor
          1219 }//endfor 
1220 }//end if 
1221 } 
1222 
1223<br>1224 //--
1224 //----------------------------------------------------------------------------- 
1225 // Convert numeric ascii string to an unsigned int 
1226 //----------------------------------------------------------------------------- 
1227 int str_to_int(char * str){ 
1228 int result=0;
1229 int index=0; 
1230 int digit=0; 
1231 
1232 for ( index = 0; (str[index]!=\0')&(index <= 4); ++index ){<br>1233 digit=str[index] - 0; //get the ascii char valua an
1233 digit=str[index] - 0'; //get the ascii char valua and convert to numeric digit<br>1234 result=10*result + digit; //add the digit to the result and multiply old result
                                                    1/2 //add the digit to the result and multiply old result by 10
1235 } 
1236 
1237 return(result); 
1238 } 
1239 
1240 
1241 //----------------------------------------------------------------------------- 
1242 // Parse received string for commands 
1243 //----------------------------------------------------------------------------- 
1244 // Dty=100; //duty cycle = 100% (varies between 50-100%)<br>1245 // PWMfreq=200; //PWMfreq controls PWM frequency 200 =
                                         //PWMfreq controls PWM frequency 200 = > 20kHz
1246 
1247 void parse_string(char * str){<br>1248 int i=0;<br>//strin
1248 int i=0; \frac{1248 \text{ int}}{249 \text{ int}} cnum=0; //string index
                                      \frac{1}{2} //converted number
1250 char str6[6];
1251 
1252 
1253 //if numeric input, then expect to set a variable 1254 if(str[0] == \^{\circ}\ //expected first char for r
                                1/expected first char for numeric input
1255 for(i=0;(str[i]!='\0')&(i<=4);i++){
1256 str6[i]=str[(i+1)];<br>1257 1/41257 }//end for<br>1258 str6[5]-
             str6[5] = \0;
1259<br>1260
             cnum=str_to_int(str6); //converted number
1261<br>1262
1262 printSerialROM_str("\r\nNumber received= \0");<br>1263 printSerial_int(cnum); //display conveted num
1263 printSerial_int(cnum); //display conveted number 1264 //set pwm frequency
         1/8et pwm frequency
1265 if((str[7]=='f')&(str[8]=='r')&(str[9]=='e')&(str[10]=='q')&(str[11]=='\0')){<br>1266 if((cnum>=Fres)&(cnum<=Frax)){
1266 if((cnum>=Fres)&(cnum<=Fmax)){<br>1267 PWMfreq=cnum;
1267 PWMfreq=cnum;<br>1268 printSerialROM_s
1268 printSerialROM_str(freqString);<br>1269 printSerial_int(PWMfreq);
1269 printSerial_int(PWMfreq);<br>1270 printSerialROM str(NL);
                 printSerialROM_str(NL);
\begin{array}{ccc} 1271 & & \frac{1}{2} \\ 1272 & & \text{el} \end{array}1272 else{<br>1273 print:
                 printSerialROM_str(InvalidNumberString); // print string to terminal
\begin{array}{ccc} 1274 & & \end{array}<br>1275 }//e
              1//end if
1276 //set duty cycle 
1277 else if((str[7]=='d')&(str[8]=='t')&(str[9]=='y')&(str[10]=='\0')){
1278 if((cnum>=Dtymin)&(cnum<=Dtymax))\{<br>1279 Dtv=cnum:
                 Dty=cnum;
1280 printSerialROM_str(dtyString);<br>1281 printSerial int(Dtv);
1281 printSerial_int(Dty);<br>1282 printSerialROM str(1)
                 printSerialROM_str(NL);
1283 } 
                 else{
```
1285 printSerialROM str(InvalidNumberString); // print string to terminal 1286 } 1287  $\frac{1}{288}$  //end if 1288 //set pulse time<br>1289 else if((str[7] 1289 else if((str[7]=='p')&(str[8]=='t')&(str[9]=='i')&(str[10]=='m')&(str[11]=='e')&(str[12]=='\0')){<br>1290 if((cnum>=1)&(cnum<=100)){  $if((cnum>=1)$ &(cnum<=100)){ 1291 Ptime=cnum; 1292 printSerialROM\_str(ptimeString); 1293 printSerial\_int(Ptime);<br>1294 printSerialROM str(N printSerialROM\_str(NL); 1295<br>1296 1296 else{<br>1297 print printSerialROM\_str(InvalidNumberString); // print string to terminal  $\begin{array}{ccc} 1298 & & \cdot \\ 1299 & & \frac{1}{e} \end{array}$  $1299$   $\frac{}/\sqrt{}$ end if<br>1300  $\frac{}/\sqrt{}$ set voltag 1300 //set voltage output setpoint<br>1301 less if  $((str[7]=v')\&(str[8])$ 1301 else if((str[7]=='v')&(str[8]=='s')&(str[9]=='e')&(str[10]=='t')&(str[11]=='\0')){<br>1302 if((cnum>=0)&(cnum<=Vlimit)){ 1302 if((cnum>=0)&(cnum<=Vlimit)){<br>1303 Vset=cnum; 1303 Vset=cnum;<br>1304 printSerialR 1304 printSerialROM\_str(vsetString);<br>1305 printSerial\_int(Vset); 1305 printSerial\_int(Vset);<br>1306 printSerialROM str(N) printSerialROM\_str(NL); 1307<br>1308 1308 else{<br>1309 print: printSerialROM\_str(InvalidNumberString); // print string to terminal 1310 } 1311 }//end if 1312 //set voltage limit setpoint<br>1313 else if((str[7]=='v')&(str else if((str[7]=='v')&(str[8]=='l')&(str[9]=='i')&(str[10]=='m')&(str[11]=='i')&(str[12]=='t')&(str[13]=='\0')){ 1314  $if((cnum>=0))$ {<br>1315  $V$ limit=cnum 1315 Vlimit=cnum;<br>1316 printSerialRO 1316 printSerialROM\_str(vlimitString);<br>1317 printSerial\_int(Vlimit); 1317 printSerial\_int(Vlimit);<br>1318 printSerialROM\_str(NL 1318 printSerialROM\_str(NL);<br>1319 if(Vset>Vlimit){Vset=Vli if(Vset>Vlimit){Vset=Vlimit;} //reset Vset to Vlimit in required 1320 }<br>1321 el 1321 else{<br>1322 print printSerialROM\_str(InvalidNumberString); // print string to terminal 1323 }  $}/\ell$ end if 1325 //set Kpfreq<br>1326 else if((sti 1326 else if((str[7]=='k')&(str[8]=='p')&(str[9]=='\0')){<br>1327 if((cnum>=0)){  $1327$  if((cnum $>=0$ )){<br>1328 Kpfreq=cnum: 1328 Kpfreq=cnum;<br>1329 printSerialROM 1329 printSerialROM\_str(kpString);<br>1330 printSerial int(Kpfreq); 1330 printSerial\_int(Kpfreq);<br>1331 printSerialROM str(NL) printSerialROM\_str(NL); 1332 } 1333 else{ 1334 printSerialROM\_str(InvalidNumberString); // print string to terminal 1335 } 1336 }//end if<br>1337 //set Kifreq 1337 //set Kifreq<br>1338 else if((s) 1338 else if((str[7]=='k')&(str[8]=='i')&(str[9]=='\0')){<br>1339 if((cnum>=0)){ 1339 if((cnum>=0)){<br>1340 Kifreq=cnum; 1340 Kifreq=cnum;<br>1341 printSerialROI 1341 printSerialROM\_str(kiString);<br>1342 printSerial\_int(Kifreq); 1342 printSerial\_int(Kifreq);<br>1343 printSerialROM\_str(NL printSerialROM\_str(NL); 1344 } 1345 else{<br>1346 print printSerialROM\_str(InvalidNumberString); // print string to terminal 1347 } 1348  $\frac{1}{\pi}$  //end if 1349 //if no valid input<br>1350  $\frac{1}{2}$  else<sup>{</sup> 1350 else{<br>1351 pri  $\text{printSerialROM\_str(InvalidString);}$  //  $\text{print}$  received string to terminal  $1352$   $\frac{1}{\sqrt{e}}$  else 1353<br>1354 }//end numeric set if 1355 1356 //manual pulse trigger<br>1357 else if $((str[0]=2p')d$ 1357 else if((str[0]=='p')&(str[1]=='u')&(str[2]=='l')&(str[3]=='s')&(str[4]=='e')&(str[5]=='\0')){<br>1358 if((IOCON1bits.OVRENH==1)&(PSCONFIG.PWMlockout==0)){ // If the timer is 1358 if((IOCON1bits.OVRENH==1)&(PSCONFIG.PWMlockout==0)){ // If the timer isnt running and lockout disabled printSerialROM\_str(PulseString); printSerialROM\_str(PulseString);

1360 if((Vin<Vinmin)&(PSCONFIG.dummypulse==0)){<br>1361 PSCONFIG.PSerror=1; //set power supply 1361 PSCONFIG.PSerror=1; //set power supply error flag<br>1362 PSCONFIG.lowVin=1; //set DC link undervolt flag 1362 PSCONFIG.lowVin=1; //set DC link undervolt flag<br>1363 PWMstop(); //shut down power supply //shut down power supply  $\begin{array}{cc} 1364 & 1 \\ 1365 & 1 \end{array}$ else{ 1366 PWMstart(); // start pulse timer and enable outputs 1367 } 1368 }<br>1369 }//e }//end pulse trigger else if 1370 1371 //software reset<br>1372 else if((str[0] 1372 else if((str[0]=='r')&(str[1]=='e')&(str[2]=='s')&(str[3]=='e')&(str[4]=='t')&(str[5]=='\0')){<br>1373 RCON=0x0000; 1373 RCON=0x0000;<br>1374 printSerialROM\_ 1374 printSerialROM\_str("\r\n\r\nRCON= \0");<br>1375 printSerial\_binary\_int(RCON); 1375 printSerial\_binary\_int(RCON);<br>1376 printSerialROM\_str(ResetInitSt 1376 printSerialROM\_str(ResetInitString);<br>1377 asm("RESET"); 1377 asm("RESET");<br>1378 }//end else if }//end else if 1379 1380 //display data<br>1381 else if((str[0] 1381 else if((str[0]=='d')&(str[1]=='a')&(str[2]=='t')&(str[3]=='a')&(str[4]=='\0')){ 1382 ProgCON.PSDataReady=1; //print PWM data to console 1383 }//end else if 1384 1385 //dummy pulse<br>1386 – else if $((str0)$ 1386 else if((str[0]=='d')&(str[1]=='p')&(str[3]=='\0')){ 1387 PSCONFIG.dummypulse=1; //set dummypulse flag 1388 printSerialROM\_str("\r\nDummypulse selected, saftey checks disabled \0"); 1389 }//end else if 1390 1391 //help menu<br>1392 else if((sti 1392 else if((str[0]=='h')&(str[1]=='e')&(str[2]=='l')&(str[3]=='p')&(str[4]=='\0')){<br>1393 printSerialROM\_str("\r\nValid Commands:\r\n\$xxxx freq (sets PWM freq ( 1393 printSerialROM\_str("\r\nValid Commands:\r\n\$xxxxx freq (sets PWM freq 00200=20kHz, 00250>=freq>=00150)\0");<br>1394 printSerialROM\_str("\r\n\$xxxxx dty (sets PWM duty cycle 00100=100%, 00100>=dty>=00050)\0"); 1394 printSerialROM\_str("\r\n\$xxxxx dty (sets PWM duty cycle 00100=100%, 00100>=dty>=00050)\0");<br>1395 printSerialROM\_str("\r\n\$xxxxx ptime (sets pulse time 00100=10ms, 00100>=ptime>=00001)\0"); 1395 printSerialROM\_str("\r\n\$xxxxx ptime (sets pulse time 00100=10ms, 00100>=ptime>=00001)\0");<br>1396 printSerialROM\_str("\r\n\$xxxxx vset (sets output voltage 08000=>80kV, 00000<=vset<=V1imit)\0 1396 printSerialROM\_str("\r\n\$xxxxx vset (sets output voltage 08000=>80kV, 00000<=vset<=Vlimit)\0");<br>1397 printSerialROM\_str("\r\n\$xxxxx vlimit(sets crowbar voltage limit 08500=>85kV, 00000<=Vlimit)\0"); 1397 printSerialROM\_str("\r\n\$xxxxx vlimit(sets crowbar voltage limit 08500=>85kV, 00000<=Vlimit)\0");<br>1398 printSerialROM\_str("\r\npulse (triggers output pulse)\r\ndp(enables dummy pulse)\0"); 1398 printSerialROM\_str("\r\npulse (triggers output pulse)\r\ndp(enables dummy pulse)\0");<br>1399 printSerialROM\_str("\r\ndata (prints out power supply operation data)\0"); printSerialROM\_str("\r\ndata (prints out power supply operation data)\0"); 1400 printSerialROM\_str("\r\nreset (dsPIC hardware reset)\r\n\0");<br>1401 }//end help else if  $\frac{1}{2}$ //end help else if 1402<br>1403 1403 //for all other input<br>1404 else { 1404 else {<br>1405 pri 1405 printSerialROM\_str(InvalidString); // print string to terminal<br>1406  $\frac{1}{\sqrt{2}}$  //end else  $1$ //end else 1407 1408 printSerialROM\_str(NL); 1409 }//end of sub

1410